

'Assignment-02'

Amirun Nahin

ID: 23201416

Sec: 06-A

Course: CSE350

Date: 28-03-2026

Answer to the question no-01

(a)

from the given circuit,

$$\begin{aligned}\text{total resistance in the ladder} &= \frac{R}{2} + R + R + \frac{3R}{2} \\ &= \frac{R + 2R + 2R + 3R}{2} \\ &= \frac{8R}{2} \\ &= 4R\end{aligned}$$

Now, using voltage divider rule,

$$V_1 = \frac{\frac{R}{2}}{4R} \times (8-0) = \frac{R}{2} \times \frac{1}{4R} \times 8 = 1V$$

$$V_2 = \frac{R + \frac{R}{2}}{4R} \times (8-0) = \frac{3R}{2} \times \frac{1}{4R} \times 8 = 3V$$

$$V_3 = \frac{R + R + \frac{R}{2}}{4R} \times (8-0) = \frac{5R}{2} \times \frac{1}{4R} \times 8 = 5V$$

So, the table listing the quantization intervals:

Quantization Range	Quantization level	Digital output
0-1	0.5	00
1-3	2	01
3-5	4	10
5-8	6.5	11

(b)

The maximum digital input to the DAC is 11 since it is a 2bit DAC.

Now, given that,

$$V_{out} = -6.5$$

$$\Rightarrow -\frac{R_f}{2R} \left(V_{B1} + \frac{V_{B0}}{2} \right) = -6.5$$

$$\Rightarrow -\frac{13}{2R} \left(5 + \frac{5}{2} \right) = -6.5$$

$$\Rightarrow -\frac{13}{2R} \times \frac{15}{2} = -6.5$$

$$\Rightarrow \frac{1}{R} \times -\frac{195}{4} = -6.5$$

$$\Rightarrow R = 7.5 \text{ k}\Omega$$

We can calculate the step-size from 1LSB voltage,

$$V_{out} = -\frac{R_f}{2R} \times \left(\frac{5}{2} + 0 \right)$$

$$= -\frac{13}{2 \times 7.5} \times \frac{5}{2}$$

$$= -2.167 \text{ V}$$

So, the resistor's value is $7.5 \text{ k}\Omega$ and step size

is -2.167 V .

Now, output voltages of the remaining inputs are:

input 00:

$$\begin{aligned} V_{out} &= \frac{-R_f}{2R} \times (0+0) \\ &= 0 \text{ V} \end{aligned}$$

input 01:

$$\begin{aligned} V_{out} &= \frac{-R_f}{2R} \times \left(0 + \frac{5}{2}\right) \\ &= \frac{-13}{2 \times 7.5} \times \left(\frac{5}{2}\right) \\ &= -2.167 \text{ V} \end{aligned}$$

input 10:

$$\begin{aligned} V_{out} &= \frac{-R_f}{2R} \times (5+0) \\ &= \frac{-13}{2 \times 7.5} \times 5 \\ &= -4.33 \text{ V} \end{aligned}$$

input 11:

$$\begin{aligned} V_{out} &= \frac{-R_f}{2R} \times \left(5 + \frac{5}{2}\right) \\ &= \frac{-13}{2 \times 7.5} \times \left(\frac{15}{2}\right) \\ &= -6.5 \text{ V} \end{aligned}$$

(Ans.)

(c)

from (a) and (b),

digital output for $V_{in} = 5.5V$ is 11.

Now, output voltage,

$$\begin{aligned} V_{out} &= \frac{-R_f}{2R} \times \left(V_{B1} + \frac{V_{B0}}{2} \right) \\ &= \frac{-13}{2 \times 7.5} \times \left(5 + \frac{5}{2} \right) \\ &= -6.5V \end{aligned}$$

(Ans.)

(d)

Given,

$$n = 2$$

$$f = 2 \times 10^6 \text{ Hz}$$

We know,

$$t_1 = 2^n T_c$$

$$\Rightarrow t_1 = 2^2 \times \frac{1}{2 \times 10^6}$$

$$\Rightarrow t_1 = 2 \times 10^{-6} \text{ s}$$

$$\Rightarrow t_1 = 2 \mu\text{s}$$

given,

$$\text{conversion time} = 2.7 \mu\text{s}$$

$$\Rightarrow t_1 + t_2 = 2.7$$

$$\Rightarrow t_2 = 2.7 - t_1$$

$$\Rightarrow t_2 = 2.7 - 2$$

$$\Rightarrow t_2 = 0.7 \mu s$$

Now,

$$\frac{V_{in}}{V_{ref}} \times t_1 = t_2$$

$$\Rightarrow V_{in} = \frac{t_2 \times V_{ref}}{t_1}$$

$$\Rightarrow V_{in} = \frac{0.7 \times 8}{2}$$

$$\Rightarrow V_{in} = 2.8 \text{ V}$$

and, maximum conversion time = $2t_1$
 $= 2 \times 2$
 $= 4 \mu s$

So, $V_{in} = 2.8 \text{ V}$ and $t_{max} = 4 \mu s$

(Ans.)

(e)

Given, $V_{in} = 5.5 \text{ V}$.

Now, we know,

$$\frac{V_{in}}{V_{ref}} \times t_1 = (N+1) \times \frac{1}{f}$$

$$\Rightarrow \frac{5.5}{8} \times 2 \times 10^{-6} = (N+1) \times \frac{1}{2 \times 10^6}$$

$$\Rightarrow \frac{5.5}{8} \times 2 \times 10^{-6} \times 2 \times 10^6 = (N+1)$$

$$N+1 = 2.75$$

$$\Rightarrow N = 1.75$$

$$\Rightarrow N \approx 1$$

$\therefore$ digital output is 01

So, output voltage,

$$V_{out} = -\frac{V_{ref}}{2} \times \frac{R_f}{2R} \times (2b_0 + b_1)$$

$$= -\frac{5}{2} \times \frac{13}{2 \times 7.5}$$

$$= -2.167 \text{ V}$$

$$\therefore \text{Error} = \left| \frac{-2.167 - (-6.5)}{-6.5} \right| \times 100\%$$

$$= 66.67\%$$

(Ans.)

Answer to the question no-02

(a)

from figure 3,

$$R_1 = 2 \text{ k}\Omega$$

$$R_2 = 8 \text{ k}\Omega$$

$$V_H = 4 \text{ V}$$

$$V_L = -8 \text{ V}$$

Now,

$$V_{TH} = \left(-\frac{R_1}{R_2} \right) \cdot V_L$$

$$= \left(-\frac{2}{8} \right) \cdot (-8)$$

$$= 2 \text{ V}$$

$$V_{TL} = \left(-\frac{R_1}{R_2} \right) \cdot V_H$$

$$= \left(-\frac{2}{8} \right) \cdot (4)$$

$$= -1 \text{ V}$$

$$\therefore T_1 = R_i \cdot C_i \left(\frac{V_{TH} - V_{TL}}{V_H} \right)$$

$$= R_i \cdot C_i \cdot \left(\frac{2+1}{4} \right)$$

$$T_1 = \frac{3}{4} R_i C_i$$

$$\begin{aligned}
 \text{and, } T_2 &= R_i \cdot C_i \cdot \left(\frac{V_{TL} - V_{TH}}{V_L} \right) \\
 &= R_i \cdot C_i \cdot \left(\frac{-1-2}{-8} \right) \\
 &= \frac{3}{8} R_i \cdot C_i
 \end{aligned}$$

$$\begin{aligned}
 \text{So, } T &= T_1 + T_2 \\
 &= \frac{3}{4} R_i C_i + \frac{3}{8} R_i C_i \\
 &= \frac{6R_i C_i + 3R_i C_i}{8} \\
 &= \frac{9}{8} R_i C_i
 \end{aligned}$$

So, the frequency, we know,

$$\begin{aligned}
 f &= \frac{1}{T} \\
 \Rightarrow f &= \frac{1}{\frac{9}{8} R_i C_i} \\
 \Rightarrow f &= \frac{8}{9 R_i C_i}
 \end{aligned}$$

(Ans.)

(b)

from 'a',

$$T_1 = \frac{3}{4} R_1 C_1$$

$$T_2 = \frac{3}{8} R_1 C_1$$

$$\text{Duty Cycle} = \left(\frac{T_1}{T_1 + T_2} \right) \times 100\%$$

$$= \left(\frac{\frac{3}{4} R_1 C_1}{\frac{3}{4} R_1 C_1 + \frac{3}{8} R_1 C_1} \right) \times 100\%$$

$$= 66.67\%$$

Now, we have to design a square wave generator having duty cycle 66.67%. Given,

$$R_1 = 10 \text{ k}\Omega,$$

$$R_2 = 20 \text{ k}\Omega,$$

$$R_x = 10 \text{ k}\Omega,$$

$$C_x = 50 \text{ nF} = 50 \times 10^{-9} \text{ F}$$

$$f = 1 \text{ kHz} = 1 \times 10^3 \text{ Hz}$$

$$\begin{aligned} \therefore \tau &= R_x C_x \\ &= 10 \times 10^3 \times 50 \times 10^{-9} \\ &= 5 \times 10^{-4} \text{ s} \end{aligned}$$

$$\therefore T = \frac{1}{f} = \frac{1}{1 \times 10^3} = 1 \times 10^{-3} \text{ s}$$

Now, $T_1 = \tau \ln \left(\frac{V_H - V_L}{V_H - V_{TH}} \right)$

$$= 5 \times 10^{-4} \times \ln \left(\frac{V_H - V_L \cdot \frac{R_1}{R_1 + R_2}}{V_H - V_H \cdot \frac{R_1}{R_1 + R_2}} \right)$$

$$= 5 \times 10^{-4} \times \ln \left(\frac{V_H - V_L \cdot \frac{10}{30}}{V_H - V_H \cdot \frac{10}{30}} \right)$$

$$= 5 \times 10^{-4} \ln \left(\frac{\frac{30V_H - 10V_L}{30}}{\frac{30V_H - 10V_H}{30}} \right)$$

$$= 5 \times 10^{-4} \ln \left(\frac{30V_H - 10V_L}{20V_H} \right)$$

Again,

$$T_2 = \tau \ln \left(\frac{V_L - V_{TH}}{V_L - V_{TL}} \right)$$

$$= 5 \times 10^{-4} \ln \left(\frac{V_L - V_H \cdot \frac{R_1}{R_1 + R_2}}{V_L - V_L \cdot \frac{R_1}{R_1 + R_2}} \right)$$

$$= 5 \times 10^{-4} \times \ln \left(\frac{V_L - V_H \cdot \frac{10}{30}}{V_L - V_L \cdot \frac{10}{30}} \right)$$

$$= 5 \times 10^{-4} \ln \left(\frac{\frac{30V_L - 10V_H}{30}}{\frac{30V_L - 10V_L}{30}} \right)$$

$$T_2 = 5 \times 10^{-4} \ln \left(\frac{30V_L - 10V_H}{20V_L} \right)$$

Now,

$$T_1 + T_2 = 1 \times 10^{-3}$$

$$\Rightarrow 5 \times 10^{-4} \times \ln \left(\frac{30V_H - 10V_L}{20V_H} \right) + 5 \times 10^{-4} \times \ln \left(\frac{30V_L - 10V_H}{20V_L} \right) = 1 \times 10^{-3}$$

$$\Rightarrow \ln \left(\frac{30V_H - 10V_L}{20V_H} \right) + \ln \left(\frac{30V_L - 10V_H}{20V_L} \right) = \frac{1 \times 10^{-3}}{5 \times 10^{-4}}$$

$$\Rightarrow \ln \left(\frac{30V_H - 10V_L}{20V_H} \cdot \frac{30V_L - 10V_H}{20V_L} \right) = 2$$

$$\Rightarrow \frac{(30V_H - 10V_L) \cdot (30V_L - 10V_H)}{400V_H \cdot V_L} = e^2$$

$$\Rightarrow \frac{900V_H V_L - 300V_H^2 - 300V_L^2 + 100V_H V_L}{400V_H V_L} = e^2$$

$$\Rightarrow \frac{1000V_H V_L - 300V_H^2 - 300V_L^2}{400V_H V_L} = e^2$$

Now, assuming $V_L = -10V$.

$$\Rightarrow \frac{1000 \cdot V_H \cdot (-10) - 300(V_H^2) - 300 \cdot (-10)^2}{400 \cdot V_H \cdot (-10)} = e^2$$


$$\Rightarrow -10000V_H - 300V_H^2 - 30000 = -29556.224V_H$$

$$\Rightarrow 300V_H^2 - 19556.224V_H + 30000 = 0$$

$$\therefore V_H = 1.57V$$

So, we get $V_H = 1.57V$ and $V_L = -10V$

Now, the circuit,

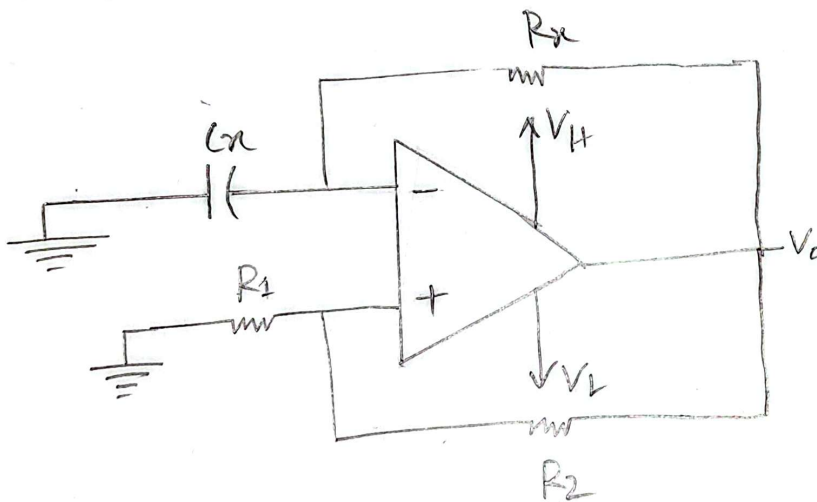

$$R_n = 10k\Omega$$

$$R_1 = 10k\Omega$$

$$R_2 = 20k\Omega$$

$$C_n = 50nF$$

$$V_H = 1.57V$$

$$V_L = -10V$$

(Ans)

Answer to the question no-03

(a)

from 'figure-4',


$$V_H = 8V$$

$$V_L = -7V$$

$$V_{TH} = 2V$$

$$V_{TL} = -1.5V$$

Now, VTC for the given schmitt trigger:

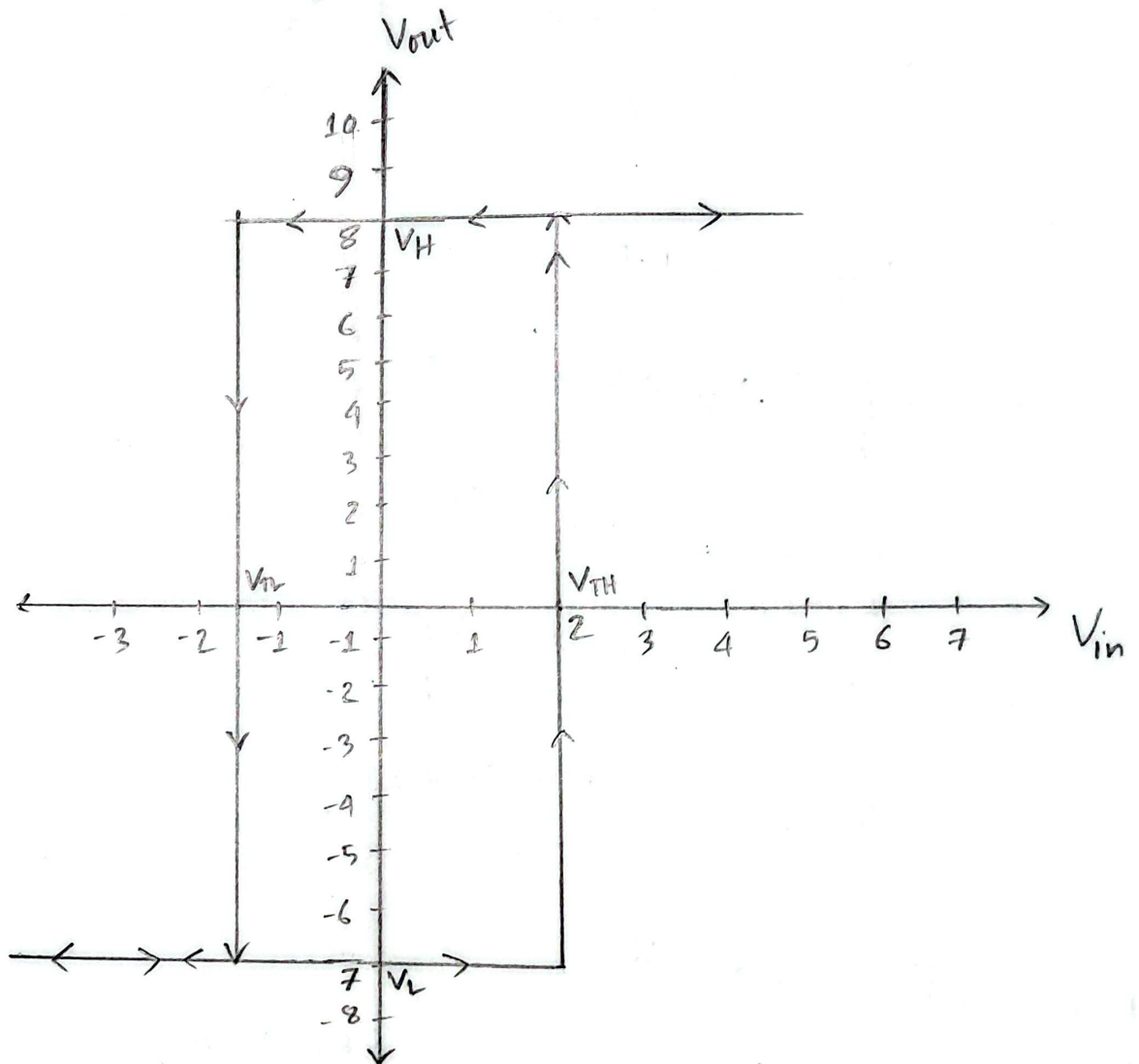

This is a VTC of Non-inverting schmitt trigger since the given schmitt trigger is a non-inverting schmitt trigger.

(b)

from 'a', we got,

$$V_{TH} = 2V$$

$$\Rightarrow \left(-\frac{R_1}{R_2}\right) \cdot V_L + V_S = 2$$

$$\Rightarrow -\frac{R_1}{R_2} \cdot (-7) + V_S = 2$$

$$\Rightarrow V_S = 2 - \frac{7R_1}{R_2}$$

$$\Rightarrow V_S = \frac{2R_2 - 7R_1}{R_2} \text{ ----- (i)}$$

again,

$$V_{TL} = -1.5$$

$$\Rightarrow \left(-\frac{R_1}{R_2}\right) \cdot V_H + V_S = -1.5$$

$$\Rightarrow -\frac{R_1}{R_2} \times 8 + V_S = -1.5$$

$$\Rightarrow V_S = -1.5 + \frac{8R_1}{R_2}$$

$$\Rightarrow V_S = \frac{8R_1 - 1.5R_2}{R_2} \text{ ----- (ii)}$$

from (i) and (ii),

$$\frac{2R_2 - 7R_1}{R_2} = \frac{8R_1 - 1.5R_2}{R_2}$$

$$\Rightarrow 2R_2 - 7R_1 = 8R_1 - 1.5R_2$$

$$\Rightarrow 15R_1 = 3.5R_2$$

$$\Rightarrow \frac{R_1}{R_2} = \frac{7}{30}$$

$$\therefore R_1 = 7\text{ k}\Omega \text{ and } R_2 = 30\text{ k}\Omega$$

Now, for shift voltage,

$$\begin{aligned} V_s &= \frac{V_{TH} + V_{TL}}{2} \\ &= \frac{2 + (1.5)}{2} \\ &= 0.25\text{ V} \end{aligned}$$

Now, for reference voltage,

$$V_{TH} = \left(-\frac{R_1}{R_2}\right) \cdot V_L + V_s$$

$$\Rightarrow 2 = -\frac{7}{30} \cdot (-7) + V_s$$


$$\Rightarrow 2 = \frac{49}{30} + \left(\frac{R_1}{R_2} + 1\right) \cdot V_{ref}$$

$$\Rightarrow 2 - \frac{49}{30} = \left(\frac{7}{30} + 1\right) \cdot V_{ref}$$

$$\Rightarrow V_{ref} = \frac{11}{30} \times \frac{30}{37}$$


$$\Rightarrow V_{ref} = 0.297\text{ V}$$

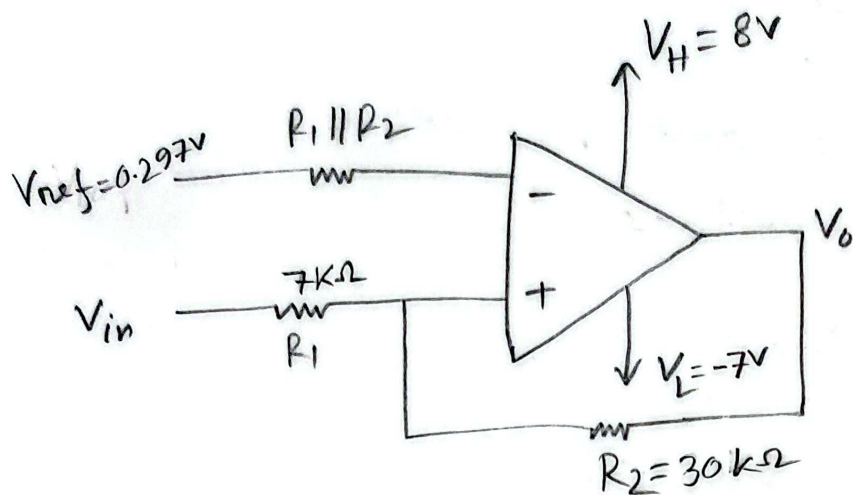Since this is a non-inverting schmitt trigger, the full circuit is drawn below:



(c)

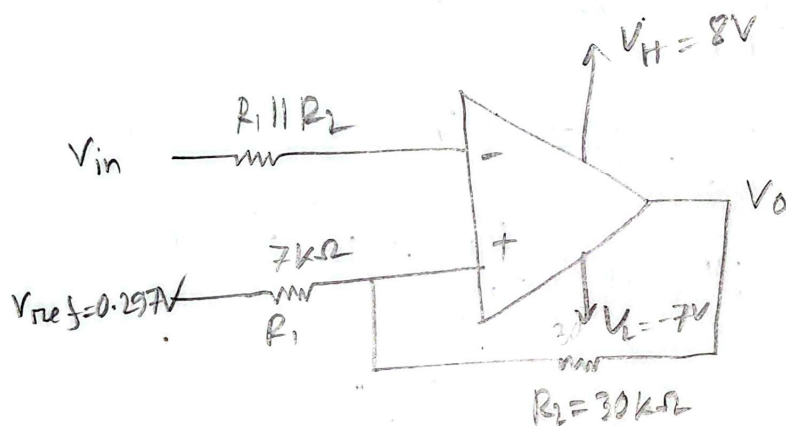If the connections of input voltage and reference voltages are swapped,



Now, this is a inverting schmitt trigger with reference,

$$R_1 = 7k\Omega$$

$$R_2 = 30k\Omega$$

$$V_{TH} = \left(\frac{R_1}{R_1 + R_2} \right) \cdot V_H + \left(\frac{R_2}{R_1 + R_2} \right) \cdot V_{ref}$$

$$= \left(\frac{7}{30 + 7} \right) \cdot 8 + \left(\frac{30}{30 + 7} \right) \cdot 0.297$$

$$\Rightarrow V_{TH} = 1.754 \text{ V}$$

$$\begin{aligned} \text{and, } V_{TL} &= \left(\frac{R_1}{R_1 + R_2} \right) \cdot V_L + \left(\frac{R_2}{R_1 + R_2} \right) \cdot V_{ref} \\ &= \left(\frac{7}{30 + 7} \right) \cdot (-7) + \left(\frac{30}{30 + 7} \right) \cdot 0.297 \\ &= -1.084 \text{ V} \end{aligned}$$

$$\begin{aligned} \text{Shift voltage, } V_S &= \left(\frac{R_2}{R_1 + R_2} \right) \cdot V_{ref} \\ &= \left(\frac{30}{30 + 7} \right) \cdot 0.297 \\ &= 0.241 \text{ V} \end{aligned}$$

$$\begin{aligned} \text{Hysteresis width} &= V_{TH} - V_{TL} \\ &= 1.754 - (-1.084) \\ &= 2.838 \text{ V} \end{aligned}$$

$$\text{So, } V_{TH} = 1.754 \text{ V, } V_{TL} = -1.084 \text{ V, } V_S = 0.241 \text{ V}$$

and $V_H = 2.838 \text{ V}$ and the modified circuit is inverting schmitt trigger with reference voltage.

(Ans.)