

Total Marks: 30

TSE, Spring 26.

- Total no of questions are **four (4)**. Answer **them all**.
- Figure in bracket [ ] next to each question indicates marks for that question.

■ **Question 1** [CO3] [20 marks]

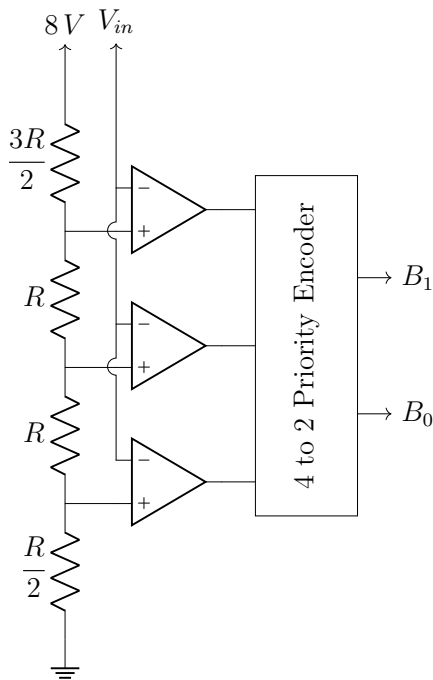


Figure 1: 2-bit Flash ADC

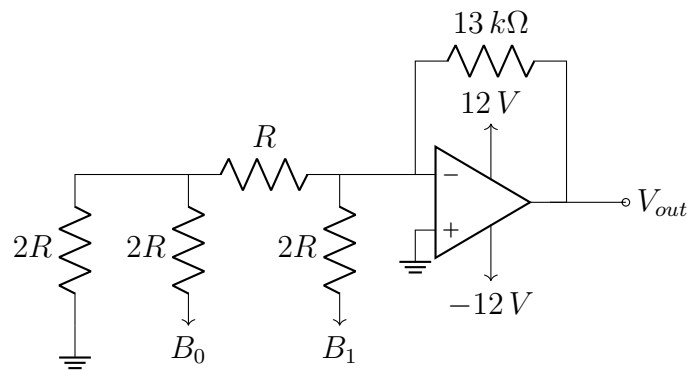


Figure 2: 2-bit R-2R Ladder DAC

$$V_{out} = -\frac{R_f}{2R} \left( V_{B_1} + \frac{V_{B_0}}{2} \right)$$

For both the circuits in the above figures, voltage of  $B_1$  &  $B_0$  is  $5V$  when logic is **HIGH**, and  $0V$ , when logic is **LOW**. The output of the ADC is passed to the DAC as input.

- (a) Make a table listing the **quantization intervals** of the ADC shown in figure 1, [4]  
along with the respective **digital output**.
- (b) If the maximum digital input to the DAC, produces a  $V_{out}$  of  $-6.5V$ , find the [4]  
value of the resistor 'R' in figure 2. Then calculate the **step size** of the DAC,  
and list all the output voltages for the **remaining inputs**.
- (c) Using your results from (a) & (b), find the digital output of the ADC for  $V_{in} =$  [3]  
 $5.5V$  and use it to find the  $V_{out}$  of the DAC.

Now consider a 2-bit **Dual Slope ADC** with a similar reference voltage as in figure 1, was used instead of the Flash ADC. It has a clock frequency of **2 MHz**.

- (d) Find the input voltage  $V_{in}$  for which the conversion time was found to be **2.7  $\mu s$** . [4]  
Also find the **maximum conversion time** of the ADC.
- (e) If for the Dual Slope ADC  $V_{in} = 5.5 V$ , find its digital output ' $B_1 B_0$ '. Then [5]  
find  $V_{out}$  if this was passed to the DAC in figure 2. Find the **%error** between the values of  $V_{out}$  for '1(c)' & '1(e)'.

■ **Question 2** [CO3] [15 marks]

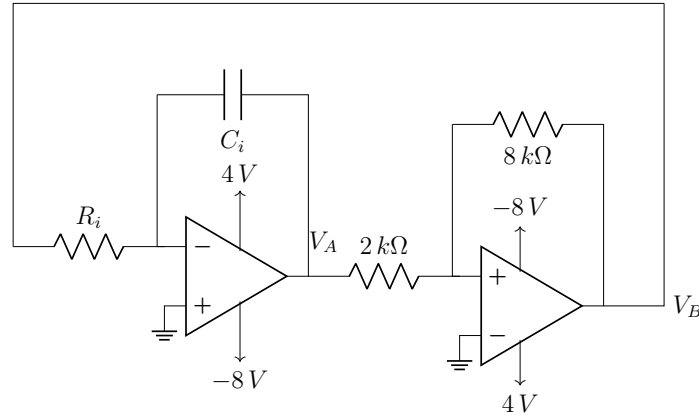


Figure 3: A Triangular Wave Generator

- (a) For the triangular wave generated by the circuit in figure 3, prove that  $f = \frac{8}{9R_i C_i}$ . [6]
- (b) You have to design a **square wave generator** that can generate a square wave [9]  
having duty cycle similar to the square wave at  $V_B$ . Find  $V_H$ ,  $V_L$  and draw the circuit given that,  $R_1 = 10 k\Omega$ ,  $R_2 = 20 k\Omega$ ,  $R_x = 10 k\Omega$ ,  $C_x = 50 nF$  and  $f = 1 kHz$ . Here,  $\tau = R_x C_x$  and  $R_2$  is the feedback resistance. [Hint: You may need to assume one of the bias voltages]

■ **Question 3** [CO3] [15 marks]

The input to & output from a certain Schmitt Trigger is shown in figure 4.

- (a) From figure 4, find the **bias voltages** & the **threshold voltages** of the Schmitt [5]  
Trigger. Then draw its **VTC** (Voltage Transfer Characteristics) on the plot given in figure 5.
- (b) Find the **shift voltage**. Design the Schmitt Trigger by specifying the values of [5]  
each component and drawing the full circuit.
- (c) If the connections of **input voltage** & **reference voltage** in the circuit of 'b' [5]  
are swapped, find the new **thresholds**, **shift voltage** & the **hysteresis width**.  
What type of Schmitt Trigger is this modified circuit?

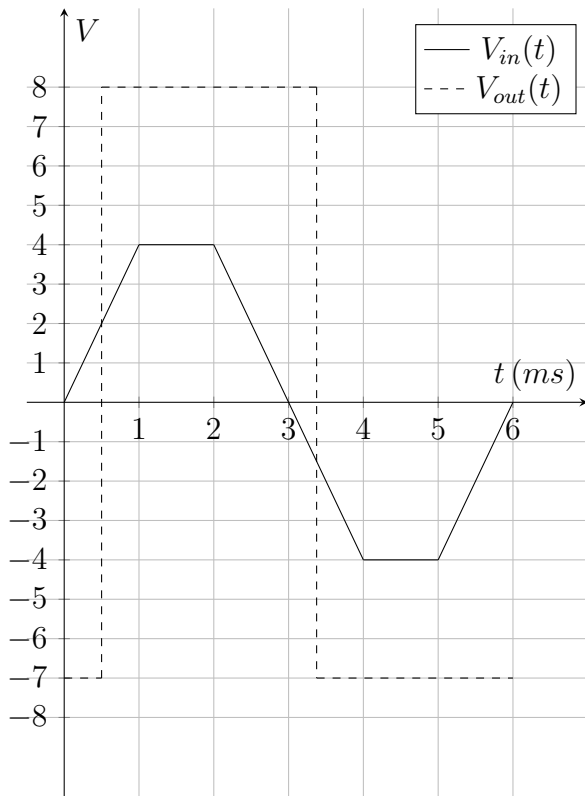


Figure 4:  $V_{in}(t)$  &  $V_{out}(t)$

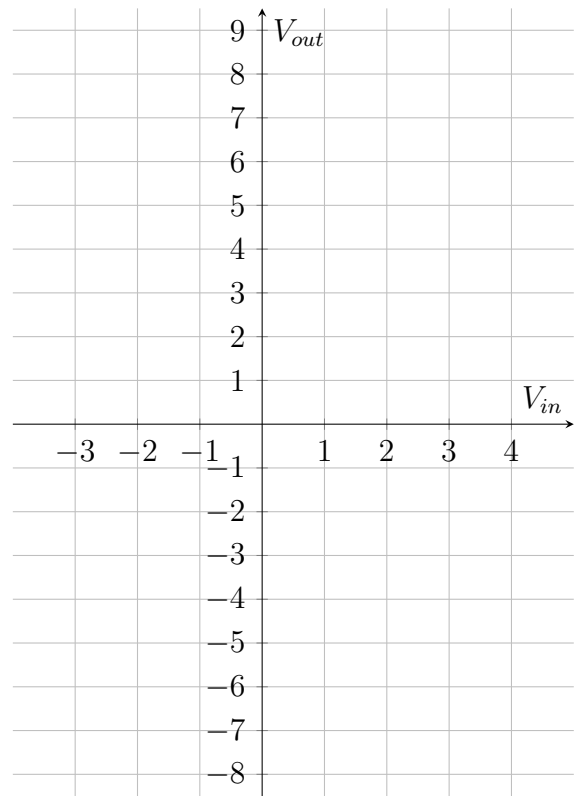


Figure 5: VTC of the Schmitt Trigger