



Inspiring Excellence

BRAC UNIVERSITY

CSE 350: Digital Electronics and Pulse techniques

Exp-01: Flash Analog to Digital converter (ADC)

Name: Sultan Mohammad Farid	Section: 6A
ID: 23201107	Group: 2

Objectives

1. To analyze a 2-bit flash analog to digital converter.

Equipment and component list

Equipment

1. Digital Multimeter
2. Trainer board

Component

- Single Supply Quad Operational Amplifier - LM324 - x1 piece
- 8-to-3 Line Priority Encoder - IC74148 - x1 piece
- Resistors -
 - 10 K Ω - x4 pieces


Task-01: Flash ADC

THEORY

Flash ADC is the fastest analog-to-digital converter. You can see the circuit diagram of a 2-bit flash ADC in figure 1. All the op-amps operate as comparators in this circuit. The analog input (V_A) is applied to the 'inverting' input of the three op-amps.

There is a resistive ladder-network with a reference voltage $V_{REF} = 5\text{ V}$ at the top of the network. We will obtain some fixed voltages at each node of this network. These nodes are denoted as V_1 , V_2 and

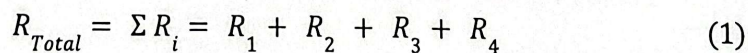Now, let us calculate the node voltages V_i 's of the ladder network. For this, keep in mind that the current towards the op-amp's input terminals are negligible. First, the total resistance of the ladder network is



So, using Ohm's law, the current through the ladder network will be (same current flows through all the R_i 's)

It is now trivial to calculate all the node voltages. The equations for all the node voltages are given below for your convenience.

2

$$V_2 = I(R_3 + R_4) = \frac{V_{REF}}{2} \quad (4)$$

$$V_3 = I(R_2 + R_3 + R_4) = \frac{3V_{REF}}{4} \quad (5)$$

Now, closely analyze the operation of all the op-amps. OA1 has input voltage V_A at its '-' input (inverting input) and V_1 at '+' input (non-inverting input). If $V_A < V_1$, OA1 will give a HIGH output. Similarly, OA2 will give HIGH output if $V_A < V_2$ and OA3 if $V_A < V_3$.


Next, we send the outputs of all the op-amps to a priority encoder. We will then get our desired 2-bit digital signal at the output of this encoder which corresponds to the original analog input signal.

For this flash ADC design, we will need $2^n - 1$ op-amps for implementing an n-bit ADC. This presents a huge disadvantage in terms of practical implementation in the laboratory.


Procedure:

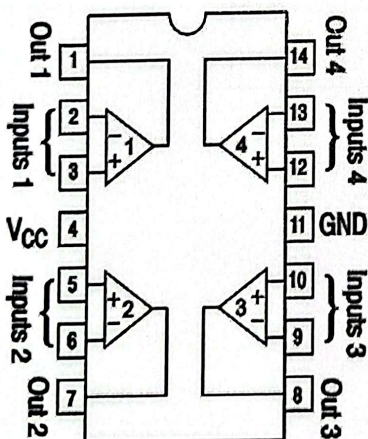1. Construct the circuit as shown in figure 1. Consider, $R = 10 \text{ K}\Omega$.
2. We will not use any external LEDs. Connect the outputs of the encoder to the LEDs of the Trainer Board.
3. Vary the analog input voltage, V_{IN} or V_A from 0V to 5V.
4. Observe when the two LEDs switch ON or OFF and measure the input voltage which causes the transitions. Fill up data table 1 using this data.

Note: The encoder is "Active LOW". This means that whenever the output (A_0, A_1) is supposed to be "Logical 1", they are at a LOW voltage. Hence, the corresponding LED will turn OFF!



LM324 IC (Quad Op-Amp) pin diagram

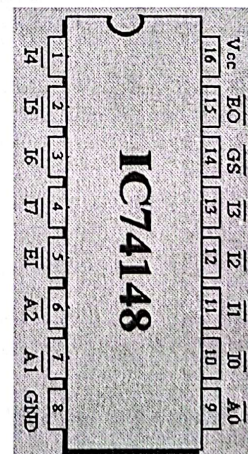

74148 IC (Encoder) pin diagram

Data Tables

Table 1: Flash AD Converter.

Input Voltage $V_{IN} = V_A$	State of LED ₁	State of LED ₀	Digital Binary Output
0 - 1.33	ON	ON	00
1.33 - 2.66	ON	OFF	01
2.66 - 4.00	OFF	ON	10
4.00 - 5.00	OFF	OFF	11

Table 1: Data Table for Flash AD Converter

Lab Task 1

Use your "group number" as input voltage V_A and observe the binary digital output using LEDs. Then, measure the output voltages using a multimeter. If the group number is greater than 5, divide it by 3 and use the resultant value as input. Explain the reason for obtaining the binary output using the voltages you have measured. (Note: disconnect the LEDs when measuring the output voltages)

Input Voltage $V_{IN} = V_A$	Digital Binary Output
2.06V	01 $V_1 = 2.43V$ $V_0 = 4.3mV$

Input 2.06 V falls in the (1.33 - 2.66) region, that's why we are getting 01 as the Digital Binary output.

Lab Task 2

Adjust the input voltage such that we get Binary output 00 and 01. For each case, measure the output voltages of the encoder. Explain why the LEDs turn on or off. (Note: disconnect the LEDs when measuring the output voltages)

When the input range is between 0 to 1.33 V, both of the LEDs are turned ON. When we increased the value to 2V, A_0 LED turns off.

Output bits. A_1A_0	V_{A1}	V_{A0}
00	1.72V	1.68V
01	1.66V	8.7mV

Lab Task 3

Measure the voltages of points V_3 , V_2 and V_1 . Do the values match with the theory?

The voltages V_3 , V_2 , V_1 somewhat closed to the theory that are 3.75V, 2.5, 1.25V respectively.

V_1 (V)	V_2 (V)	V_3 (V)
1.33V	2.7V	4.02V

Amir Tabassum

Signature

Report

1. Write down an advantage and a disadvantage of a Flash AD converter.

Ans.

Flash AD converter needs a lot of components but it works very fast.

2. If we wanted to build a 3-bit Flash AD converter, how many resistors and comparators (op-amps) would we need?

Ans.

for 3 bit Flash AD converter, $n=3$

$$\therefore \text{resistors needed} = 2^3 = 8$$

$$\therefore \text{comparators needed} = 2^3 - 1 = 7$$

3. What is the advantage of using an ACTIVE LOW encoder instead of an ACTIVE HIGH one?

If we use Active High Encoder, we will need 1 extra comparator. Instead, if we use active low ones, in the I_0 of the encoder, the voltage will remain V_L though not connected to a comparator.

4. Using your measured values of V_1 , V_2 and V_3 in Lab Task 3, calculate the current through the resistors.

The experimental values, $V_1 = 1.33V$ $V_2 = 2.7V$ & $V_3 = 4.02V$

Resistance used $= R_1 = R_2 = R_3 = R_4 = R = 10k\Omega$

$$\text{Now, current through } R_1, I_1 = \frac{\Delta V}{R_1} = \frac{V_{ref} - V_3}{10k\Omega} = \frac{5 - 4.02}{10 \times 10^3} = 9.8 \times 10^{-5} A$$

$$" " R_2, I_2 = \frac{\Delta V}{R_2} = \frac{V_3 - V_2}{10k\Omega} = \frac{4.02 - 2.7}{10 \times 10^3} = 1.32 \times 10^{-4} A$$

$$" " R_3, I_3 = \frac{\Delta V}{R_3} = \frac{V_2 - V_1}{10k\Omega} = \frac{2.7 - 1.33}{10 \times 10^3} = 1.37 \times 10^{-4} A$$

$$" " R_4, I_4 = \frac{\Delta V}{R_4} = \frac{V_1 - 0}{10k\Omega} = \frac{1.33 - 0}{10 \times 10^3} = 1.33 \times 10^{-4} A$$

5. Write a discussion and include the following: your overall experience, accuracy of the measured data, difficulties experienced, and your thoughts on those.

Ans.

My overall experience was very good. It was really great to implement that we learned. ~~That~~ The analog to digital data conversion is one of the first step towards digitalization of the world. Moreover, there was also the implementation of thing we learned previously in our previous courses CSE250 & CSE251. The accuracy of the measured data was closed to the theoretical value. We faced difficulty while designing the circuit in breadboard because of one ~~was~~ misplaced wire. Later, we noticed that and it worked.