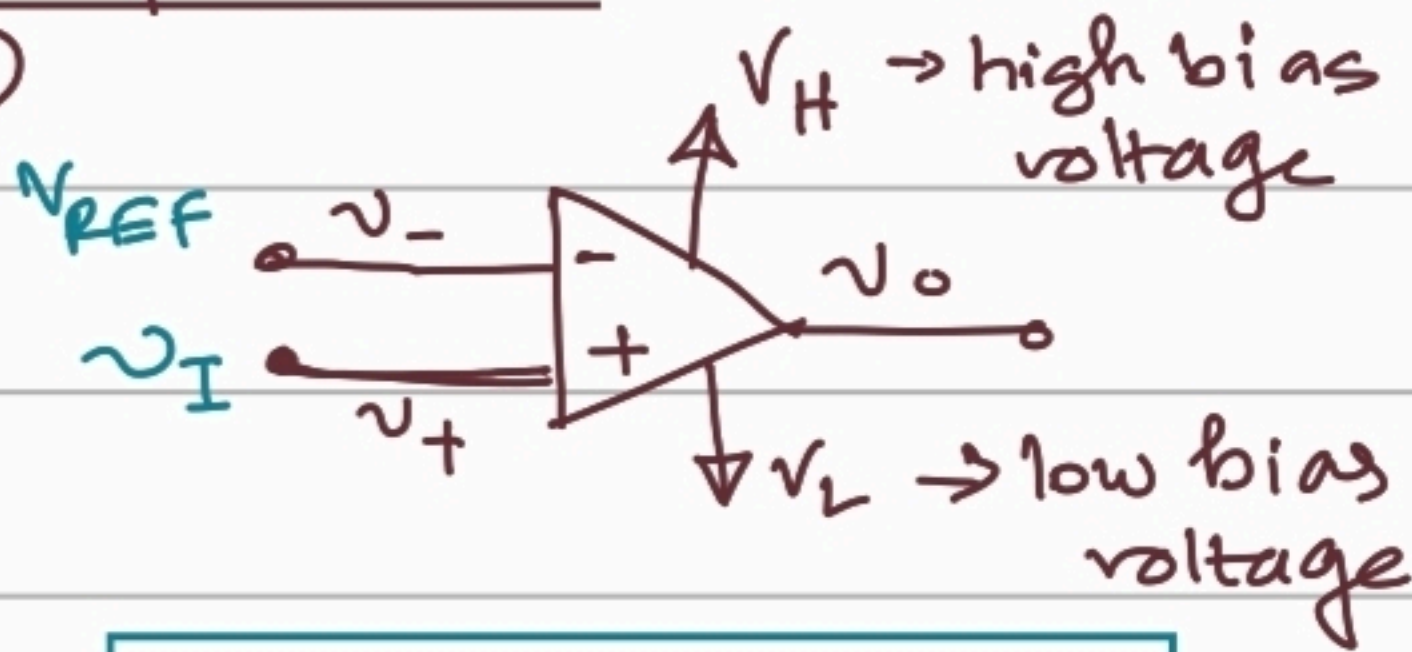


Lecture 18: Schmitt Trigger Circuit.

Otto H. Schmitt (1934) envisioned this circuit.

Comparators:


①




$$\begin{aligned} v_+ > v_- &\Rightarrow v_o = V_H \\ v_+ < v_- &\Rightarrow v_o = V_L \end{aligned}$$

$$\begin{aligned} v_+ = v_I > V_{REF} = v_- &\Rightarrow v_o = V_H \\ v_+ = v_I < V_{REF} = v_- &\Rightarrow v_o = V_L \end{aligned}$$

Transfer characteristics

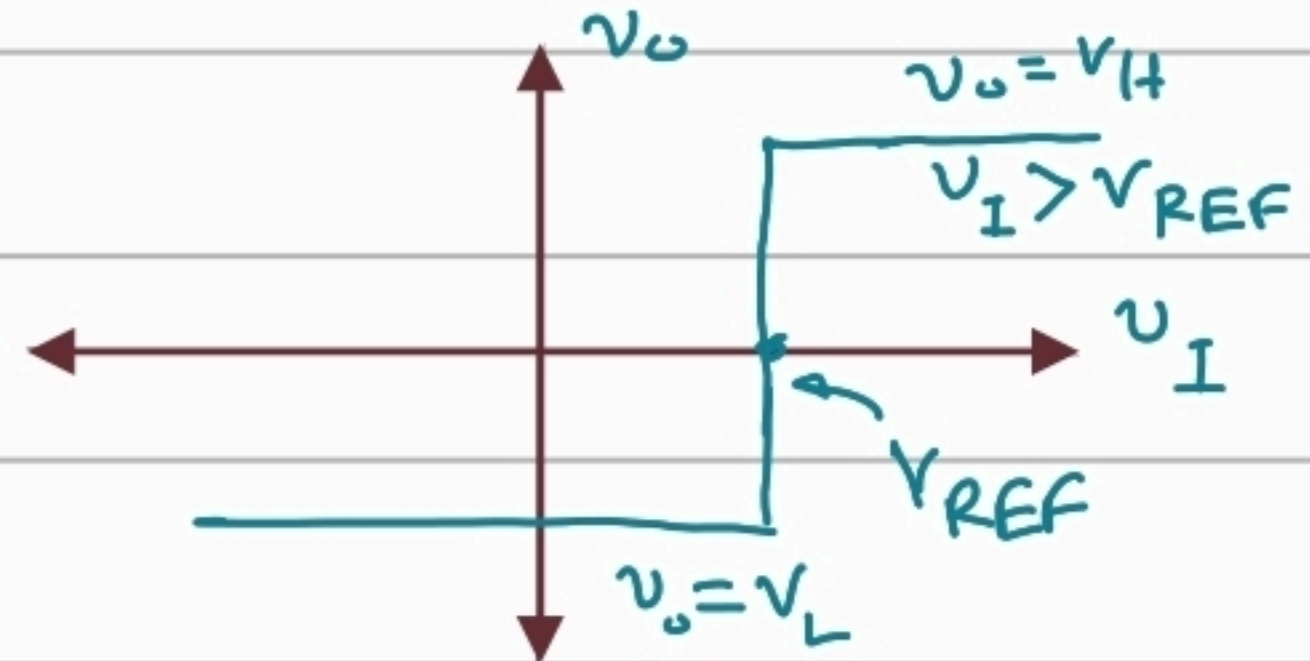


②

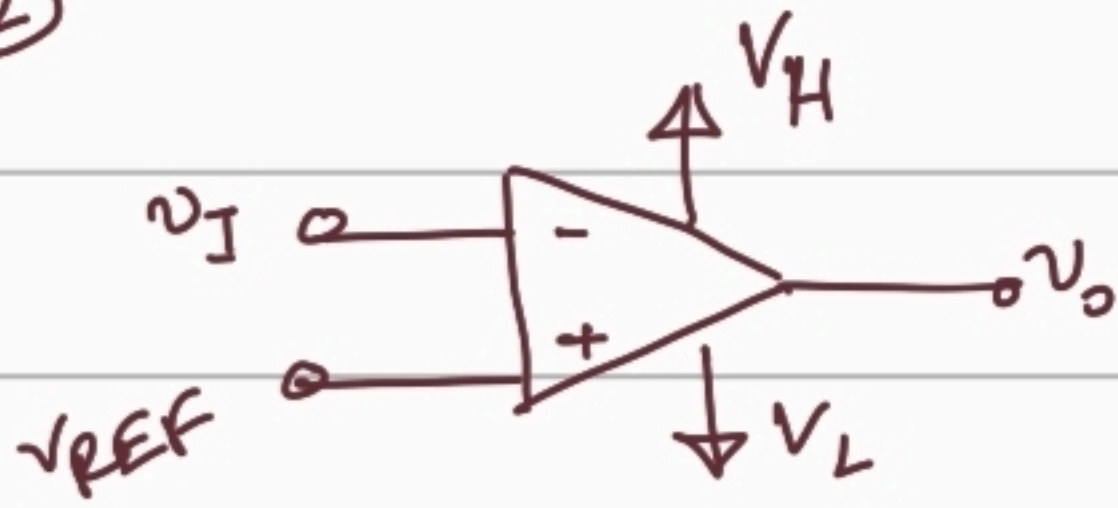


$$v_+ = V_{REF} > v_I = v_- \Rightarrow v_o = V_H$$

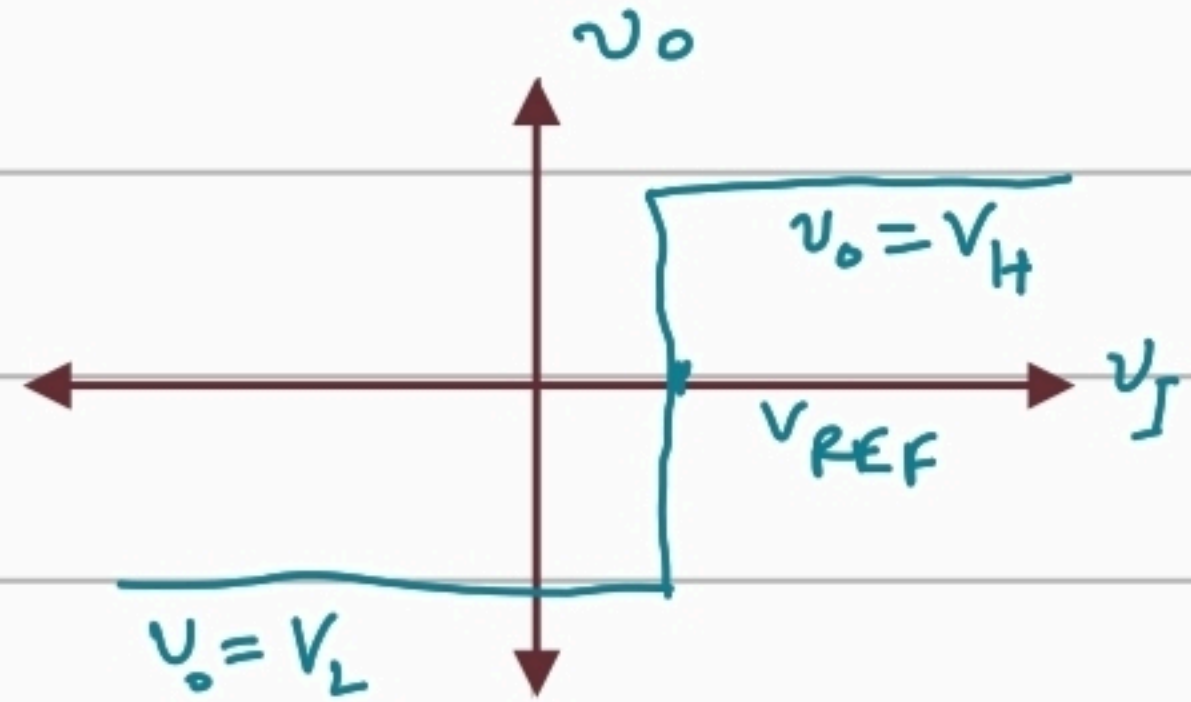
$$v_+ = V_{REF} < v_I = v_- \Rightarrow v_o = V_L$$



③

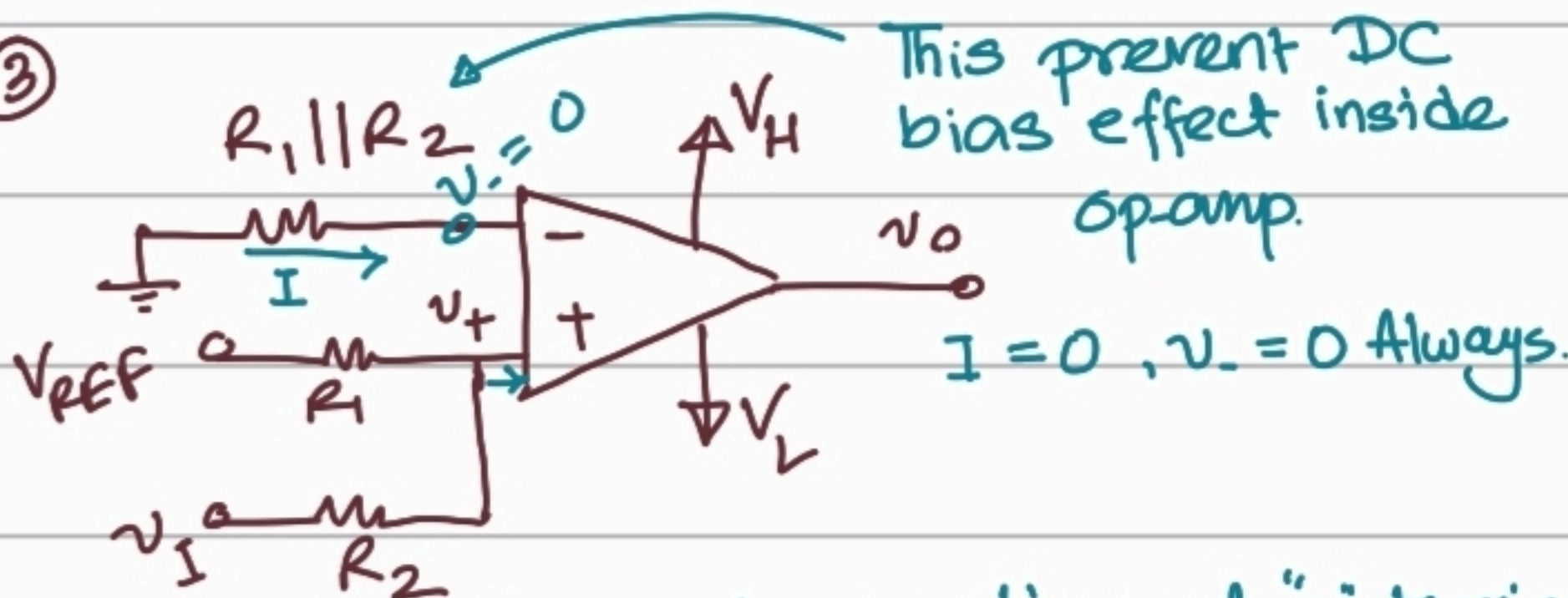

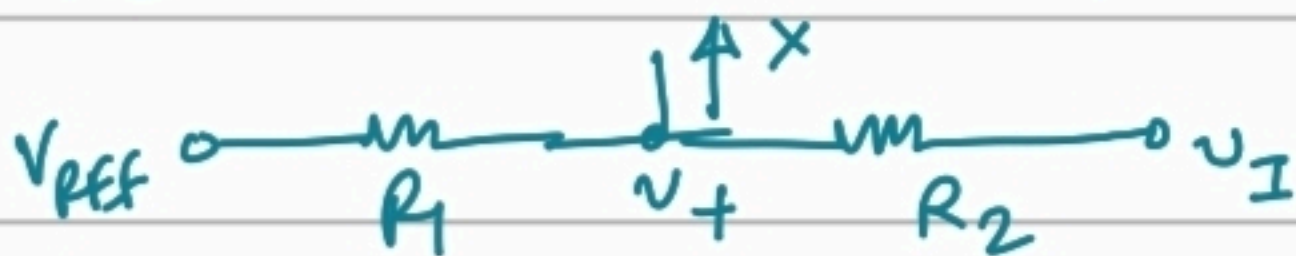
We can write node equation at '+' terminal



$$\frac{v_+ - V_{REF}}{R_1} + \frac{v_+ - v_I}{R_2} = 0$$

$$\Rightarrow v_+ = V_{REF} \left(\frac{R_2}{R_1 + R_2} \right) + v_I \left(\frac{R_1}{R_1 + R_2} \right)$$

$$v_- = 0$$

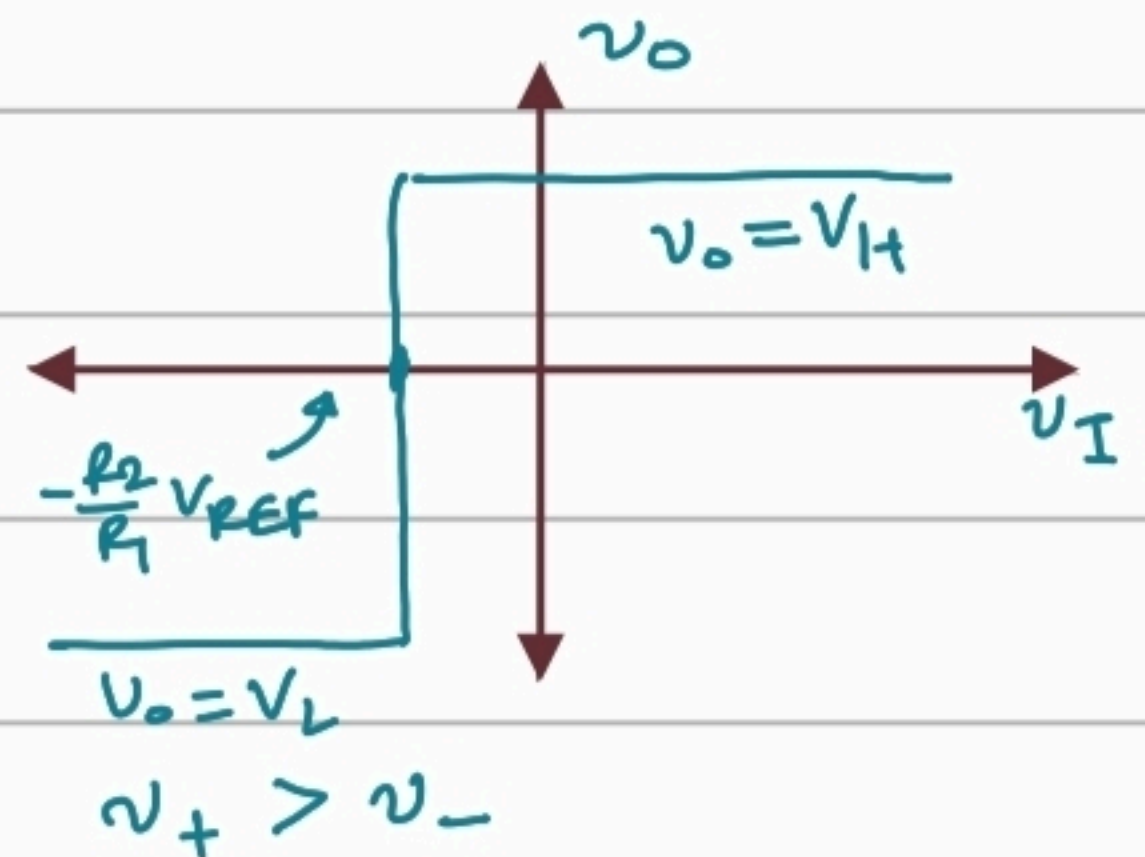


$$\Rightarrow \frac{v_I R_1}{R_1 + R_2} + V_{REF} \frac{R_2}{R_1 + R_2} > 0$$

$$\Rightarrow v_I > \left(-\frac{R_2}{R_1} \right) V_{REF}$$

$$\Rightarrow v_o = V_H$$


$$\text{or } v_I < \left(-\frac{R_2}{R_1} \right) V_{REF}$$

$$\Rightarrow v_o = V_L$$

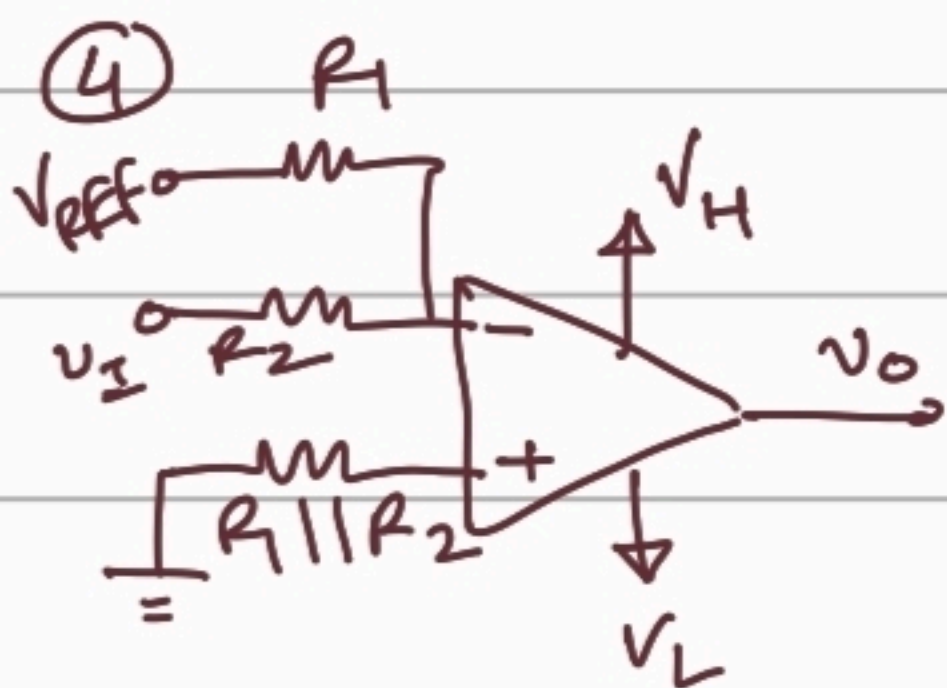

$$v_+ = 0$$

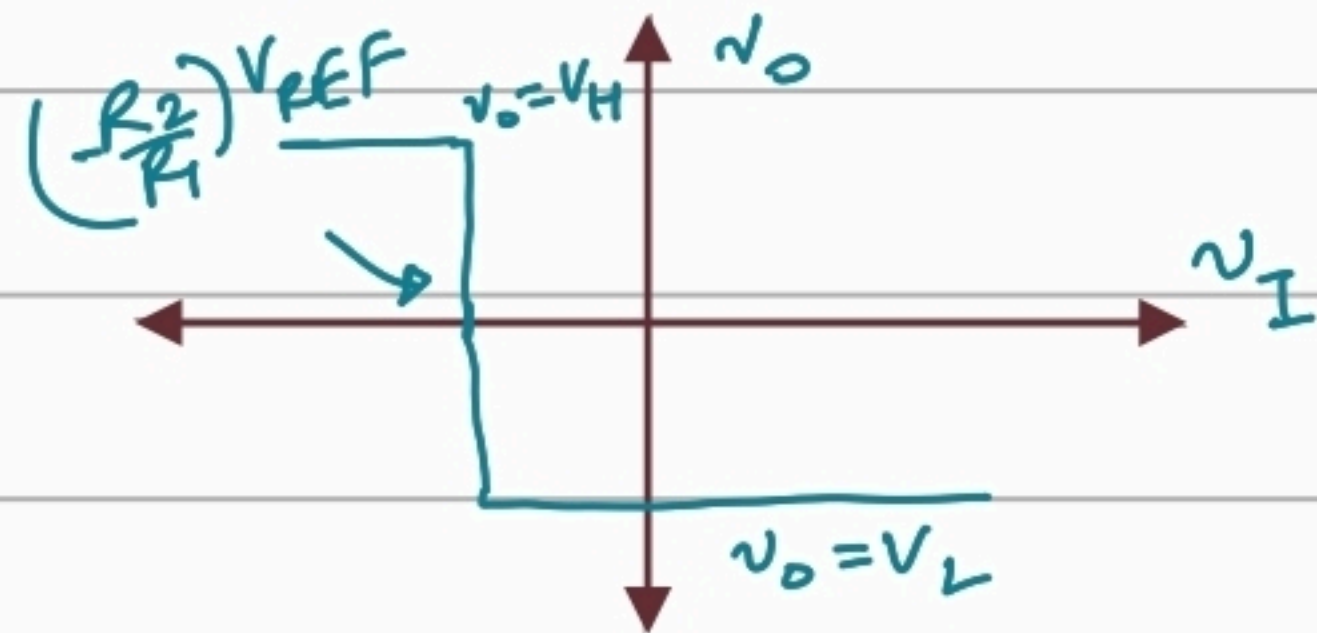and $v_- = v_I \frac{R_1}{R_1 + R_2} + V_{REF} \frac{R_2}{R_1 + R_2}$



$$v_+ > v_-$$


$$\Rightarrow v_I < \left(-\frac{R_2}{R_1}\right) V_{REF}$$

$$\Rightarrow v_O = V_H$$

otherwise, $v_O = V_L$

Schmitt Trigger

Inverting S.T.

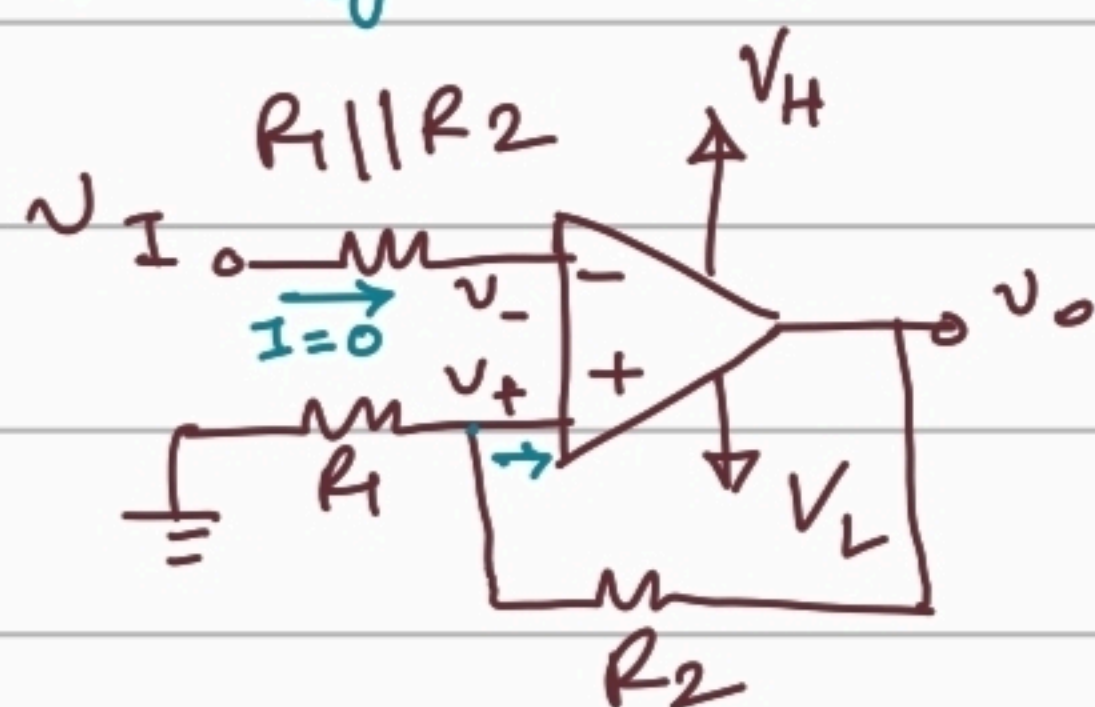

$$v_- = v_I$$

$$v_+ = v_O \frac{R_1}{R_1 + R_2}$$

[use node eqn at "+" terminal]


We can increase $v_I = v_-$ until it crosses the voltage of $v_+ = \frac{R_1 V_{REF}}{R_1 + R_2}$. After that output changes to V_L .

So $V_{REF} \cdot \frac{R_1}{R_1 + R_2}$ is denoted as higher threshold voltage. V_{TH}


Case 2: $|v_I| \gg 0$ but v_I is positive. we can expect that $v_- > v_+$ and $v_O = V_L \Rightarrow v_+ = V_L \frac{R_1}{R_1 + R_2}$.

When v_I decreases below the $v_+ = V_L \frac{R_1}{R_1 + R_2}$, v_O changes from V_L to V_H .

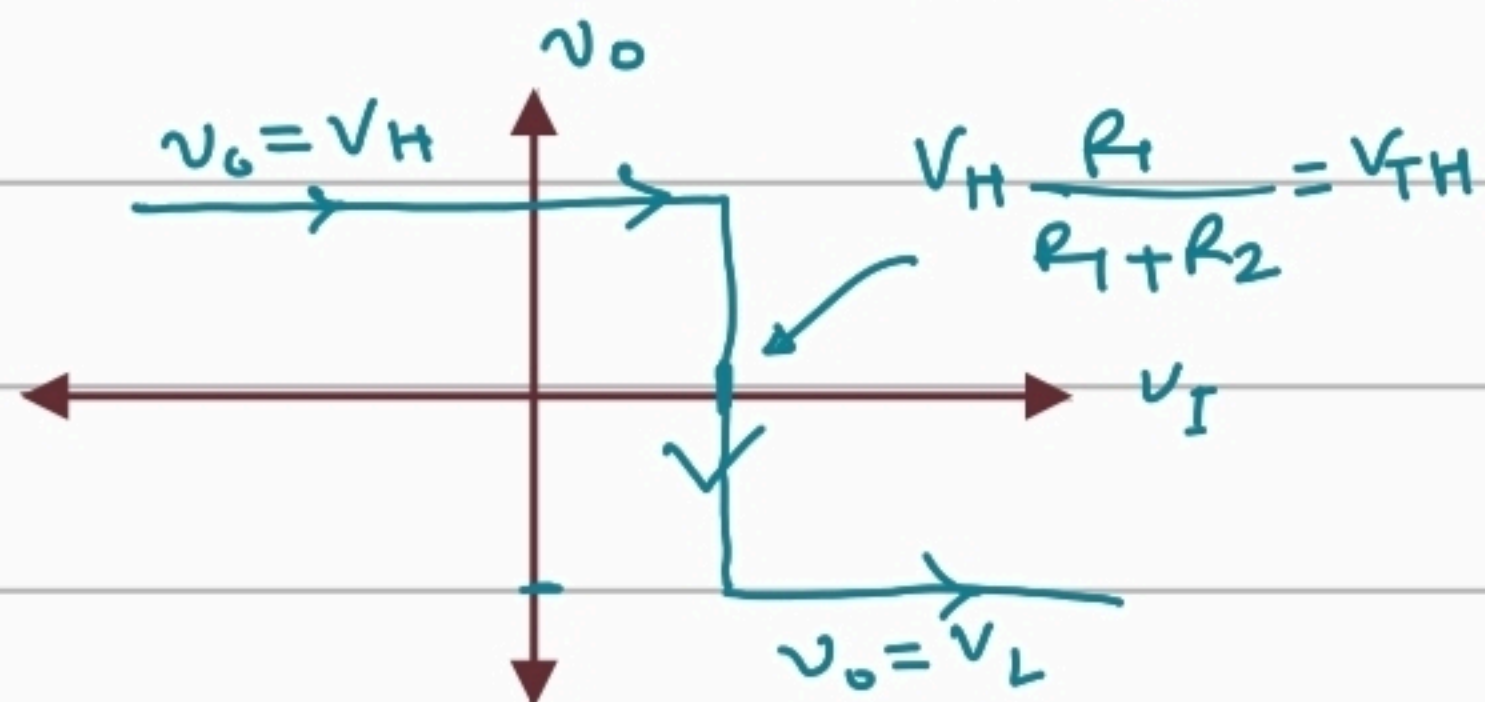Lower threshold voltage. $V_{TL} = V_L \frac{R_1}{R_1 + R_2}$



Combined transfer characteristics.

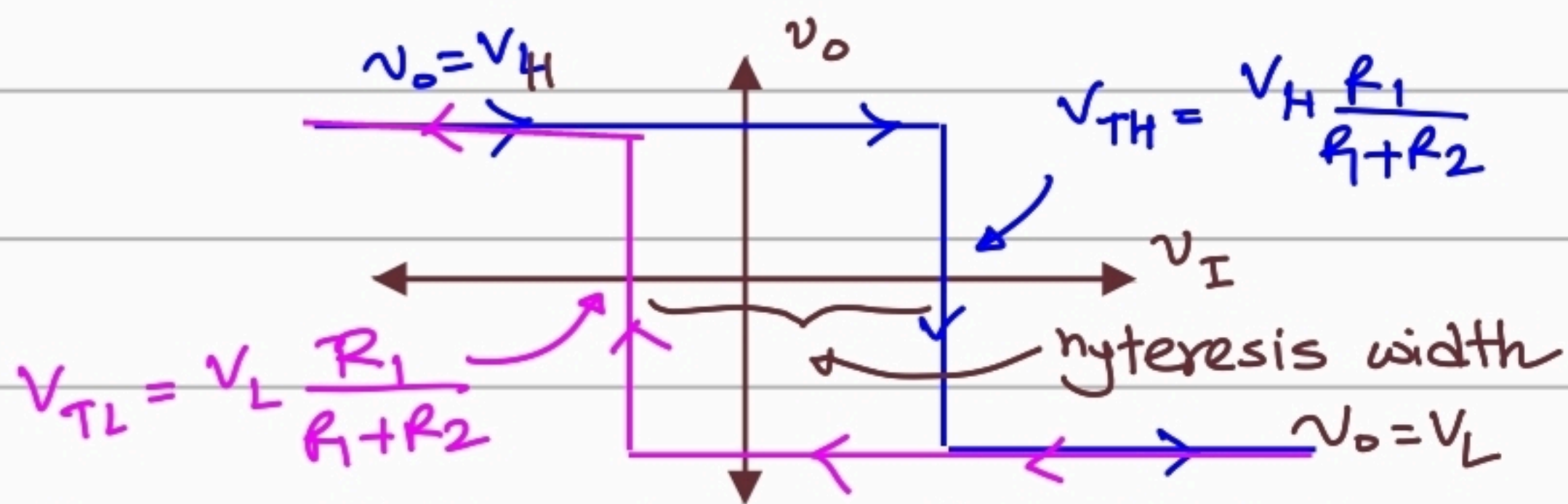

Bistable multivibrator = Schmitt trigger

It has two stable output states. $v_o = V_H / V_L$

Example 15.6 Neamann

Determine the hysteresis width of a particular Schmitt trigger.


$R_1 = 10k\Omega$, $R_2 = 90k\Omega$, $V_H = 10V$ and $V_L = -10V$.

Solⁿ:


Hysteresis width = $V_{TH} - V_{TL}$

$$\Rightarrow V_{TH} - V_{TL} = V_H \frac{R_1}{R_1 + R_2} - V_L \frac{R_1}{R_1 + R_2} = (V_H - V_L) \frac{R_1}{R_1 + R_2} = 20 \times \frac{10}{100} = 2V$$

Non-inverting Schmitt Trigger Circuit:

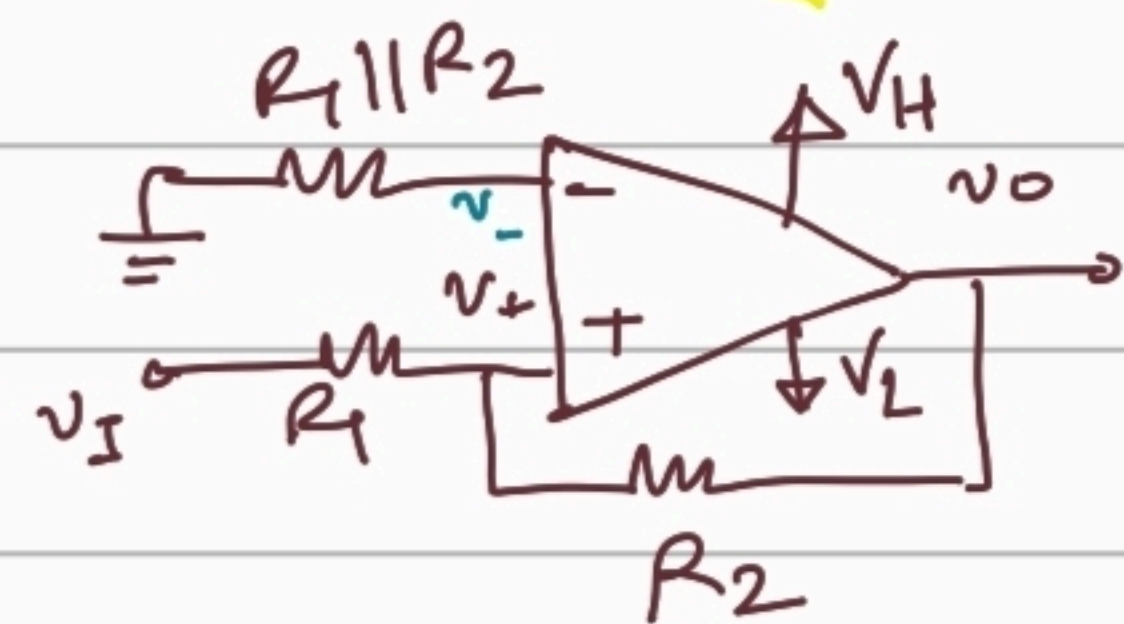

Consider the two cases just like before and use $|v_i| \gg 0$

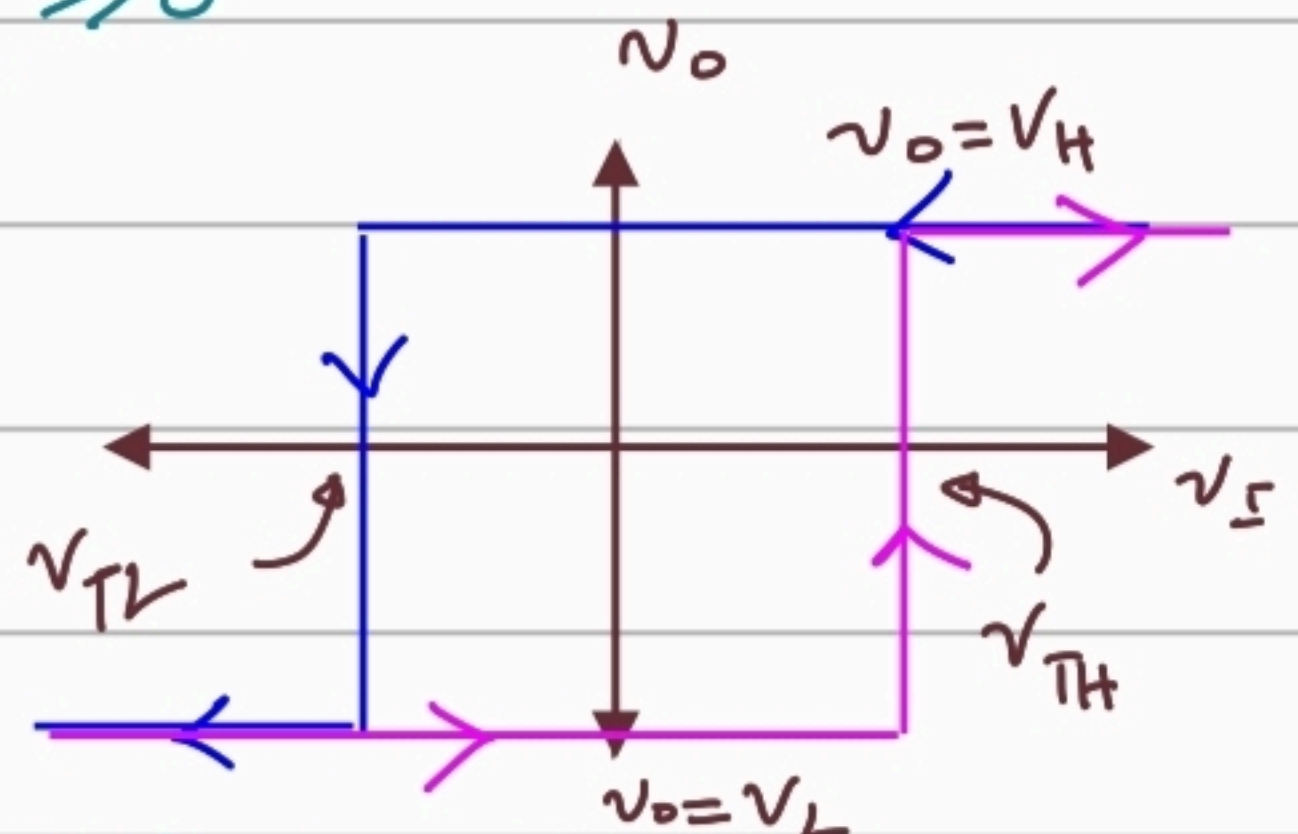

$$\begin{aligned} v_- &= 0 \\ v_+ &= v_o \frac{R_1}{R_1 + R_2} + v_i \frac{R_2}{R_1 + R_2} \end{aligned}$$

At transition point $v_+ = v_-$ and for V_{TH} we can say from transfer characteristics that $v_o = V_L$



$$0 = V_L \frac{R_1}{R_1 + R_2} + V_{TH} \frac{R_2}{R_1 + R_2} \Rightarrow \underline{V_{TH}} = \left(-\frac{R_1}{R_2} \right) \underline{V_L}$$

Similarly, we can get. $\underline{V_{TL}} = \left(-\frac{R_1}{R_2} \right) \underline{V_H}$

$v_i \uparrow \downarrow$, $v_o \uparrow \downarrow$ when $|v_i| \gg 0$

Schmitt Trigger with Applied Voltage:

Inverting S.T.

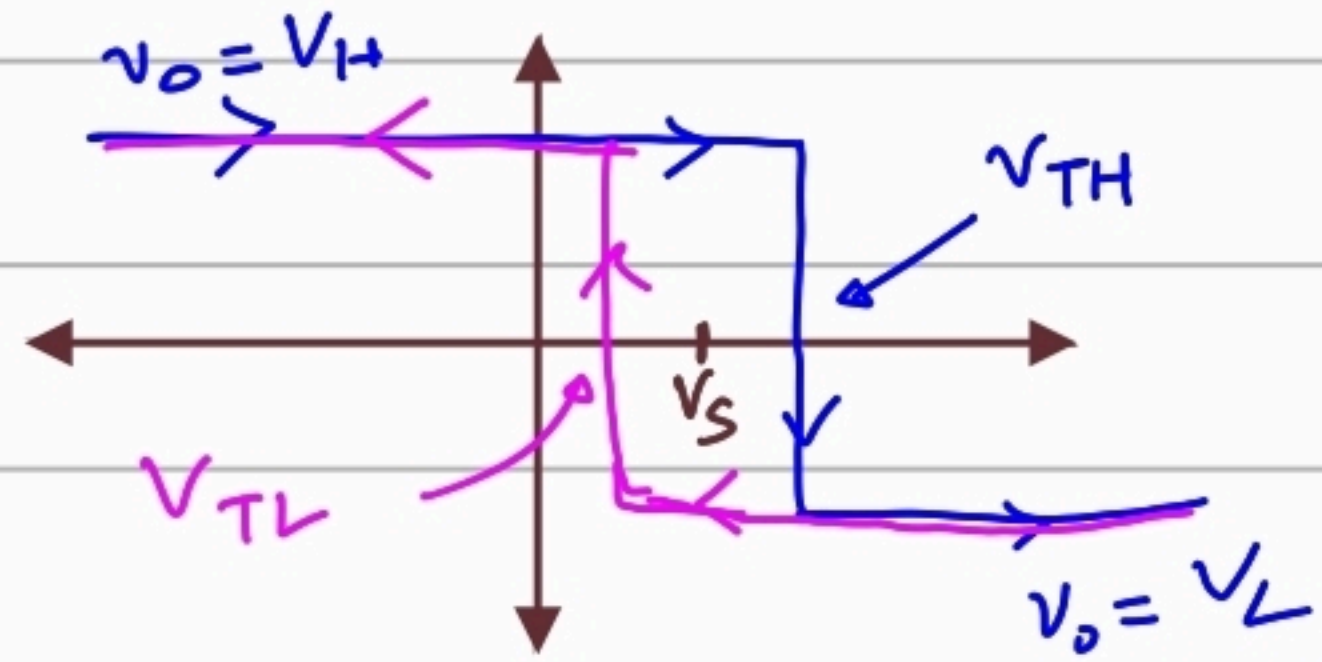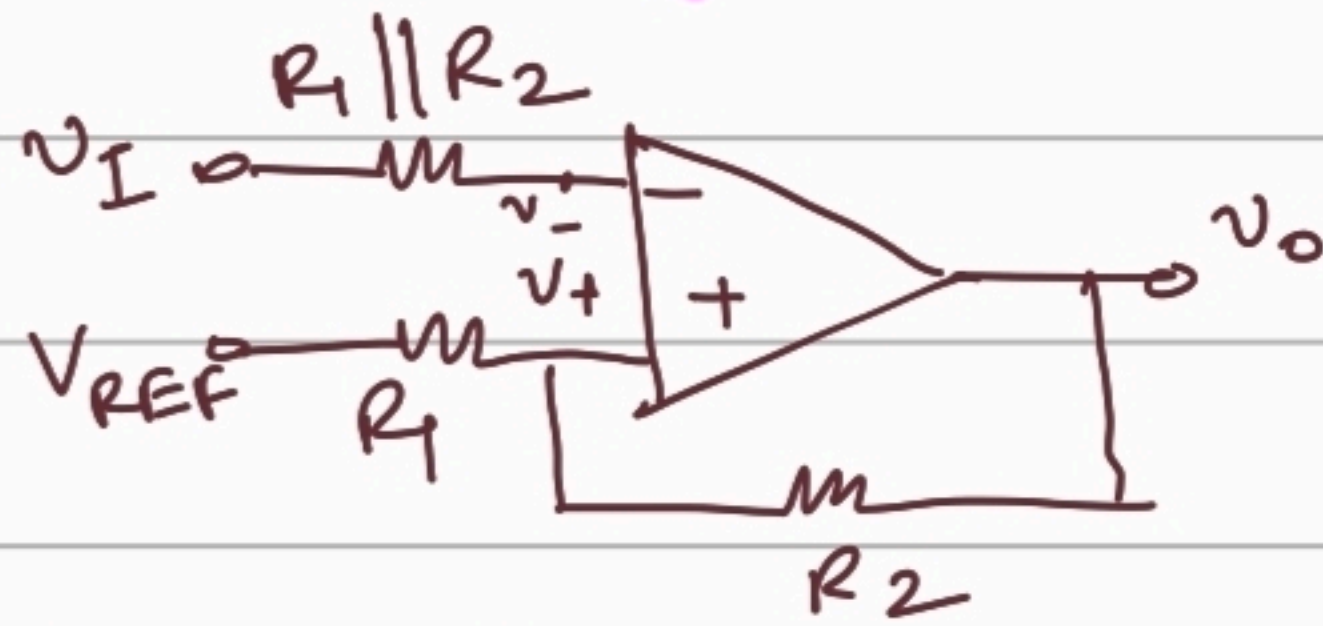

V_S = Shift voltage.

Now, $v_- = v_+ (v_O = V_H, v_I = V_{TH})$

$$\Rightarrow V_{TH} = V_{REF} \left(\frac{R_2}{R_1 + R_2} \right) + V_H \left(\frac{R_1}{R_1 + R_2} \right)$$



Similarly, $v_- = v_+ (v_O = V_L, v_I = V_{TL})$

$$\Rightarrow V_{TL} = V_{REF} \left(\frac{R_2}{R_1 + R_2} \right) + V_L \left(\frac{R_1}{R_1 + R_2} \right)$$

So shift/voltage switching

$$V_S = V_{REF} \frac{R_2}{R_1 + R_2}$$

NonInverting S.T.

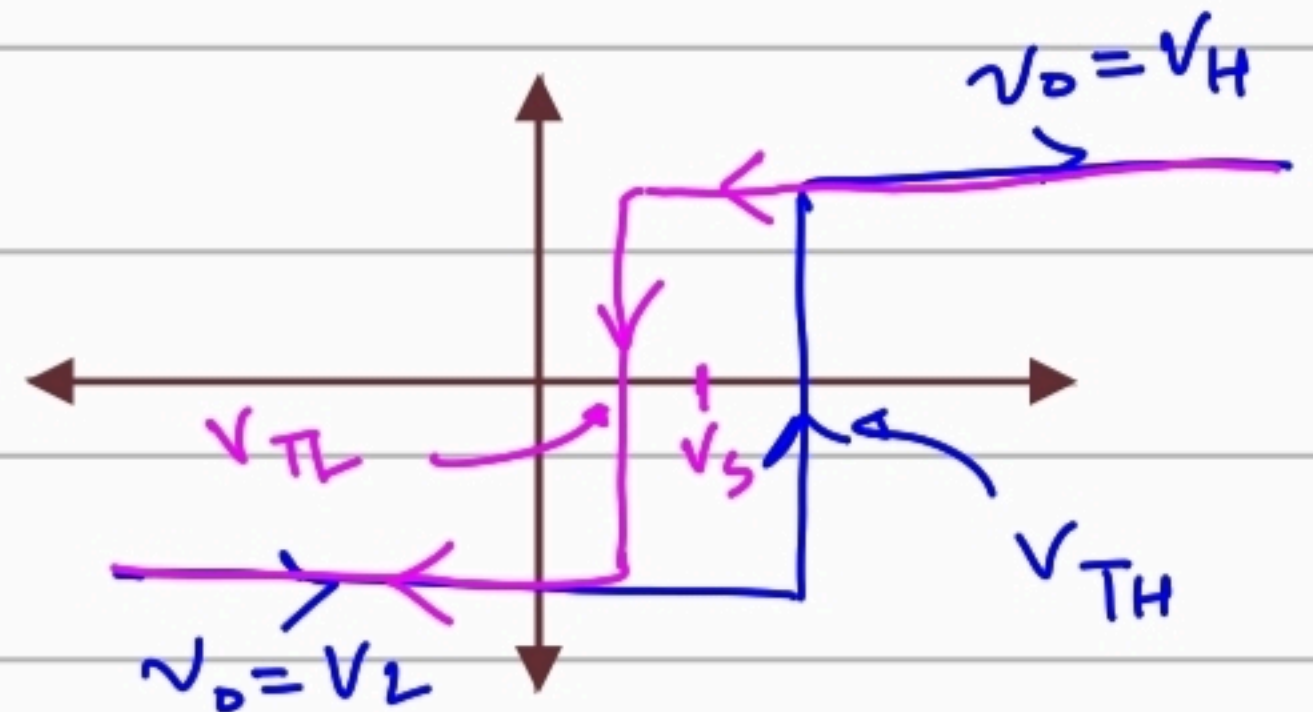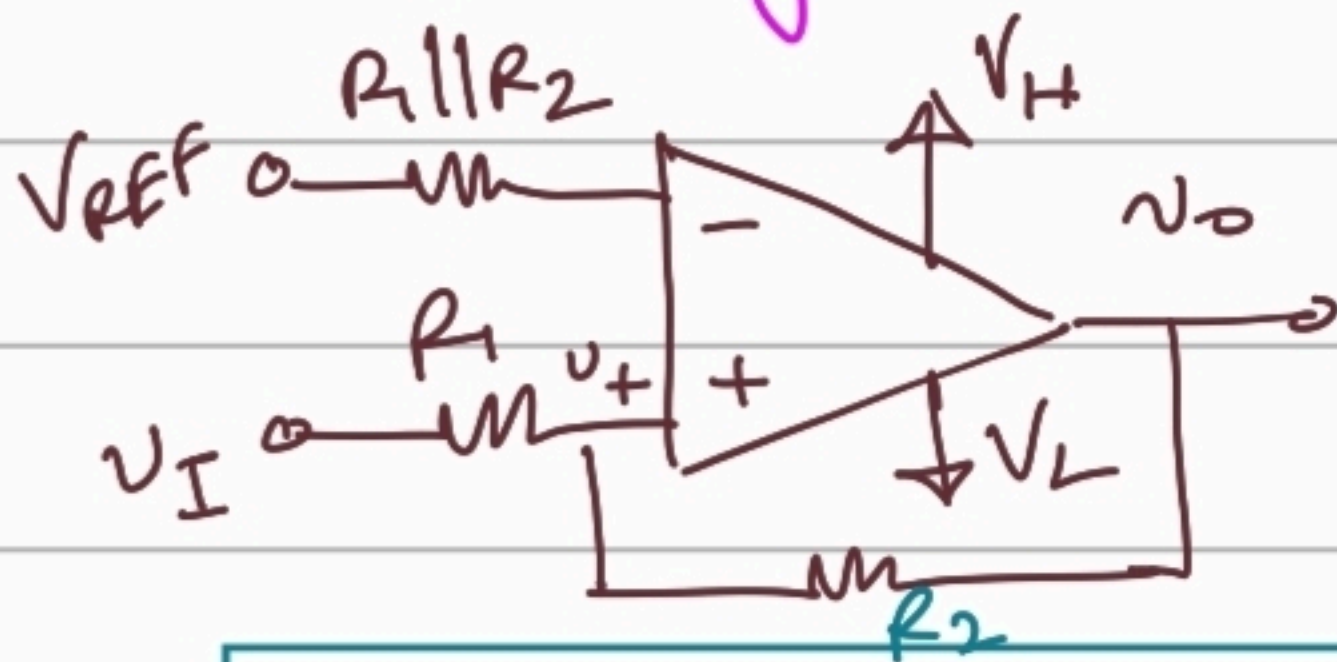

$$v_- = V_{REF}$$

$$v_+ = v_I \frac{R_2}{R_1 + R_2} + v_O \frac{R_1}{R_1 + R_2}$$

$$V_{TH} = \left(\frac{R_1 + R_2}{R_2} \right) V_{REF} + \left(-\frac{R_1}{R_2} \right) V_L$$

$$V_{TL} = \left(\frac{R_1 + R_2}{R_2} \right) V_{REF} + \left(-\frac{R_1}{R_2} \right) V_H$$


Shift/voltage switching $V_S = \left(\frac{R_1 + R_2}{R_2} \right) V_{REF}$

Application:

☐ Smoke Detector

☐ Street light Control


Noise source: Chattering effect

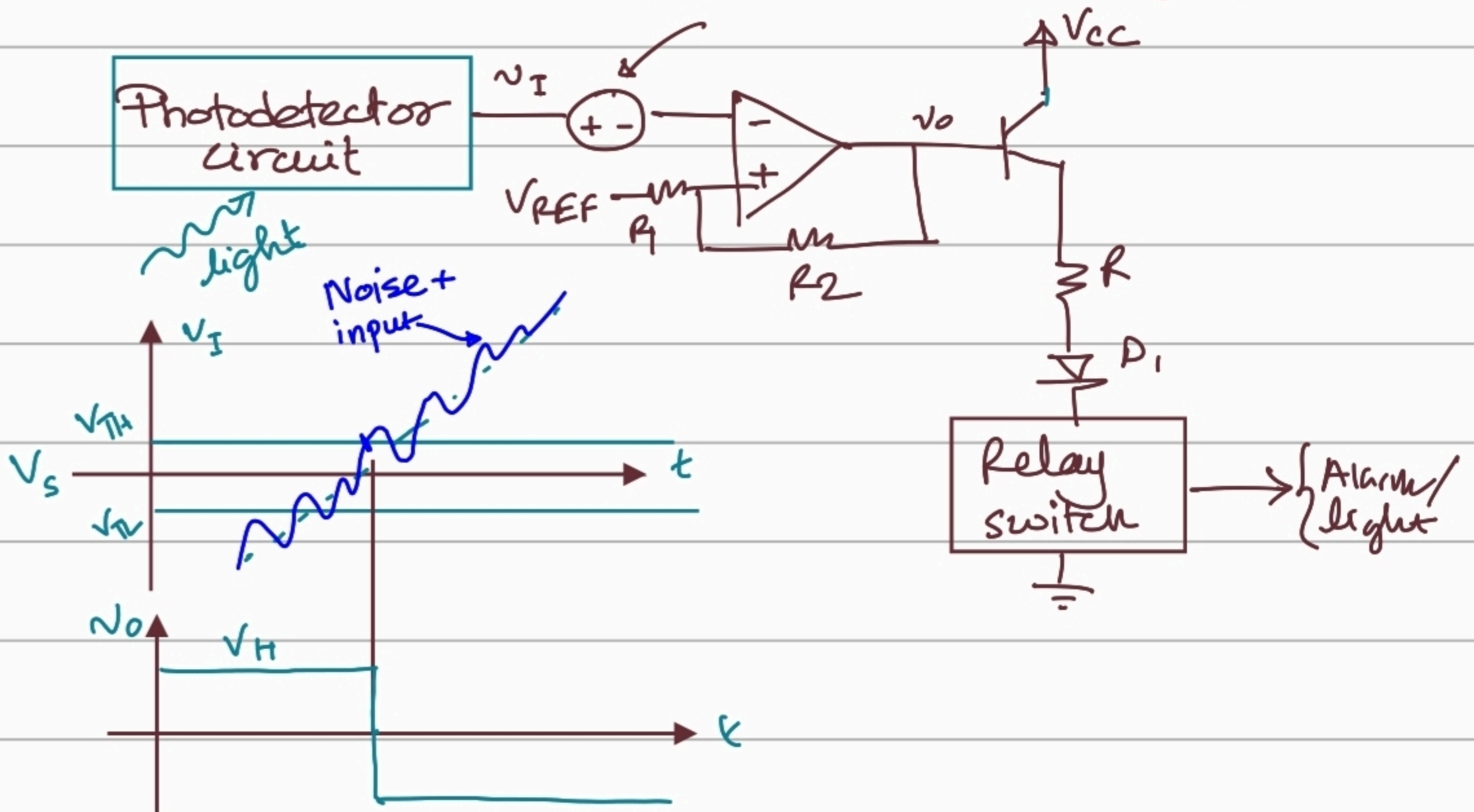

Design problem 15.7 (Practice | Final Exam)

Lecture 19: Signal Generators.

Basic R-C circuit:

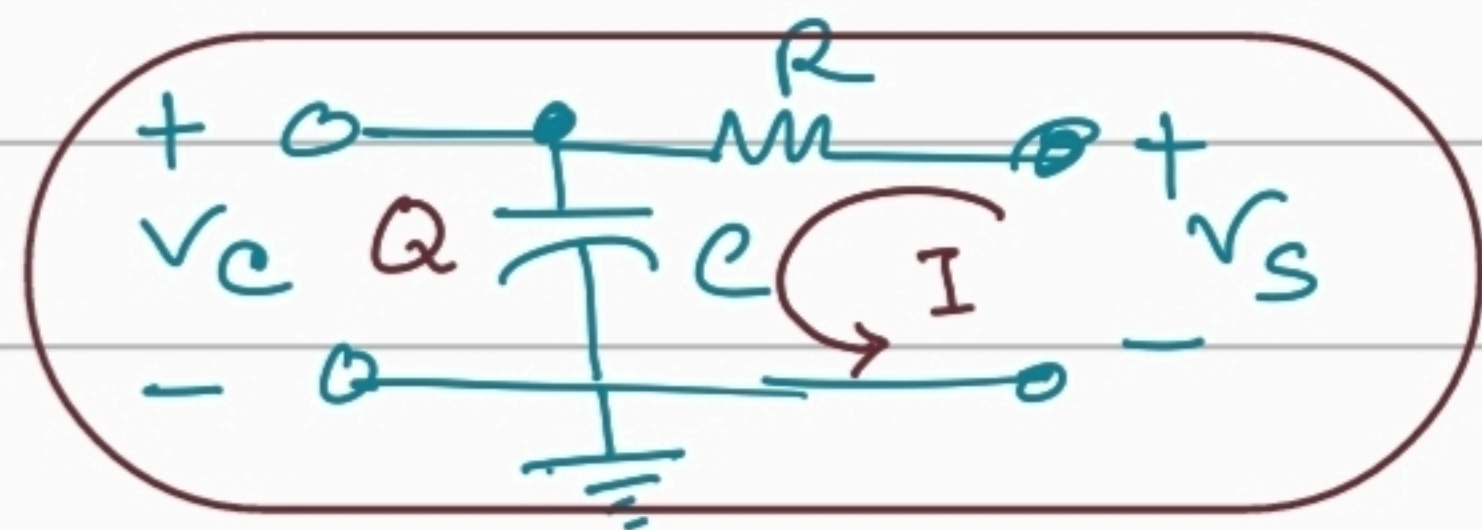

Suppose, at initial time t_1 , the capacitor has a voltage $V_C(t_1) = V_{\text{initial}}$.

If $V_S > V_C(t_1)$, $Q \uparrow$ and

if $V_S < V_C(t_1)$, $Q \downarrow$.

From the definition of current flow, we know that, $I = \frac{dQ}{dt}$

Using the definition of capacitance ($C = \frac{Q}{V}$)

$$I = \frac{dQ}{dt} = \frac{d}{dt}(CV_C) = \boxed{C \frac{dV_C}{dt} = \frac{V_S - V_C}{R}}$$

We want to determine the voltage across capacitor for the time $t_1 < t < \infty$.