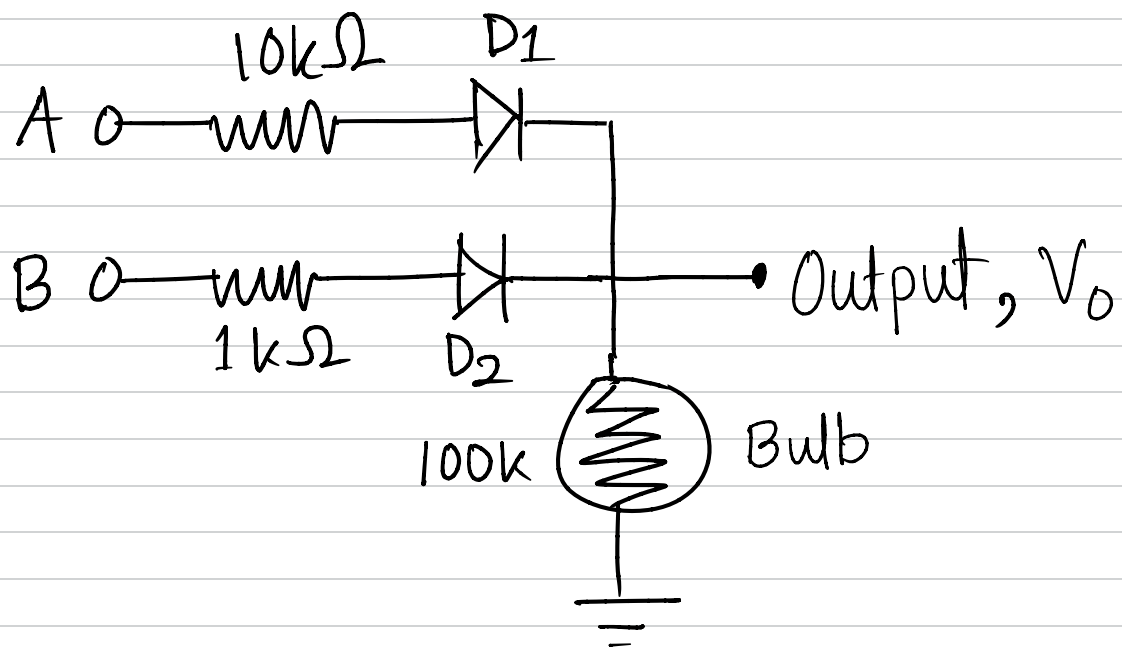


Week 1

Diode Logic


Question 1



Solve the circuit to find the output voltage for each of the input combinations.

Calculate the average power dissipation.

Solution:

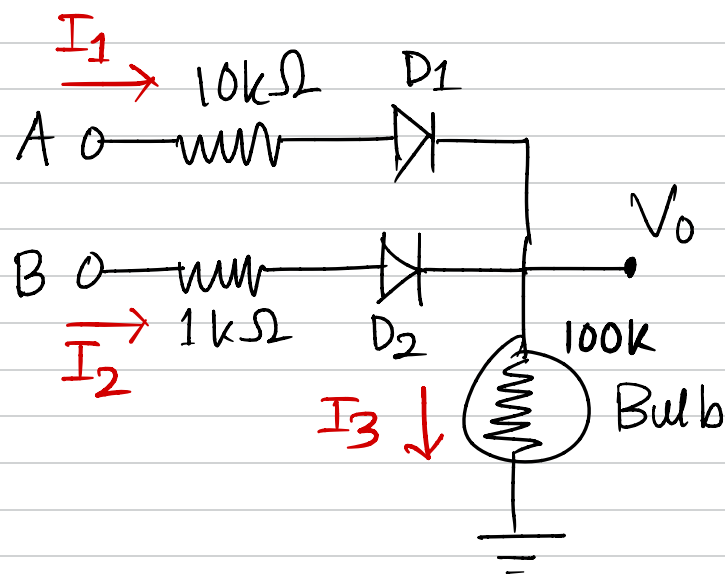

Case 1:

$$A = B = 0\text{ V}$$

Both diodes D_1 and D_2 are OFF

$$V_0 = 0\text{ V}$$

Case 2: $A = 5\text{ V}$, $B = 0\text{ V}$

Diode D_1 will be ON, D_2 will be OFF

Nodal Analysis $\Rightarrow$

$$I_1 + I_2 = I_3$$

$$\Rightarrow \frac{5 - (V_0 + 0.7)}{10\text{k}} + 0 = \frac{V_0 - 0}{100\text{k}}$$

$$\Rightarrow V_0 = 3.91\text{ V}$$

Case 3: $A = 0 \text{ V}$, $B = 5 \text{ V}$

Diode D_1 will be OFF, D_2 will be ON

Nodal Analysis $\Rightarrow$

$$I_1 + I_2 = I_3$$

$$\Rightarrow 0 + \frac{5 - (V_0 + 0.7)}{1k} = \frac{V_0 - 0}{100k}$$

$$\Rightarrow V_0 = 4.25 \text{ V}$$

Case 4: $A = 5 \text{ V}$, $B = 5 \text{ V}$

Both diode D_1 and D_2 will be OFF

Nodal Analysis $\Rightarrow$

$$I_1 + I_2 = I_3$$


$$\Rightarrow \frac{5 - (V_0 + 0.7)}{10k} + \frac{5 - (V_0 + 0.7)}{1k} = \frac{V_0 - 0}{100k}$$

$$\Rightarrow V_0 = 4.26 \text{ V}$$

Power Dissipation


Case 1:

$$\begin{aligned} P &= \sum \Delta V I \\ &= (0-0) \times 0 \\ &= 0 \text{ W} \end{aligned}$$

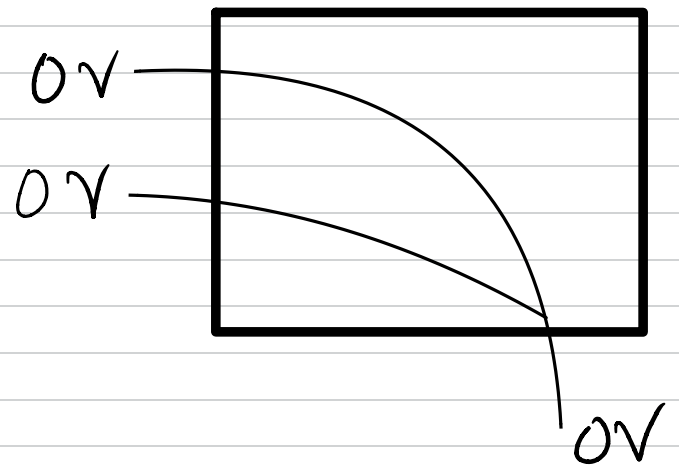


Case 2:

$$\begin{aligned} P &= \sum \Delta V I \\ &= (5-0) \times \frac{3.91}{100k} \\ &= 0.195 \text{ mW} \end{aligned}$$

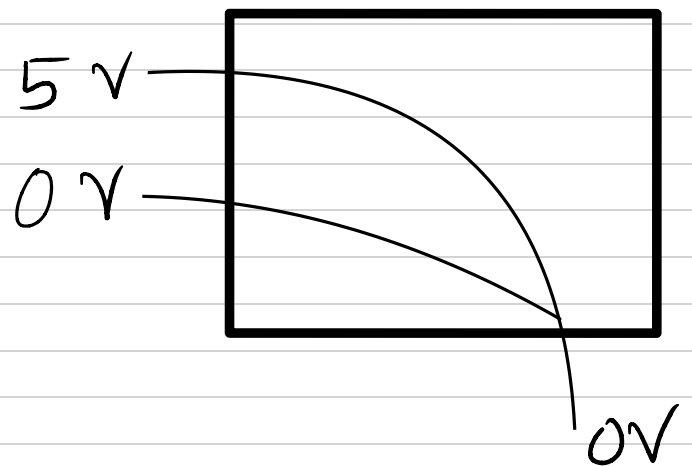


Case 3:

$$\begin{aligned} P &= \sum \Delta V I \\ &= (5-0) \times \frac{4.25}{100k} \\ &= 0.2125 \text{ mW} \end{aligned}$$

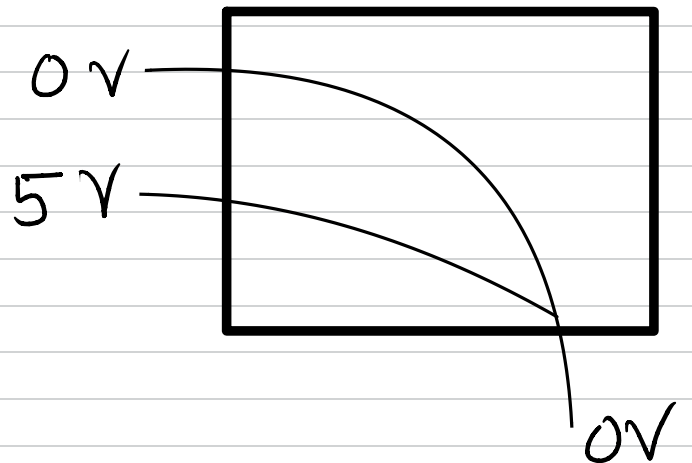

Case 4:
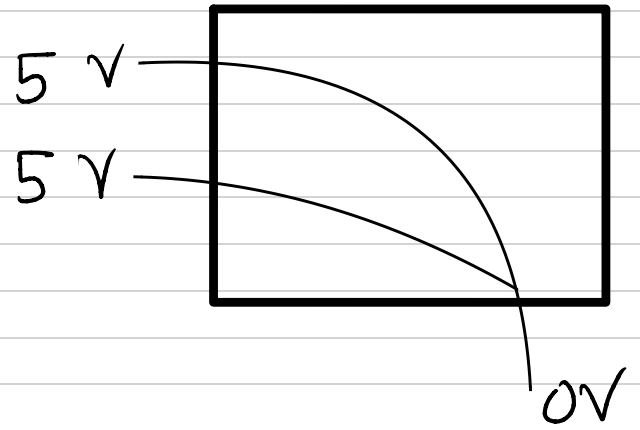
$$\begin{aligned} P &= \sum \Delta V I \\ &= (5-0) \times \frac{4.26}{100k} \\ &= 0.213 \text{ mW} \end{aligned}$$



Alternate approach


$$\begin{aligned} P &= \sum \Delta V I \\ &= (5-0) \times \frac{5-(4.26+0.7)}{10k} + (5-0) \times \frac{5-(4.26+0.7)}{1k} \\ &= 0.213 \text{ mW} \end{aligned}$$

$\therefore$ Average power dissipation

$$= \frac{0+0.195+0.2125+0.213}{4}$$

$$= 0.155 \text{ mW}$$

Question 2

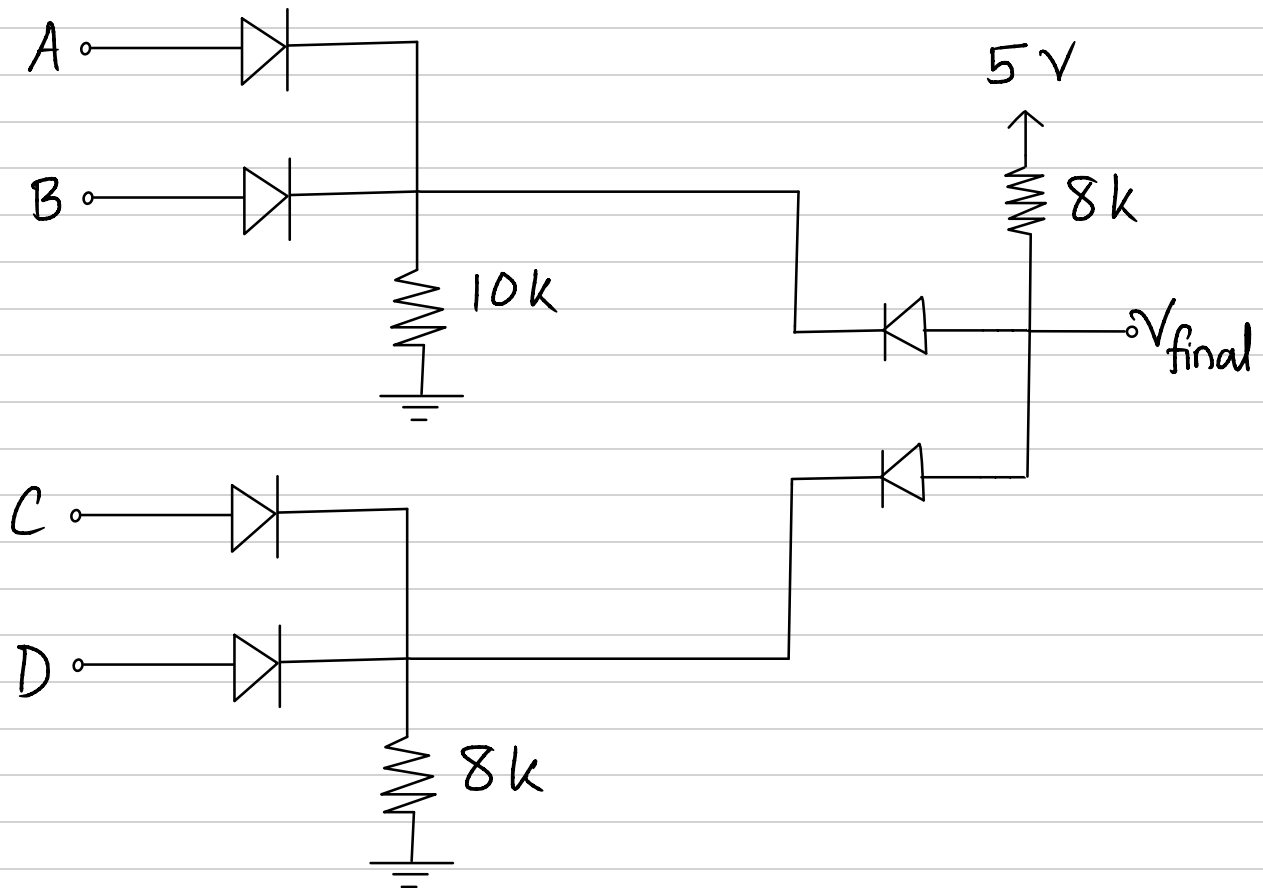

Determine the boolean expression of V_{final} in terms of input A, B, C, D


Solution: $V_{final} = (A+B) \cdot (C+D)$

Week 1 - DL

Question 3

For the given DL AND Gate circuit if $V(\text{LOW}) = 0 \text{ V}$ and $V(\text{HIGH}) = 5 \text{ V}$.

- | | |
|-----|---|
| (a) | Find out the output voltage V_o for each input combination. |
| (b) | Find out the maximum power dissipation. |

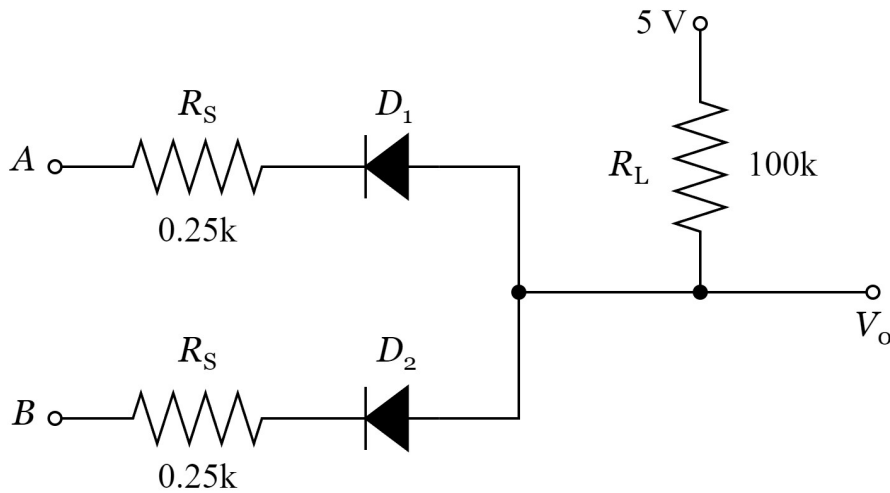


Solution:

- | | |
|-----|---|
| (a) | Find out the output voltage V_o for each input combination. |
|-----|---|

Case 1: $V_A = V_B = 5 \text{ V}$

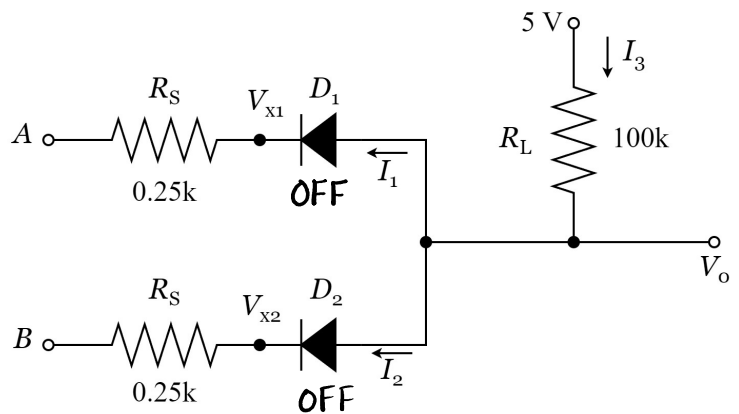Then diodes D_1 and D_2 are OFF because cathode voltage is higher than anode voltage



$$\therefore I_1 = I_2 = I_3 = 0$$


$\therefore$ No voltage difference across R_L .

$$\therefore V_o = 5 \text{ V}$$

Case 2: $V_A = 0\text{ V}$, $V_B = 5\text{ V}$

D_1 ON since Cathode Voltage $<$ Anode Voltage

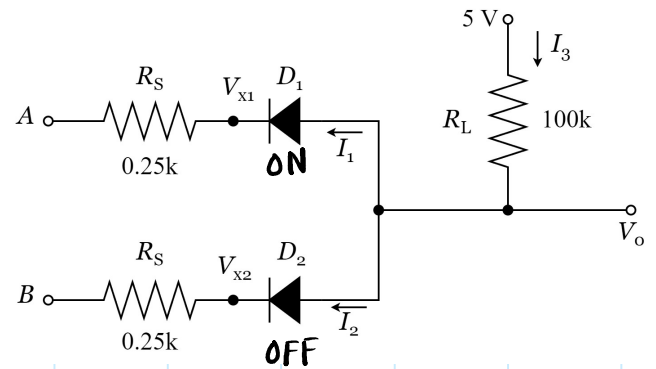D_2 OFF since Cathode Voltage $>$ Anode Voltage



$$\therefore I_2 = 0 \text{ and } I_1 = I_3$$

$$\text{Now, } I_3 = \frac{5 - V_O}{100\text{k}\Omega}$$

$$\begin{aligned} \text{and, } I_1 &= \frac{V_{x1} - 0}{0.25\text{k}} \\ &= \frac{(V_O - 0.7) - 0}{0.25\text{k}} \end{aligned}$$

$$\text{Since, } I_1 = I_3$$


$$\Rightarrow \frac{V_O - 0.7}{0.25\text{k}} = \frac{5 - V_O}{100\text{k}}$$

$$\Rightarrow V_O = 0.71\text{ V}$$

Case 3: $V_A = 5\text{ V}$, $V_B = 0\text{ V}$

D_1 OFF since Cathode Voltage $>$ Anode Voltage

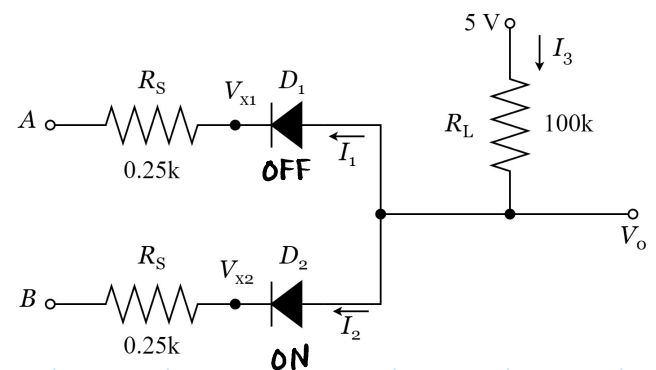D_2 ON since Cathode Voltage $<$ Anode Voltage



$$\therefore I_1 = 0 \text{ and } I_2 = I_3$$

$$\text{Now, } I_3 = \frac{5 - V_o}{100k\Omega}$$

$$\begin{aligned} \text{and, } I_2 &= \frac{V_{x2} - 0}{0.25k} \\ &= \frac{(V_o - 0.7) - 0}{0.25k} \end{aligned}$$

$$\text{Since, } I_2 = I_3$$

$$\Rightarrow \frac{V_o - 0.7}{0.25k} = \frac{5 - V_o}{100k}$$


$$\Rightarrow V_o = 0.71 \text{ V}$$

Case 2 and Case 3 are similar because the device is symmetric

Case 4: $V_A = 0 \text{ V}$, $V_B = 0 \text{ V}$

D_1 ON since Cathode Voltage < Anode Voltage

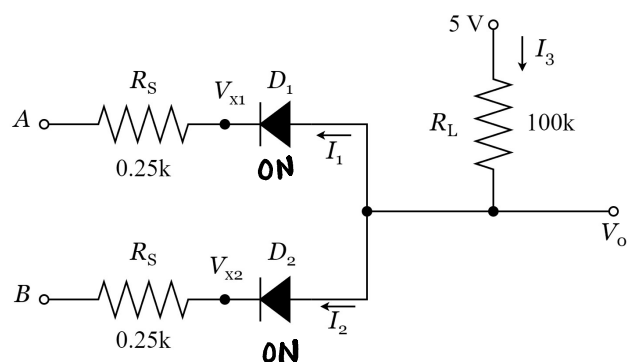D_2 ON since Cathode Voltage < Anode Voltage



$$I_1 = I_2 = \frac{V_o - 0.7}{0.25k}$$

$$I_3 = I_1 + I_2 = 2I_1$$

$$\Rightarrow \frac{5 - V_o}{100k} = 2 \times \frac{V_o - 0.7}{0.25k}$$

$$\Rightarrow V_o = 0.7054 \text{ V}$$

(b) Find out the maximum power dissipation.

Max power dissipation happens when current is maximum. This happens when V_o is Lowest (case 4)

$$\therefore V_o = 0.7054 \text{ V and } I_3 = \frac{5 - 0.7054}{100k}$$
$$= 0.429 \text{ mA}$$

$$\therefore \text{Power Dissipation} = \sum I \Delta V$$
$$= I_3 (5 - 0)$$
$$= 0.2147 \text{ mW}$$

