



Total Marks: 60 (20×3)

Time: **90 Minutes**

- Total no of questions are **four (4)**. Answer any **three (3)**.
- Figure in bracket [] next to each question indicates marks for that question.
- Write your set number on top of your answer sheet
- There is no need to draw circuits in your answer sheet.

Name:	ID:	Section:
-------	-----	----------

Question 1

[20]

For this **Schmitt Trigger** circuit in Figure 1, given: $V_H = 10\text{ V}$, $V_L = -10\text{ V}$, $v_{ref} = 2\text{ V}$.

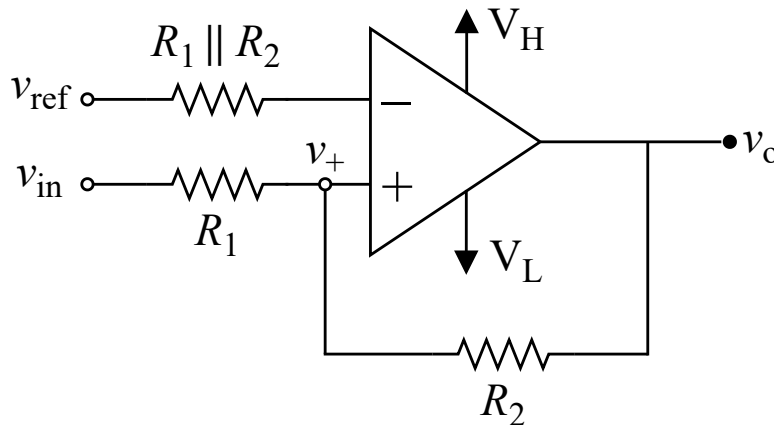


Figure 1: Schmitt Trigger

CO1	(a)	What type of Schmitt trigger circuit is this (inverting or non-inverting)?	[2]
-----	-----	---	-----

For question (b), given: $R_1 = 1\text{ k}\Omega$ and $R_2 = 2\text{ k}\Omega$.

CO1	(b)	Draw the VTC (v_i vs v_o) with appropriate labels (Values of V_H , V_L , V_{TH} , V_{TL} , Hysteresis Width)	[8]
-----	-----	--	-----

Consider the same Figure 1. Now for question (c), $V_{TH} = 5\text{ V}$, $V_{TL} = 0\text{ V}$ and $R_1 || R_2 = 4\text{ k}\Omega$.

CO1	(c)	Calculate the value of R_1 and R_2 .	[10]
-----	-----	--	------

Question 2

[20]

Figure 2 consists of a square wave generator, and Figure 3 depicts a logical function.

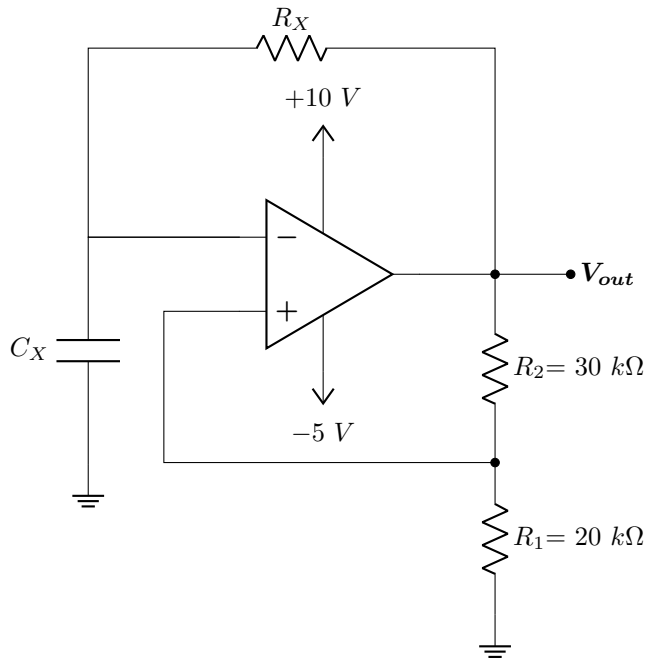


Figure 2: Square Wave Generator

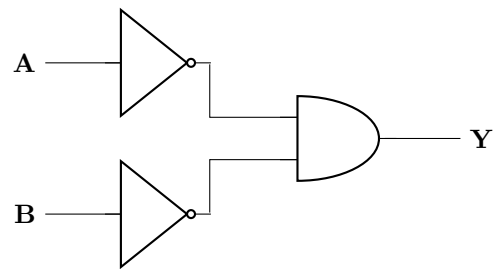


Figure 3: Logic Circuit

Consider the square wave generator in Figure 2.

CO1	(a)	Determine the values of V_{TH} (<i>upper threshold</i>) and V_{TL} (<i>lower threshold</i>).	[2+2]
CO1	(b)	Determine the period, time constant, and the duty cycle of the square wave generator, given that the frequency is 100 Hz .	[8]

Consider the logic circuit in Figure 3.

CO1	(a)	Design the equivalent CMOS logic circuit for the logic circuit using a combination of NMOS and PMOS transistors. Hence, write down the truth table showing the "ON" or "OFF" state of the MOSFETS for each input case.	[8]
-----	-----	--	-----

Question 3

[20]

The figure below shows the input-output characteristics of a converter. The output of the converter is denoted as V_o and the input as V_{in} .

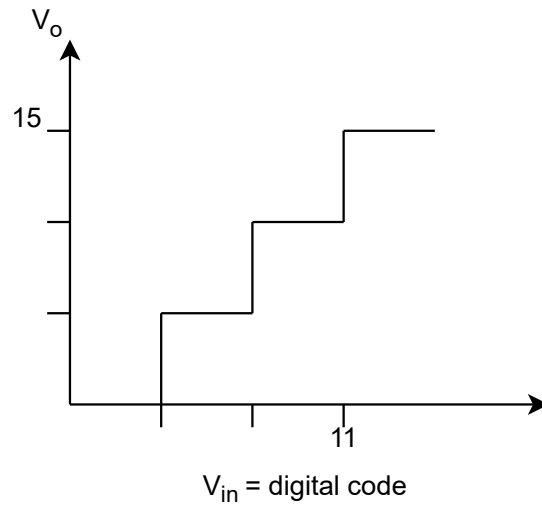


Figure 4

CO3	(a)	Identify the converter type and the number of bits used by the converter. Further, calculate V_{ref} when $R_F = 2R$.	[2+4]
CO3	(b)	Draw the converter with appropriate values from part (a).	[4]
CO3	(c)	Calculate all the outputs, V_o , for the converter. Copy the transfer curve in Figure 4 and write down the missing input and output values.	[8+2]

Question 4

[20]

The figure shows a 2-bit Flash ADC with $V_{REF} = 10V$ and its input ranged from 0 to 10V. **Given:** $R_1 = 5k\Omega$, $R_2 = 10k\Omega$, $R_3 = 10k\Omega$, $R_4 = 15k\Omega$. The two outputs of the ADC are connected to two LEDs.

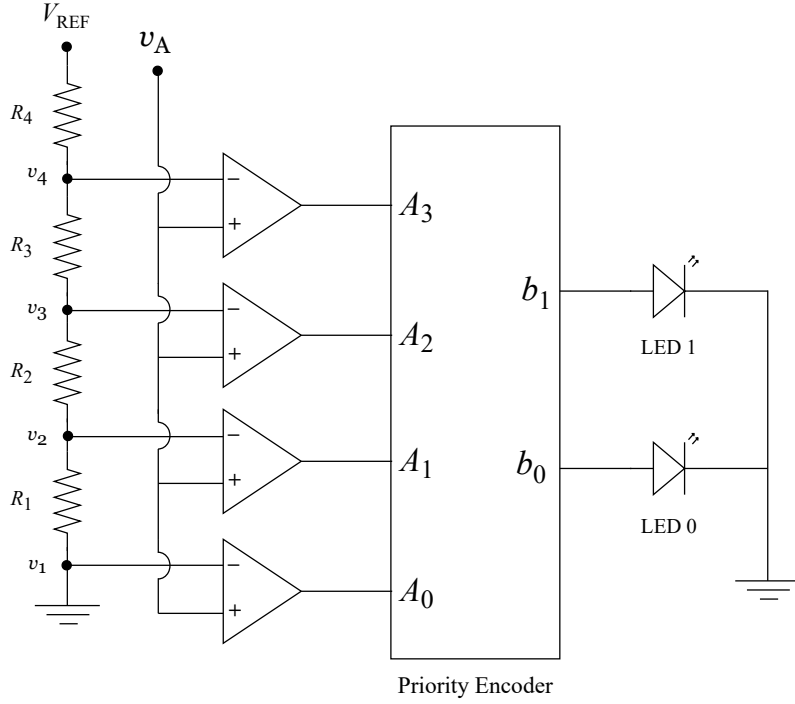


Figure 5: 2-bit flash ADC

Sampled Value (V)	Time (s)
5.00	0.0
7.40	0.5
5.71	3.0
1.22	4.0

Table 1: Sampled values at different time instances

CO3	(a)	Determine the quantization range, corresponding digital output, and the states of the LED for the 2-bit Flash ADC shown in Figure 5.	[5+5]
CO3	(b)	Four sample values at four different time instances obtained from an analog signal are shown in Table 1. Identify the quantization range for each sampled value. Determine the corresponding encoded output, and identify the states of the LEDs.	[5+5]