

ADC + DAC: Md. Jahin Alam Jishnu Mahmud



Signal Generator + Schmitt trigger: Md Obaidur Rahman ,
Himaddri Roy

MOS+CMOS: Tasnim Ferdous apu, Quazi Shafayat Hossain

- While posting your question here, please follow this format:

(a)	CO	Question	[Marks]
(b)	CO	Question	[Marks]
(c)	CO	Question	[Marks]

ADC+DAC[MJA]

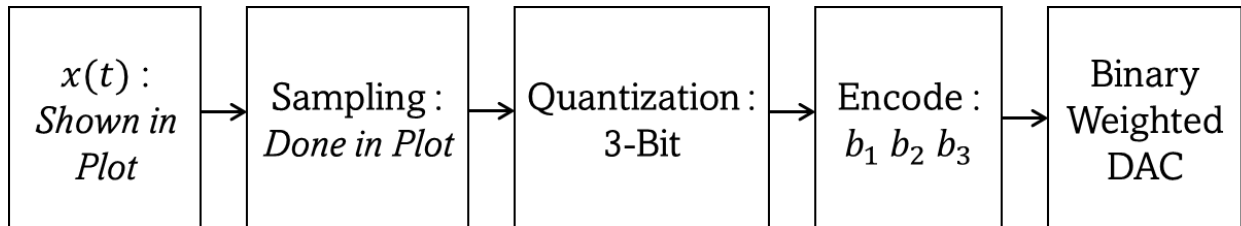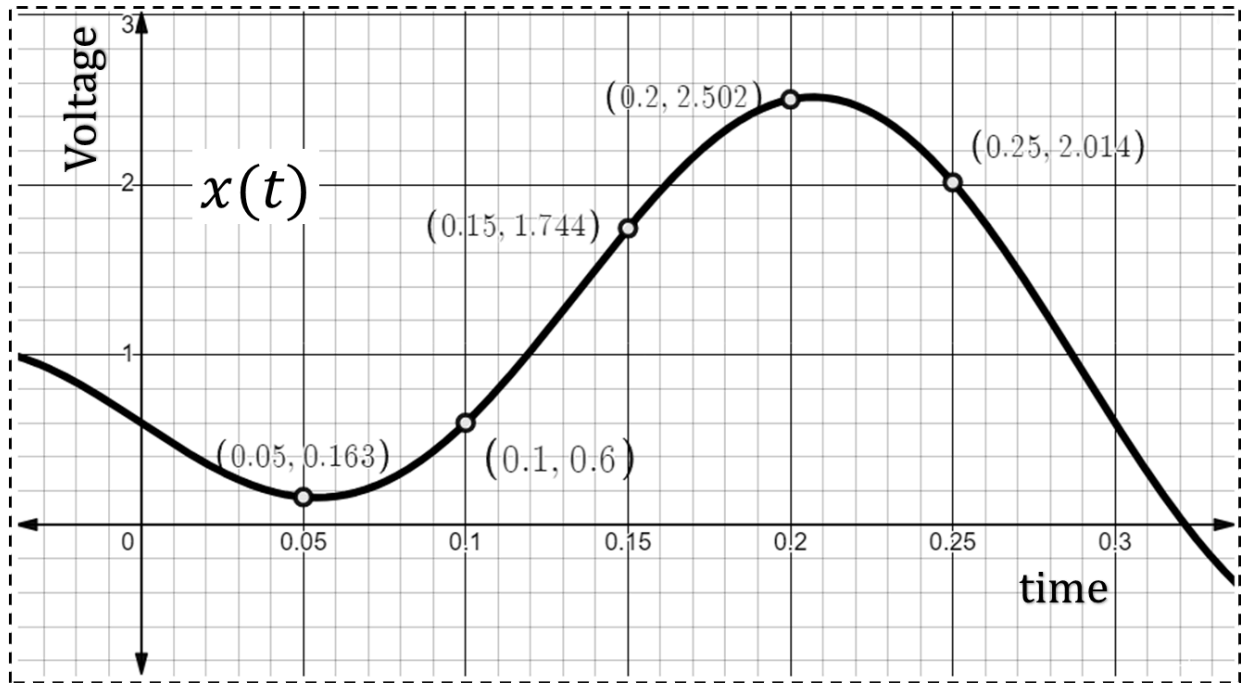

A signal $x(t)$ is provided. A process of ‘AC-DC’ and ‘DC-AC’ conversion is done to the signal. The plot shows $x(t)$ and 5 sampled (not quantized) values. The entire process is shown in the flow chart above. The conversion is done using the following known quantities:

$$V_{min} = 0 \text{ V}, \quad V_{max} = 2.6 \text{ V}, \quad V_{REF} \text{ (for DAC)} = 2.6 \text{ V} \text{ [Set-A]}$$

$$V_{min} = 0 \text{ V}, \quad V_{max} = 3.2 \text{ V}, \quad V_{REF} \text{ (for DAC)} = 3.2 \text{ V} \text{ [Set-B]}$$

(a)	CO2	Determine the Resolution, Δ . Then, find all the quantization ranges for the ‘AC-DC’ conversion above.	[2+8]
(b)	CO2	Find the quantized ranges that will be assigned to the 5 sampled values. Also, find the encoded version for each of them $[b_1 \ b_2 \ b_3]$.	[2.5+2.5]
(c)	CO2	Use the encoded values of the 5 points and pass it through the DAC shown above. What are the 5 outputs from it?	[5]

Set A :-

(a) $\Delta = \frac{2.6}{2^3} = 0.325 \text{ V}$

Quantization Range	7	2.6	}	111
		2.275		
	6	1.95	}	110
		1.625		
	5	1.3	}	100
		0.975		
	3	0.65	}	010
		0.325		
	1	0	}	000


Set-B :-

(a) $\Delta = \frac{3.2}{2^3} = 0.4$

Quantization Range	7	3.2	}	111
		2.8		
	6	2.4	}	110
		2.0		
	5	1.6	}	100
		1.2		
	3	0.8	}	010
		0.4		
	1	0	}	000


(b) 5 sampled values

0.163, 0.6, 1.744, 2.502, 2.014

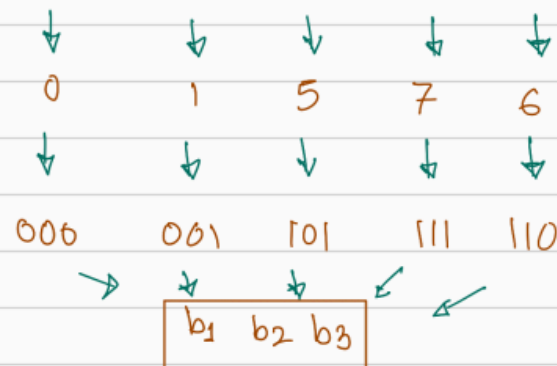


(b) 5 sampled values

0.163, 0.6, 1.744, 2.502, 2.014

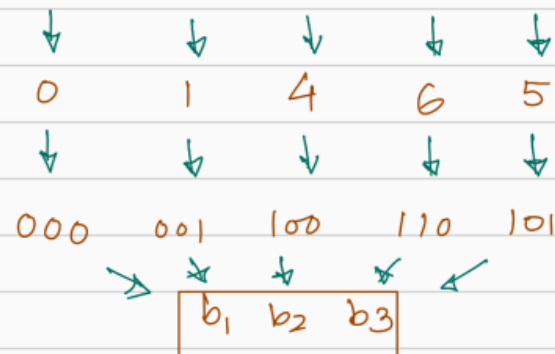

(c) ADE V_o [$R_f = R$] $= V_{ref} \left(b_1 + \frac{b_2}{2} + \frac{b_3}{4} \right)$ # The 5 outputs : $V_{ref} = 2.6$ (i) 0V (ii) 0.65V (iii) 3.25V (iv) 4.55V (v) 3.9V Does not Match	(c) ADE V_o [$R_f = R$] $= V_{ref} \left(b_1 + \frac{b_2}{2} + \frac{b_3}{4} \right)$ # The 5 outputs : $V_{ref} = 3.2$ (i) 0V (ii) 0.8V (iii) 3.2V (iv) 4.8V (v) 4V Does not Match
--	---

Schmitt Trigger [OBR]

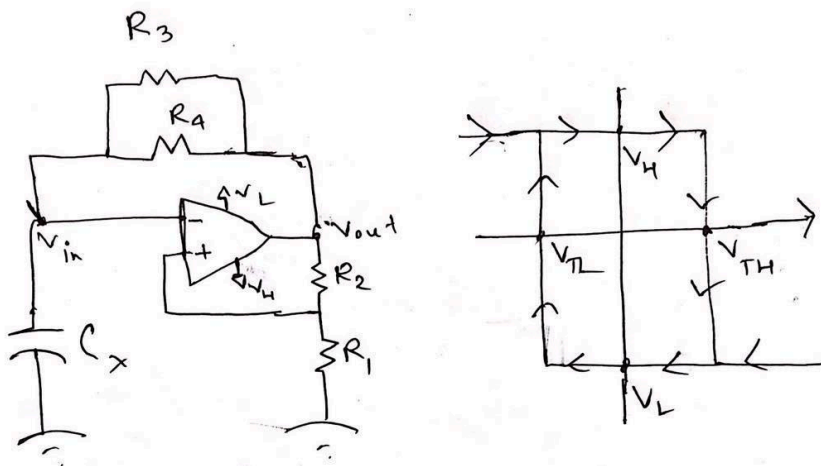

For the following circuit, the value of C_x , R_2 , R_3 and R_4 are $0.05\mu F$, $15k\Omega$, $60k\Omega$ and $100k\Omega$. In the figure, the values of V_H , V_L and V_{TH} are 8V, -10V and 5.5 V.

(a)	CO3	Find the hysteresis Width and value of R_1 .	[2.5+2.5]
(b)	CO3	Find the frequency and duty cycle of the signal generator.	[7]
(c)	CO3	Draw the graph of (V_{in} vs t) and (V_{out} vs t) with clearly showing the maximum and minimum value of each signal and time period.	[4]
(d)	CO3	If R_3 is removed, what are the effects on duty cycle and time period? If V_{TH} is increased, what are the effects on duty cycle and time period?	[2+2]

Set - A

(a)

$$V_{TH} = \frac{R_1}{R_1 + R_2} V_H$$

$$\Rightarrow (5.5 = \frac{R_1}{R_1 + 15} \times 8)$$

$$\Rightarrow \boxed{R_1 = 33k\Omega}$$

$$\frac{V_{TH}}{V_{TH}} = \frac{V_L}{V_H} = (-6.875V) \leftarrow V_{TH}$$

$$\therefore \text{width} = \boxed{12.375V}$$

Set - B

$$V_{TH} = \frac{R_1}{R_1 + R_2} V_L$$

$$\Rightarrow (-7.5) = \frac{R_1}{R_1 + 15} \times (-10)$$

$$\Rightarrow \boxed{R_1 = 45k\Omega}$$

$$\frac{V_{TH}}{V_{TH}} = \frac{V_H}{V_L} \Rightarrow \boxed{V_{TH} = 6V}$$

$$\therefore \text{width} = \boxed{13.5V}$$

(b) $R_x = (100 \parallel 160) = 37.5k\Omega$

$$T_1 = R_x C_x \ln \left| \frac{V_H - V_{TH}}{V_H - V_{TH}} \right|$$

$$\boxed{T_1 = 3.34ms}$$

$$T_2 = R_x C_x \ln \left| \frac{V_L - V_{TH}}{V_L - V_{TH}} \right|$$

$$\boxed{T_2 = 3ms}$$

$$f = \frac{1}{T_1 + T_2} = \boxed{157.728Hz}$$

$R_x = (65 \parallel 90) = 37.74k\Omega$



$$T_1 = R_x C_x \ln \left| \frac{V_H - V_{TH}}{V_H - V_{TH}} \right|$$

$$\boxed{T_1 = 3.47ms}$$

$$T_2 = R_x C_x \ln \left| \frac{V_L - V_{TH}}{V_L - V_{TH}} \right|$$

$$\boxed{T_2 = 3.15ms}$$
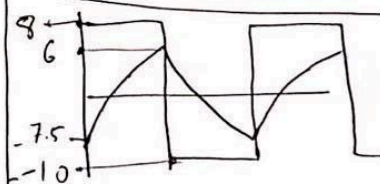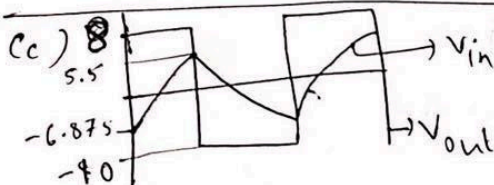
$$f = \frac{1}{T_1 + T_2} = \boxed{151.057Hz}$$




(d) R_3 remove $\rightarrow R_x \uparrow \rightarrow T$ increase
duty cycle $\rightarrow$ fix


$V_{TH} \uparrow \rightarrow T_1 \uparrow, T_2 \downarrow$
 $T \rightarrow$ uncertain
duty cycle $\rightarrow \uparrow$

MOSFET+CMOS[TAF]

Ques1:

The enhancement-load NMOS NOR gate in the figure is biased at $V_{DD} = 5\text{ V}$. The transistor parameters are $K_n = 0.3\text{ mA/V}^2$, $V_{TN1} = 0.5\text{ V}$, $V_{TN2} = 0.8\text{ V}$, $V_{TNL} = 0.7\text{ V}$.

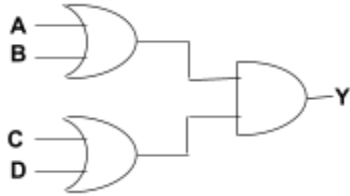CO1	(a)	Find the operating mode of the load NMOS transistor.	[2]
CO1	(b)	Find the value of v_o in V and I_{DL} , I_{D1} , I_{D2} in mA for $v_1 = 5\text{ V}$, $v_2 = 5\text{ V}$	[4+6]
CO1	(c)	Given is a static CMOS compound gate.  i. Identify the boolean function for output, Y. ii. Design the CMOS circuit for Y. Clearly show the PMOS and NMOS networks.	[2+6]

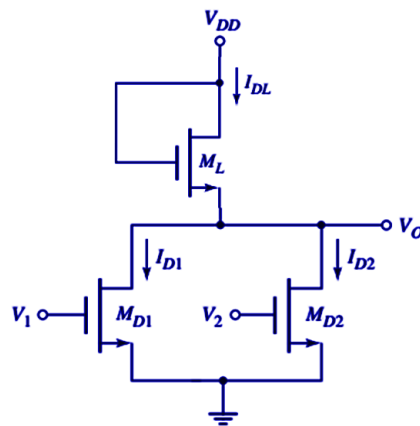

Solution :

Set A: $K_n = 0.3 \text{ mA/V}^2$, $V_{TN1} = 0.5$, $V_{TN2} = 0.8 \text{ V}$; $V_{TNL} = 0.7 \text{ V}$

Set B: $K_n = 0.35 \text{ mA/V}^2$, $V_{TN1} = 0.55$, $V_{TN2} = 0.8 \text{ V}$; $V_{TNL} = 0.7 \text{ V}$

a) $V_{DS} \geq V_{GS} - V_{TH} \rightarrow V_{GS} = V_{DSL}$ [operating mode $\rightarrow$ ML $\rightarrow$ 2 marks]
 [saturation] As, $V_{DSL} > V_{DSL} - V_{TNL}$; M_L always in saturation.

b) $V_1 = V_2 = 5 \text{ V}$
 $I_{DL} = I_{D1} + I_{D2}$ [$V_0, I_{DL}, I_{D1}, I_{D2} \rightarrow$ 2 marks each]

$$\Rightarrow K_n (V_{GS} - V_{TNL})^2 = K_n [2(V_{GS_{D1}} - V_{TN_{D1}})V_{DS_{D1}} - V_{DS_{D1}}^2] + K_n [2(V_{GS_{D2}} - V_{TN_{D2}})V_{DS_{D2}} - V_{DS_{D2}}^2]$$

$$\Rightarrow (V_{DD} - V_0 - V_{TNL})^2 = [2(V_1 - V_{TN_{D1}})V_0 - V_0^2] + [2(V_2 - V_{TN_{D2}})V_0 - V_0^2]$$

Set A

$$\Rightarrow (4.3 - V_0)^2 = 17.4V_0 - 2V_0^2$$

$$\Rightarrow 18.49 - 8.6V_0 + V_0^2 = 17.4V_0 - 2V_0^2$$

$$\Rightarrow 3V_0^2 - 26V_0 + 18.49 = 0$$

$$\Rightarrow V_0 = 7.885 \text{ V} > V_{DD}$$

① $V_0 = 0.781 \text{ V}$

② $I_{D1} = 3.71 \text{ mA}$

③ $I_{DD1} = 1.925 \text{ mA}$

④ $I_{DD2} = 1.785 \text{ mA}$

Set B

$$\Rightarrow (4.3 - V_0)^2 = 17.3V_0 - 2V_0^2$$

$$\Rightarrow 18.49 - 8.6V_0 + V_0^2 = 17.4V_0 - 2V_0^2$$

$$\Rightarrow 3V_0^2 - 25.9V_0 + 18.49 = 0$$

$$\Rightarrow V_0 = 7.847 \text{ V} > V_{DD}$$

① $V_0 = 0.785 \text{ V}$


② $I_{D1} = 4.32 \text{ mA}$

③ $I_{DD1} = 2.229 \text{ mA}$

④ $I_{DD2} = 2.092 \text{ mA}$

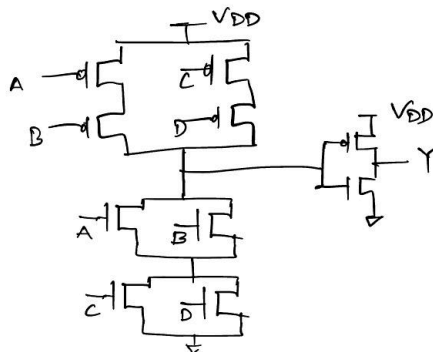c) $Y = (A+B) \cdot (C+D)$

[2 marks $\rightarrow$ Boolean Expression]



[4+4 marks $\rightarrow$ PMOS + NMOS]

Dual Slope[JMD]

Solution

Dual slope analog-digital solution:

Set A #3

(a) $t_i = 4 \times 10^{-3}$

$V_{ref} = 4V$

analog value = $2 + 2\sin(200\pi t_i) = 3.18V$ $\left\{ \begin{array}{l} \text{Rad} \\ 3.18 \checkmark \\ \text{Deg} \\ 2.09 \text{ allow} \end{array} \right.$

$$\frac{3.18}{4.00} = \frac{m}{2^N}$$

$N = 4 \text{ bit}$

$m = 12.72V \longrightarrow \boxed{1100}$

(b) $T_1 = T_p \times 2^N$

$T_1 = \frac{1}{2 \times 10^6} \times 2^4 = 8 \times 10^{-6} s$


$T_2 = T_p \times m$

$T_2 = 12.72 \times \frac{1}{2 \times 10^6} = 6.36 \times 10^{-6} s$

$\left[\text{allow } T_2 = 12 \times \frac{1}{2 \times 10^6} = 6 \times 10^{-6} s \right]$

total time = $T_1 + T_2 = (8 + 6.36) \times 10^{-6} = \boxed{14.36 \times 10^{-6} s}$

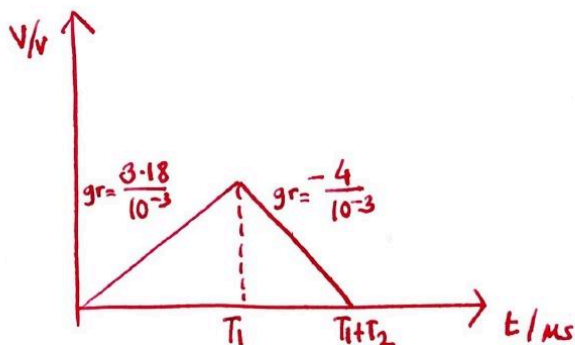$\left[\text{allow } T_1 + T_2 = (8 + 6) \times 10^{-6} = 14 \times 10^{-6} s \right]$



$RC = 1k\Omega \cdot 1\mu F$
 $= 10^3 \cdot 10^{-6} = 10^{-3}$

(c) $T_{max} = 2T_1 = 2 \times 8 \times 10^{-6} = 16 \times 10^{-6} s$

$f_{max \text{ possible}} = \frac{1}{16 \times 10^{-6}} = 62,500 \text{ Hz}$

$F_s = 4000 \text{ Hz}$

$f_{max \text{ possible}} > f_{s \text{ sampled}}$

$\left. \begin{array}{l} F_s = 4000 \text{ Hz} \\ f_{max \text{ possible}} > f_{s \text{ sampled}} \end{array} \right\} \text{ADC can support this rate}$

CSE 350

Section: B

#2

(a) analog value $y_1 = 2 + 2 \cos(300\pi t)$ $t_1 = 5 \times 10^{-3} s$

rad
analog value = 2V

Degree (allow)
= 3.993 V


$V_{ref} = 4V$

$$\frac{m}{2^4} = \frac{2}{4} \quad m = 8 \longrightarrow \boxed{1000}$$

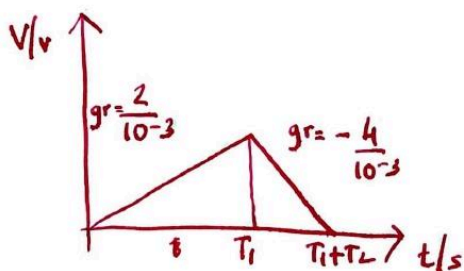(b) $T_1 = T_p \times 2^N = \frac{1}{2 \times 10^6} \times 2^4 = 8 \times 10^{-6} s$ $T_2 = T_p \times m$
 $T_2 = 8 \times \frac{1}{2 \times 10^6} = 4 \times 10^{-6} s$

total time = $T_1 + T_2 = (8 \times 10^{-6} + 4 \times 10^{-6}) = \boxed{12 \times 10^{-6} s}$

$R_e = 1k\Omega \cdot 1\mu F$
 $= 10^3 \cdot 10^{-6} = 10^{-3}$



(c) $T_{max} = 2T_1 = 16 \times 10^{-6} s$

$f_{max}^{possible} = \frac{1}{16 \times 10^{-6}} = 62,500 Hz$

$F_s = 5000 Hz$

$f_{max}^{possible} > f_{s, sampled}$

} ADC can support this rate