

Set-A Question

(a) inverting Schmitt Trigger

(b) Higher threshold, $V_{TH} = \frac{R_1}{R_1 + R_2} V_H$

$$= \frac{20k}{20k + 30k} \times 10V$$

$$V_{TH} = 4V$$

Lower threshold, $V_{TL} = \frac{R_1}{R_1 + R_2} V_L$

$$= \frac{20k}{20k + 30k} \times -5V$$

$$V_{TL} = -2V$$

(c) High time $T_1 = R_x C_x \ln \left| \frac{V_H - V_{TL}}{V_H - V_{TH}} \right|$

$$= R_x C_x \ln \left(\frac{10 + 2}{10 - 4} \right)$$

$$= R_x C_x \ln 2$$

Low time, $T_2 = R_x C_x \ln \left| \frac{V_L - V_{TH}}{V_L - V_{TL}} \right|$

$$= R_x C_x \ln \left(\frac{-5 - 4}{-5 + 2} \right)$$

$$= R_x C_x \ln 3$$

Duty cycle, $D = \frac{T_1}{T_1 + T_2} = \frac{\ln 2}{\ln 2 + \ln 3}$

$$= 0.3868 = 38.69\%$$

(d) Period, $T = T_1 + T_2 = R_x C_x (\ln 2 + \ln 3)$

$$= R_x C_x \ln 6$$

frequency = 100Hz

$$\therefore R_x C_x \ln 6 = \frac{1}{100}$$

$$\Rightarrow C_x = \frac{1}{100 R_x \ln 6} = \frac{1}{100 \times 558 \times \ln 6}$$

$$C_x = 10 \mu F = 1 \times 10^{-5} F$$

Set-B Question

(a) inverting Schmitt Trigger

(b) Higher threshold, $V_{TH} = \frac{R_1}{R_1 + R_2} V_H$

$$= \frac{10k}{10k + 30k} \times 8V$$

$$V_{TH} = 2V$$

Lower threshold, $V_{TL} = \frac{R_1}{R_1 + R_2} V_L$

$$= \frac{10k}{10k + 30k} \times -6V$$

$$V_{TL} = -4V$$

(c) High time $T_1 = R_x C_x \ln \left| \frac{V_H - V_{TL}}{V_H - V_{TH}} \right|$

$$= R_x C_x \ln \left(\frac{8 + 4}{8 - 2} \right)$$

$$= R_x C_x \ln 2$$

Low time, $T_2 = R_x C_x \ln \left| \frac{V_L - V_{TH}}{V_L - V_{TL}} \right|$

$$= R_x C_x \ln \left(\frac{-6 - 2}{-6 + 4} \right)$$

$$= R_x C_x \ln 1.5$$

Duty cycle, $D = \frac{T_1}{T_1 + T_2} = \frac{\ln 2}{\ln 2 + \ln 1.5}$

$$= 0.6309 = 63.09\%$$

(d) Period, $T = T_1 + T_2 = R_x C_x (\ln 2 + \ln 1.5)$

$$= R_x C_x \ln 3$$

frequency = 1000Hz

$$\therefore R_x C_x \ln 3 = \frac{1}{1000}$$

$$\Rightarrow C_x = \frac{1}{1000 R_x \ln 3} = \frac{1}{1000 \times 910 \times \ln 3}$$

$$C_x = 1 \mu F = 1 \times 10^{-6} F$$

Set (A)

Q2

(a) $V_{in} = low = -1.8V$

Q_1 OFF and Q_2 ON.

$V_{O1} = low = -1.8V$

So, $V_B(Q_4) = -1.8 + 0.7 = -1.1V$

$I_{Rc2} = \frac{0 - (-1.1)}{0.75k} = 1.467mA = I_E$

$I_E = 1.467mA$

(b) $V_{in} = High$

Q_1 ON, Q_2 OFF

$V_{O2} = low = -1.8V$

$V_B(Q_3) = -1.1V$

$I_{Rc1} = I_E = \frac{0 - (-1.1)}{R_{c1}}$

$\Rightarrow R_{c1} = \frac{1.1V}{1.467mA} = 0.75k\Omega$

(c) $V_{in} = High = V_{O1}$

Q_1 ON, Q_2 OFF

$V_B(Q_4) = 0V$

$V_{BE}(Q_4) = 0.7V$

$\Rightarrow V_E(Q_4) = V_{O1} = -0.7V$

$V_R = \frac{-1.8 - 0.7}{2} = -1.25V$

(d) $V_{in} = low = -1.8V$

$V_{O1} = -1.8V, V_{O2} = -0.7V$

$I_3 = \frac{(-0.7) - (-5.2)}{3k} = 1.5mA$

$I_4 = \frac{(-1.8) - (-5.2)}{3k} = 1.13mA$

$I_E = 1.467mA$

$P = \{0 - (-5.2)\} [I_3 + I_4 + I_E] = 21.3044mW$

Set (B)

(a) $V_{in} = High$

$V_{O2} = low = -1.8V$

$V_B(Q_4) = -1.8 + 0.7 = -1.1V$

$I_{Rc1} = \frac{0 - (-1.1)}{0.7k\Omega} = 1.571mA = I_E$

(b) $V_{in} = low = V_{O1} = -1.8V$

$V_B(Q_3) = -1.1V$

$I_{Rc2} = I_E = \frac{0 - (-1.1)}{R_{c2}} \Rightarrow R_{c2} = \frac{1.1V}{1.571mA} = 0.7k\Omega$

(c) $V_{in} = High \Rightarrow V_{O1} = High$

Q_1 ON, Q_2 OFF

$V_B(Q_3) = 0V$

As, $V_{BE} = 0.7V \Rightarrow V_{O1} = -0.7V = High$

$V_R = \frac{(-1.8) + (-0.7)}{2} = -1.25V$

(d) $V_{in} = High = -0.7V$

$V_{O1} = -0.7V, V_{O2} = -1.8V$

$I_4 = \frac{-1.8 - (-5.2)}{3k} = 1.13mA$; $I_3 = \frac{(-0.7) - (-5.2)}{3k} = 1.5mA$

$I_E = 1.571mA$

$P = \{0 - (-5.2)\} \{I_4 + I_3 + I_E\} = 21.8452mW$

Set-A

a)

$$V_O = -V_{REF}(b_2 + \frac{b_1}{2} + \frac{b_0}{4})$$

V_high = -4V

Encoding	VO
000	0
001	1
010	2
011	3
100	4
101	5
110	6
111	7

b)

Vref = 16V

V1 = 16/8R * R/2

V2 = 16/8R * 3R/2

Levels	Voltage
V1	1
V2	3
V3	5
V4	7
V5	9
V6	11
V7	13

Range will be
V2 < Vin < V3

For DAC, input combinations will be 011, 100, 101

c)

4 Resistors

3 Comparators

Set-B

a)

$$V_O = -V_{REF}(b_2 + \frac{b_1}{2} + \frac{b_0}{4})$$

V_high = -8V

Encoding	VO
000	0
001	2
010	4
011	6
100	8
101	10
110	12
111	14

b)

Vref = 32V

V1 = 32/8R * R/2

V2 = 32/8R * 3R/2

Levels	Voltage
V1	2
V2	6
V3	10
V4	14
V5	18
V6	22
V7	26

Range will be
V3 < Vin < V4

For DAC, input combinations will be 101, 110, 111

c)

4 Resistors

3 Comparators

Set A Question 4

(a) $\beta_F = 30$, $V_{CE(sat)} = 0.1 \text{ V}$, $\beta_R = 0.1$, $V_X = V_Y = V_Z = 6 \text{ V}$

$$I_1 = \frac{6 - 2.3}{R_1} = \frac{6 - 2.3}{10} = \boxed{0.37 \text{ mA}}$$

$$I_X = I_Y = I_Z = \beta_R I_1 = 0.1 \times 0.37 = 0.037 \text{ mA}$$

$$\therefore I_{B2} = I_1 + 3I_X = \boxed{0.481 \text{ mA}}$$

$$I_2 = \frac{V_{CC} - 0.9}{R_2} = \frac{6 - 0.9}{4} = \boxed{1.275 \text{ mA}}$$




$$I_{E2} = I_2 + I_{B2} = 1.756 \text{ mA}$$

$$I_B = \frac{0.8 - 0}{R_B} = \frac{0.8}{2} = \boxed{0.4 \text{ mA}}$$

$$\therefore I_{B0} = I_{E2} - I_B = 1.756 - 0.4 = \boxed{1.356 \text{ mA}}$$

$$I_3 = \frac{6 - 0.1}{R_c} = \frac{6 - 0.1}{5} = \boxed{1.18 \text{ mA}}$$

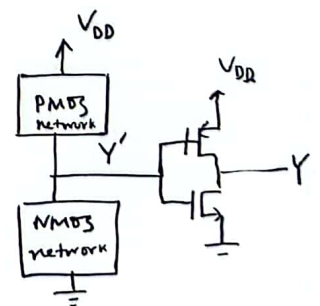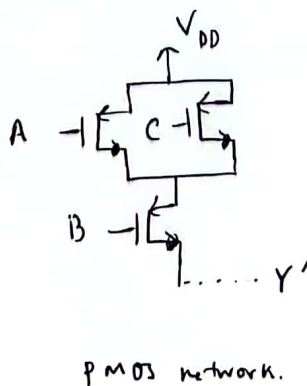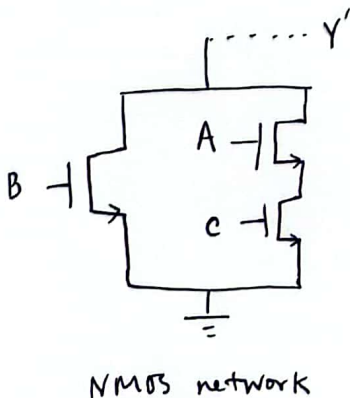(b) $Y = AC + B$. Assume, $Y' = \overline{AC + B}$



Set B Question 3

(a) $\beta_F = 30$, $V_{CE(sat)} = 0.1$, $\beta_R = 0.2$, $V_X = V_Y = V_Z = 6\text{ V}$

$$I_1 = \frac{6 - 2.3}{R_1} = \boxed{0.37\text{ mA}}$$

$$I_X = I_Y = I_Z = \beta_R I_1 = 0.2 \times 0.37 = 0.074\text{ mA}$$

$$\therefore I_{B2} = I_1 + 3I_X = \boxed{0.592\text{ mA}}$$


$$I_2 = \frac{V_{CE} - 0.9}{R_2} = \boxed{1.275\text{ mA}}$$

$$I_{E2} = I_2 + I_{B2} = 1.867\text{ mA}$$


$$I_B = \frac{0.8}{2} = \boxed{0.4\text{ mA}}, \quad I_{B0} = I_{E2} - I_B = \boxed{1.467\text{ mA}}$$

$$I_3 = \frac{6 - 0.1}{R_C} = \frac{6 - 0.1}{6} = \boxed{0.983\text{ mA}}$$

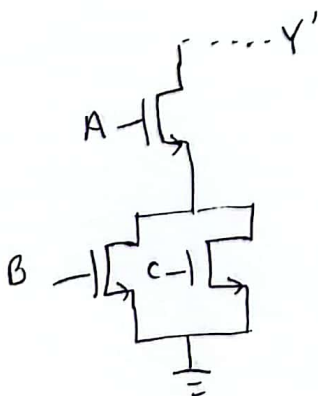(b) $y = A(B+c)$, Assume, $y' = \overline{A(B+c)}$



NMOS network

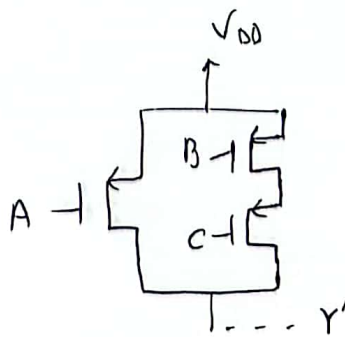

PMOS network

