

ADC + DAC - Shafayat, Himaddri

ECL - Jishnu, Himaddri

Signal Generator + Schmitt trigger - Obaidur, Jahin

TTL + MOSFET - Farhan bhai, Afia apu

Signal Generator + Schmitt trigger [JAA]

Set-A

The figure on the left is a square wave generator constructed with a schmitt trigger. The generator has a waveform depicted by the right-hand side figure.

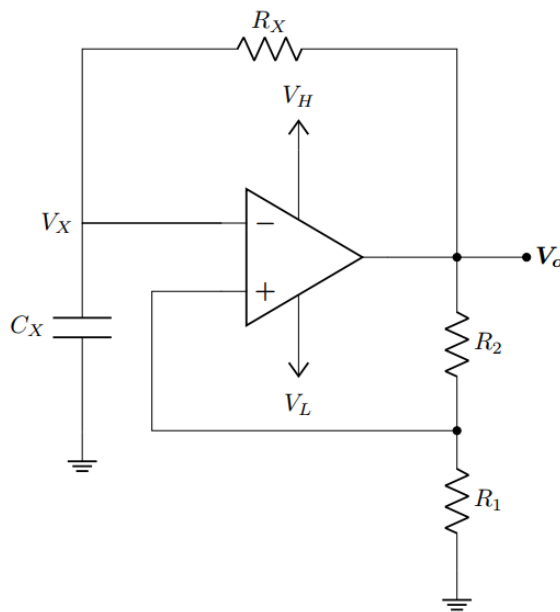


Figure 1

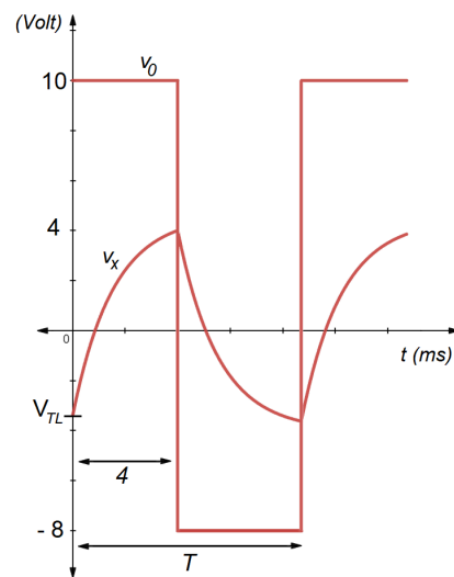


Figure 2

CO3	(a)	Identity whether the Schmitt Trigger in figure 1 is inverting or non-inverting .	[2]
CO3	(b)	Find the Hysteresis Width of the used Schmitt trigger.	[6]
CO3	(c)	Using $R_1 = 12\text{ k}\Omega$, show that R_1 is smaller than R_2 .	[4]
CO3	(d)	Determine the duty cycle of the square wave generator circuit. (<i>hint: R_x and C_x values are not required for this part</i>)	[8]

Solution - Set A

(a) *Inverting Schmitt Trigger*

$$\begin{aligned} \textcircled{b} \quad 4 &= 10 \frac{R_1}{R_1 + R_2} \rightarrow \frac{V_{TL}}{4} = -8/10 \\ V_{TL} &= -8 \frac{R_1}{R_1 + R_2} \Rightarrow \textcircled{V_{TL}} = -32/10 \\ &= \underline{\underline{-3.2V}} \end{aligned}$$

$$\therefore \text{Hysteresis Width} = V_{TH} - V_{TL} = \underline{\underline{4 + 3.2 = 7.2V}}$$

$$\begin{aligned} \textcircled{c} \quad 4 &= 10 \frac{R_1}{R_1 + R_2} \Rightarrow 4R_1 + 4R_2 = 10R_1 \\ \Rightarrow 6R_1 &= 4R_2 \Rightarrow R_2 = \frac{3}{2} R_1 \\ \Rightarrow R_2 &= \frac{3}{2} \times 12k\Omega = \underline{\underline{18k\Omega}} \end{aligned}$$

$$\textcircled{d} \quad \text{Find } T : T = T_1 + T_2$$

$$T_1 = \tau \ln \left| \frac{10 + 3.2}{10 - 4} \right| = 4$$

$$\Rightarrow \tau = 5.073 \times 10^{-3} \text{ sec}$$

$$\therefore T_2 = \tau \ln \left| \frac{-8 - 4}{-8 + 3.2} \right| = 4.648 \text{ ms}$$

$$\therefore \textcircled{T} = 8.648 \text{ ms}$$

$$\textcircled{\text{Duty}} = \frac{400}{8.648} \% = \underline{\underline{46.253\%}}$$

$$\begin{aligned} T_2 &= \tau \ln \left| \frac{V_L - V_{TH}}{V_L - V_{TL}} \right| \\ T_1 &= \tau \ln \left| \frac{V_H - V_{TL}}{V_H - V_{TH}} \right| \\ V_{TH} &= V_H \frac{R_1}{R_1 + R_2} \\ V_{TL} &= V_L \frac{R_1}{R_1 + R_2} \end{aligned}$$

Formulae :

Set-B

The figure on the left is a square wave generator constructed with a schmitt trigger. The generator has a waveform depicted by the right-handside figure.

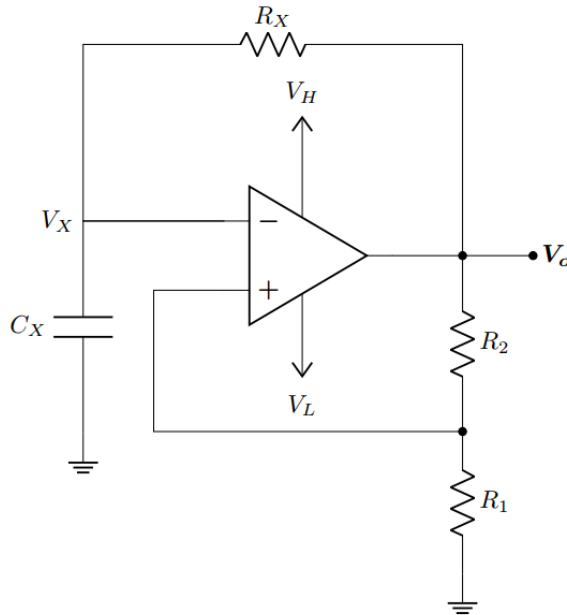


Figure 2

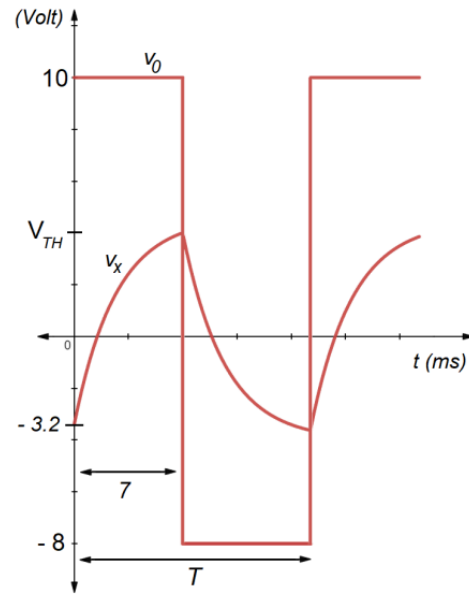


Figure 3

CO3	(a)	Identity whether the Schmitt Trigger in figure 2 is inverting or non-inverting .	[2]
CO3	(b)	Find the Hysteresis Width of the used Schmitt trigger.	[6]
CO3	(c)	Using $R_2 = 27\text{ k}\Omega$, show that R_2 is higher than R_1 .	[4]
CO3	(d)	Determine the duty cycle of the square wave generator circuit. (<i>hint: R_x and C_x values are not required for this part</i>)	[8]

Solution - Set B

(a) **Inverting Schmitt Trigger**

(b) $V_{TH} = (10/(-8)) * (-3.2) = -4V$. **Hysteresis = 7.2 V**

(c) $R_1 = (2/3) * 27 = 18\text{ k ohm}$. $R_2 > R_1$

(d) **Same process as set-A.**

The time constant, $\tau = 8.878\text{ ms}$


$T_2 = 8.135\text{ ms}$

$T = 15.135\text{ ms}$

Duty cycle = $700\% / 15.135 = 46.25\%$ (same as Set-A)

ADC + DAC [QSH]

Solution - Set A

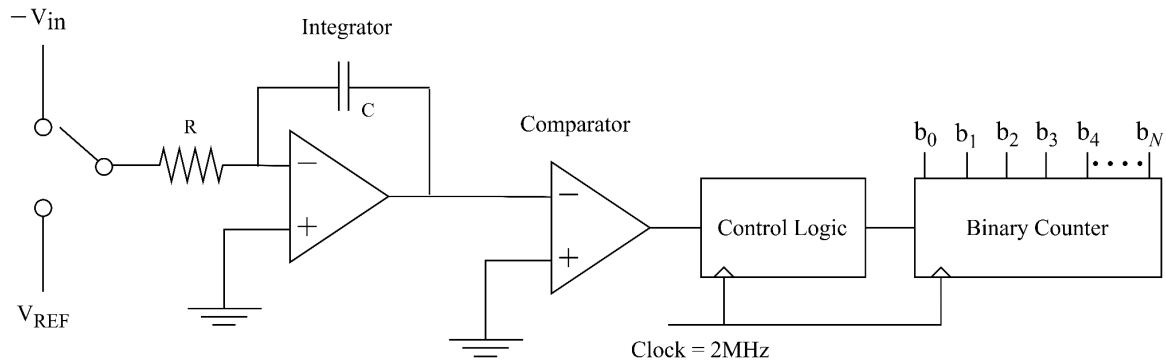

A dual slope A/D converter has $V_{REF} = 5.12$ V, and a N bit counter that outputs N -bit representation of the input signal. A 2 MHz clock is used for the clock and counter circuits

CO2	(a)	Determine the input voltage range. If step size is 0.02 V, determine the total number of steps and the number of bits used in this ADC.	7
CO2	(b)	For input voltage, $V_{in} = 3$ V, determine the ADC output count. Calculate the time required to get this output.	7
CO2	(c)	Draw V_o vs time graph for the input voltage V_{in} mentioned in (b). If $V_{in} = 4$ V, how the graph will change? Explain briefly	6

Solution:


(a) Input Voltage range = $(V_{REF} - 0) = 5.12$ V

$$\begin{aligned} \text{Total Number of Steps} &= \frac{\text{Voltage range}}{\text{step size}} \\ &= \frac{5.12}{0.02} \\ &= 256 \text{ steps} \end{aligned}$$

$$\begin{aligned} \text{Number of bits used, } N &= \log_2 256 \\ &= 8 \text{ bits} \end{aligned}$$

$$\begin{aligned} \text{(b) } V_{in} &= \frac{m}{2^N} V_{REF} \\ m &= \frac{V_{in}}{V_{REF}} 2^N \\ &= \frac{3}{5.12} 256 \\ &= 150 \text{ counts} \end{aligned}$$
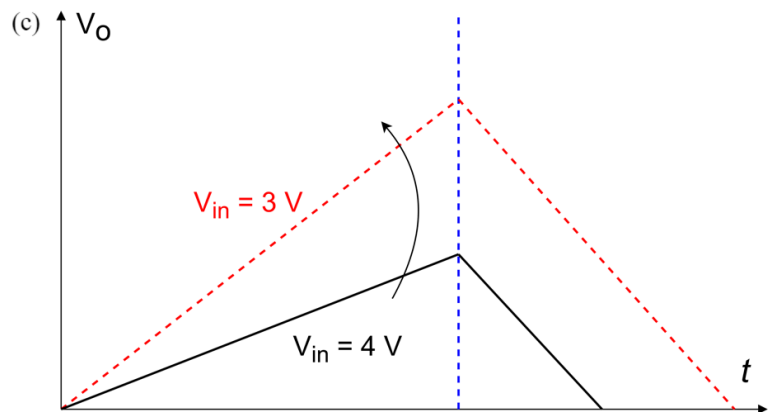
$$\begin{aligned} \text{Time required, } t &= t_1 + t_2 \\ &= \frac{256}{2 \times 10^6} + \frac{150}{2 \times 10^6} \\ &= 2.03 \times 10^{-4} \text{ seconds} \end{aligned}$$




The rising portion of the graph has a slope of $\frac{V_{in}}{RC}$

When $V_{in} = 3$ V, slope is $\frac{3}{RC}$

When input increases to $V_{in} = 4$ V, slope is $\frac{4}{RC}$. The slope increases/ becomes steeper

For both inputs, falling portion of the graphs have a slope of $-\frac{V_{REF}}{RC}$

Solution - Set B

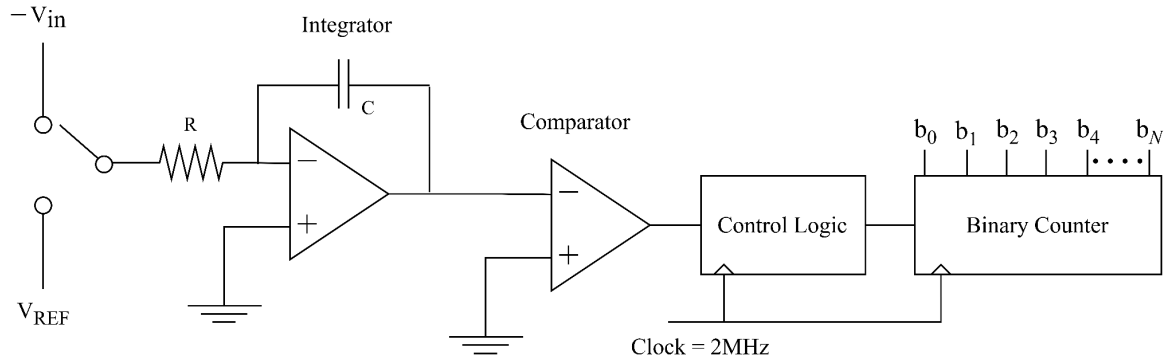

A dual slope A/D converter has $V_{REF} = 7.68$ V, and a N bit counter that outputs N -bit representation of the input signal. A 2 MHz clock is used for the clock and counter circuits

CO2	(a)	Determine the input voltage range. If step size is 0.03 V, determine the total number of steps and the number of bits used in this ADC.	7
CO2	(b)	For input voltage, $V_{in} = 6$ V, determine the ADC output count. Calculate the time required to get this output.	7
CO2	(c)	Draw V_o vs time graph for the input voltage V_{in} mentioned in (b). If $V_{in} = 4$ V, how the graph will change? Explain briefly	6

Solution:


(a) Input Voltage range = $(V_{REF} - 0) = 7.68$ V

$$\begin{aligned} \text{Total Number of Steps} &= \frac{\text{Voltage range}}{\text{step size}} \\ &= \frac{7.68}{0.03} \\ &= 256 \text{ steps} \end{aligned}$$

$$\begin{aligned} \text{Number of bits used, } N &= \log_2 256 \\ &= 8 \text{ bits} \end{aligned}$$

$$\begin{aligned} (b) \ V_{in} &= \frac{m}{2^N} V_{REF} \\ m &= \frac{V_{in}}{V_{REF}} 2^N \\ &= \frac{6}{7.68} 256 \\ &= 200 \text{ counts} \end{aligned}$$
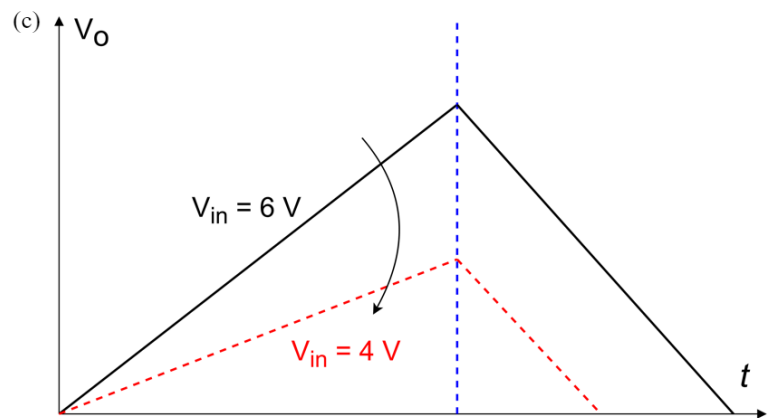
$$\begin{aligned} \text{Time required, } t &= t_1 + t_2 \\ &= \frac{256}{2 \times 10^6} + \frac{200}{2 \times 10^6} \\ &= 2.28 \times 10^{-4} \text{ seconds} \end{aligned}$$



The rising portion of the graph has a slope of $\frac{V_{in}}{RC}$

When $V_{in} = 6$ V, slope is $\frac{6}{RC}$

When input decreases to $V_{in} = 4$ V, slope becomes $\frac{4}{RC}$. The slope decreases/ becomes flatter

For both inputs, falling portion of the graphs have a slope of $-\frac{V_{REF}}{RC}$

(TTL, MOSFET)

Set-A (Q4)

$$\begin{aligned} \text{(a)} \quad I_1 &= \frac{6-2.3}{10} = 0.37 \text{ mA} \\ I_{EX} &= I_{EY} = I_{EZ} = \beta_R I_1 \\ &= 0.037 \text{ mA} \\ I_{B2} &= I_1 + 3I_{EX} \\ &= 0.481 \text{ mA} \\ I_2 &= \frac{6-0.9}{4} = 1.275 \text{ mA} \\ I_4 &= \frac{0.8}{2} = 0.4 \text{ mA} \\ I_{B0} &= I_2 + I_{B2} - I_4 \\ &= 1.356 \text{ mA} \\ I_3 &= \frac{6-0.1}{5} = 1.18 \text{ mA} \end{aligned}$$

(b) I_1, I_2, I_3, I_4 same.

$$\begin{aligned} I_{B2} &= I_1 + 2I_{EX} \\ &= 0.444 \text{ mA} \\ I_{B0} &= 1.275 + 0.444 - 0.4 \\ &= 1.319 \text{ mA} \\ I_3/I_{B0} &= 0.87 < \beta_F \\ \therefore &\text{ Saturation} \end{aligned}$$


Set-B (Q3)

$$\begin{aligned} \text{(a)} \quad I_1 &= \frac{5-2.3}{10} = 0.27 \text{ mA} \\ I_{EX} &= I_{EY} = I_{EZ} = \beta_R I_1 \\ &= 0.054 \text{ mA} \\ I_{B2} &= I_1 + 3I_{EX} \\ &= 0.432 \text{ mA} \\ I_2 &= \frac{5-1}{4} = 1 \text{ mA} \\ I_4 &= \frac{0.8}{2} = 0.4 \text{ mA} \\ I_{B0} &= I_2 + I_{B2} - I_4 \\ &= 1.032 \text{ mA} \\ I_3 &= \frac{5-0.2}{5} = 0.96 \text{ mA} \end{aligned}$$


(b) I_1, I_2, I_3, I_4 same.

$$\begin{aligned} I_{B2} &= I_1 + 2I_{EX} \\ &= 0.378 \text{ mA} \\ I_{B0} &= 1 + 0.378 - 0.4 \\ &= 0.978 \text{ mA} \\ I_3/I_{B0} &= 0.982 < \beta_F \\ \therefore &\text{ Saturation} \end{aligned}$$

(C)

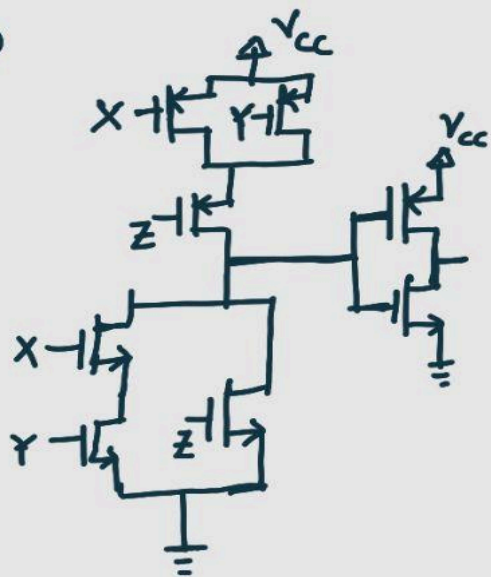

(C)

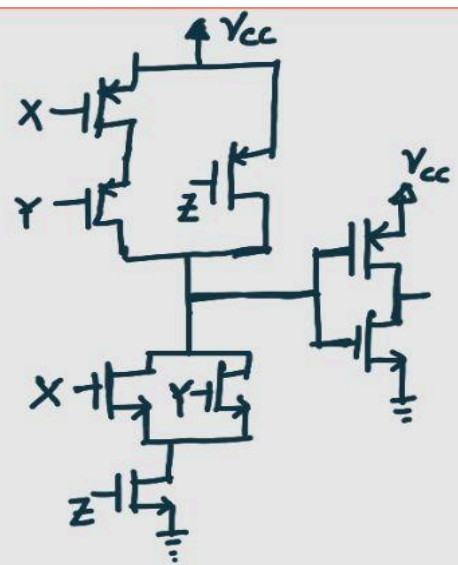

ECL

Solution- Set A

Set A Q2

(a) $V_{01} \text{ Low} = 2.5 \text{ V}$ $V_{02} = 5 - 0.7 = 4.3 \text{ V}$ (high)

$$I_{CR} = \frac{5 - V_{B4}}{0.75 \text{ k}}$$

$$V_{B4} = 2.5 + 0.7 = 3.2 \text{ V}$$

$$I_{CR} = 2.4 \text{ mA}$$

$$I_E = I_{CR} = 2.4 \text{ mA}$$

(b) $V_{02} = 2.8 \text{ V}$

$$V_{B3} = 2.8 + 0.7 = 3.5 \text{ V}$$

$$V_{C1} = V_{B3} = 3.5 \text{ V}$$

$$\frac{5 - 3.5}{R_{C1}} = I_E = 2.4 \text{ mA}$$

$$R_{C1} = 0.625 \text{ k}\Omega$$

allow

$$\frac{5 - X}{R_{C1}(\text{not max})} = 2.4 \text{ mA}$$

$$2.8 \leq X < 4$$

but cut marks as
 $R_C \neq R_{Cmax}$

(c) $V_{ref} = \frac{4.3 + 2.5}{2}$

$$= 3.4 \text{ V}$$

or

$$V_{ref} = \frac{4.3 + 2.8}{2}$$

or

$$= 3.55 \text{ V}$$

Solution- Set B

Set B Q1

$$(a) \quad V_{O1} = 3V \quad V_{B4} = 3.7V$$

$$V_{O2} = 6 - 0.7 = 5.3V$$

$$I_{CR} = \frac{6 - 3.7}{0.7} = 3.29 \text{ mA}$$

$$I_E = I_{CR} = 3.29 \text{ mA}$$

$$(b) \quad V_{O2} = 2.8V$$

$$V_{B3} = 2.8 + 0.7 = 3.5V$$

$$V_{C1} = V_{B3}$$

$$\frac{6 - 3.5}{R_{C1}} = 3.29 = I_E$$

$$R_{C1 \text{ max}} = 0.760 \text{ k}\Omega$$

allow

$$\frac{5 - X}{R_{C1} \text{ (not max)}} = 2.4 \text{ mA}$$

$$2.8 \leq X \leq 4$$

but cut marks as
 $R_C \neq R_{C \text{ max}}$

$$(c) \quad V_{ref} = \frac{2.8 + 5.3}{2}$$

$$= 4.05 \text{ V}$$

$$\text{or} \quad = \frac{3 + 5.3}{2}$$

or

$$= 4.15 \text{ V}$$