

Final Exam Questions

DAC: Tasnim Ferdous

ADC: Sazzadul Islam

S. Trigger: Quazi Shafayat Hossain Ayon Sarker

CMOS + Square Wave: shaon.eee.119@gmail.com Nur Mohammad Shaon


Please submit your questions by 22nd September 2024. Please make sure you make Set A and Set B of your question. Please provide a handwritten/latex solution with the marks distribution to your question.

- While posting your question here, please follow this format:


(a)	CO	Question	[Marks]
(b)	CO	Question	[Marks]
(c)	CO	Question	[Marks]

DAC [TNMF]

CO3	(a)	Identify the converter type and bits from the data given in Figure 1 transfer curve (V_o vs Digital Code). Calculate V_{ref} when $R_F = 2R$.	[2+4]
	(b)	Draw the converter with appropriate values from (a).	[4]
	(c)	Calculate all the outputs, V_o for the converter. Draw and fill the transfer curve of (a) with all the input and output values of the converter.	[8+2]

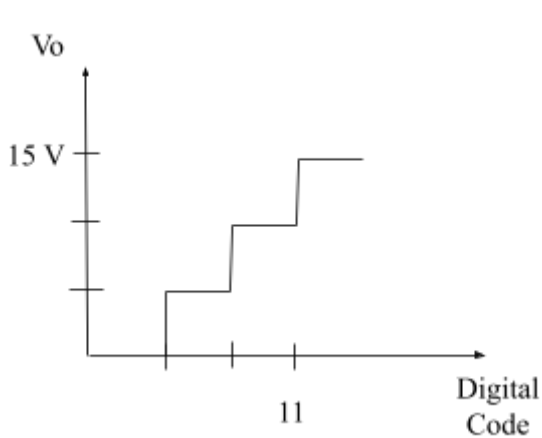

SET A

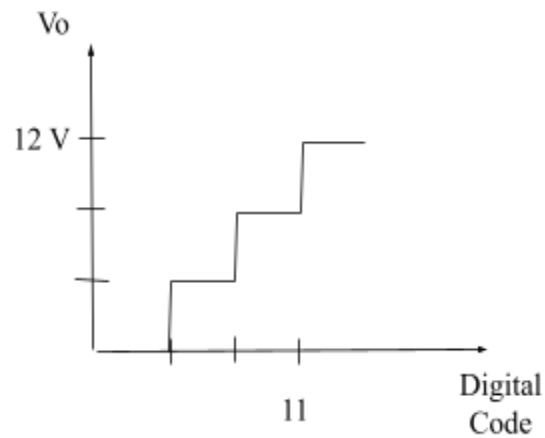

SET B

Solution

a) Binary weighted DAC. 2 bit [2]


$$V_o = -V_{ref} \cdot (2R/R) \cdot [b_1 + b_0/2] \Rightarrow V_{ref} = -V_o/3 = -15/3 = -5 \text{ V [4] [SET A]}$$

$$\Rightarrow V_{ref} = -V_o/3 = -12/3 = -4 \text{ V [4] [SET B]}$$


b) 2 bit DAC where $R_F = 2R$ [4]

c) [8+2]

V_{in}	V_o [SET A]	V_o [SET B]
00	0 V	0 V
01	5V	4V
10	10V	8V
11	15V	12V

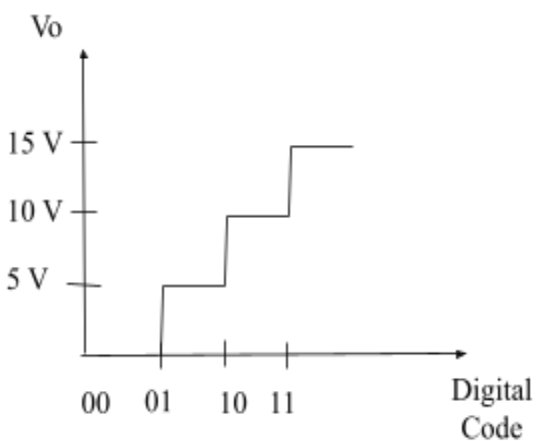

SET A

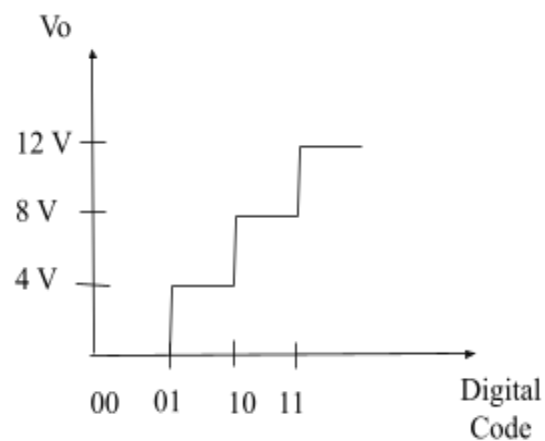

SET B

Square Wave + CMOS [NMS]

Question (Set A)

[20]

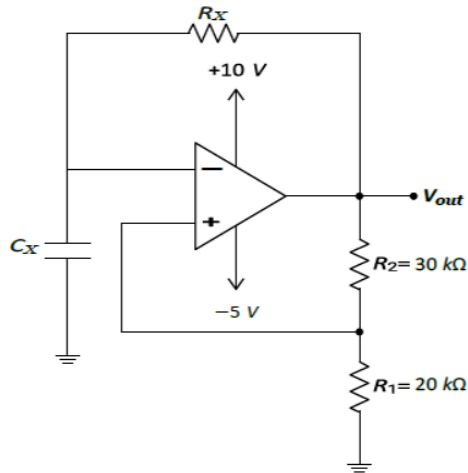


Figure 1

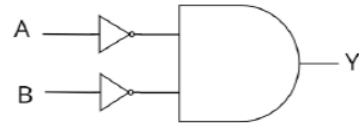


Figure 2

CO3	(a)	For the square wave generator in figure 1, determine V_{TH} and V_{TL} values of the Schmitt Trigger. (Upper and lower threshold values)	[3+3]
CO3	(b)	Determine the period, time constant and duty cycle of the square wave generator circuit, given that the frequency is 100 Hz	[6]
CO1	(c)	Design an equivalent CMOS logic circuit for figure 2 using the minimum number of NMOS and PMOS transistors. Also, provide the truth table showing the 'ON' and 'OFF' states of each MOSFET for every input test case.	[8]

Question (Set B)

[20]

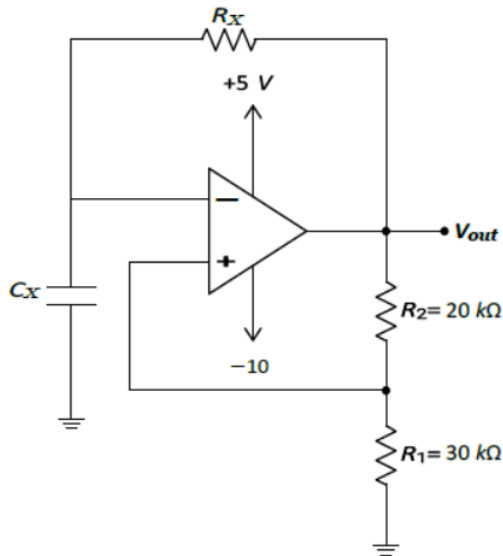


Figure 1

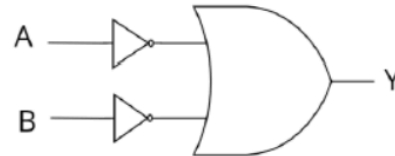


Figure 2

CO3	(a)	For the square wave generator in figure 1, determine V_{TH} and V_{TL} values of the Schmitt Trigger. (<i>Upper and lower threshold values</i>)	[3+3]
CO3	(b)	Determine the <i>period</i> , <i>time constant</i> and <i>duty cycle</i> of the square wave generator circuit, given that the <i>frequency</i> is 100 Hz	[6]
CO1	(c)	Design an equivalent CMOS logic circuit for figure 2 using the minimum number of NMOS and PMOS transistors. Also, provide the truth table showing the 'ON' and 'OFF' states of each MOSFET for every input test case.	[8]

Solutions:

Question (Set A)

[20]

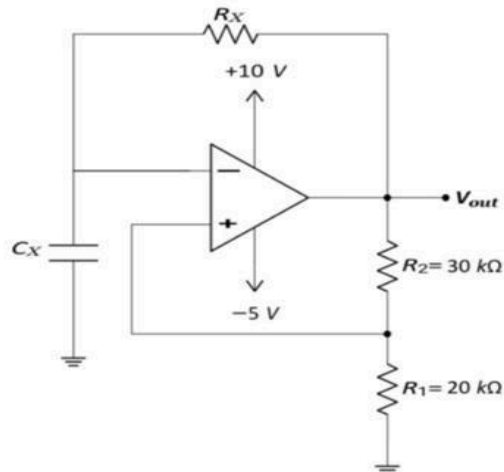


Figure 1

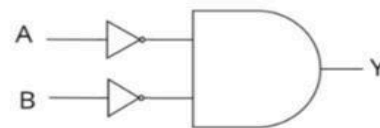


Figure 2

CO3	(a)	For the square wave generator in figure 1 , determine V_{TH} and V_{TL} values of the Schmitt Trigger. (<i>Upper and lower threshold values</i>)	[3+3]
CO3	(b)	Determine the <i>period</i> , <i>time constant</i> and <i>duty cycle</i> of the square wave generator circuit, given that the <i>frequency</i> is 100 Hz	[6]
CO1	(c)	Design an equivalent CMOS logic circuit for figure 2 using the minimum number of NMOS and PMOS transistors. Also, provide the truth table showing the 'ON' and 'OFF' states of each MOSFET for every input test case.	[8]

Soln:

(a) Upper Threshold, $V_{TH} = \frac{R_1}{R_1 + R_2} V_H$
 $= \frac{20K}{20K + 30K} \times 10V$
 $V_{TH} = 4V$

Lower Threshold, $V_{TL} = \frac{R_1}{R_1 + R_2} V_L$
 $= \frac{20K}{20K + 30K} \times (-5V)$
 $V_{TL} = -2V$

(b) given, $f = 100 \text{ Hz}$

$$\therefore \text{period, } T = \frac{1}{f} = \frac{1}{100} = 10 \text{ ms.}$$

$$\begin{aligned} \rightarrow T_1 &= R_x C_x \ln \left| \frac{V_H - V_{TL}}{V_H - V_{TH}} \right| \\ &= R_x C_x \ln \left| \frac{10 + 2}{10 - 4} \right| \\ &= R_x C_x \ln 2 \end{aligned}$$

$$\begin{aligned} \rightarrow T_2 &= R_x C_x \ln \left| \frac{V_L - V_{TH}}{V_L - V_{TL}} \right| \\ &= R_x C_x \ln \left| \frac{-5 - 4}{-5 + 2} \right| \\ &= R_x C_x \ln 3 \end{aligned}$$

$$\therefore T = T_1 + T_2$$

$$\Rightarrow 10 \text{ ms} = R_x C_x (\ln 2 + \ln 3)$$

$$\Rightarrow R_x C_x = \frac{10 \text{ ms}}{\ln 2 + \ln 3} = 5.58 \text{ ms}$$

$$\begin{aligned} \therefore T_1 &= 5.58 \ln 2 \\ &= 3.86 \text{ ms} \end{aligned}$$

$$\therefore \text{Time constant, } \tau = R_x C_x = 5.58 \text{ ms}$$

$$\text{Duty cycle, } D = \frac{T_1}{T} \times 100\%$$


$$= \frac{3.86}{10} \times 100\%$$

$$= 38.6\%$$

(Ans.)

(c)
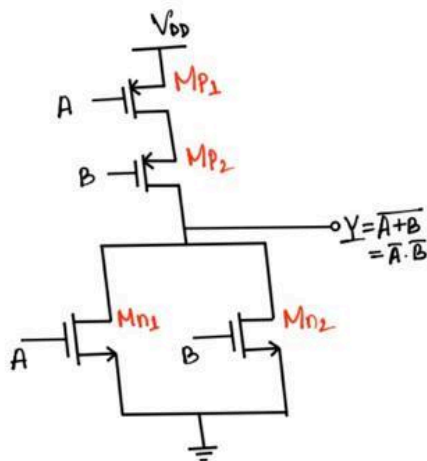
$$\text{given, } Y = \overline{A \cdot B} = \overline{A + B}$$



A	B	Y	Mn ₁	Mn ₂	Mp ₁	Mp ₂
0	0	1	OFF	OFF	ON	ON
0	1	0	OFF	ON	ON	OFF
1	0	0	ON	OFF	OFF	ON
1	1	0	ON	ON	OFF	OFF

Question (Set B)

[20]

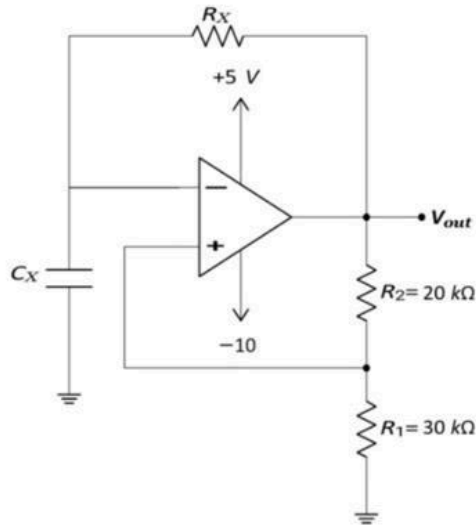


Figure 1

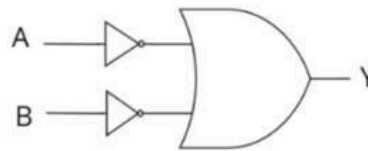


Figure 2

CO3	(a)	For the square wave generator in figure 1 , determine V_{TH} and V_{TL} values of the Schmitt Trigger. (<i>Upper and lower threshold values</i>)	[3+3]
CO3	(b)	Determine the <i>period</i> , <i>time constant</i> and <i>duty cycle</i> of the square wave generator circuit, given that the <i>frequency</i> is 100 Hz	[6]
CO1	(c)	Design an equivalent CMOS logic circuit for figure 2 using the minimum number of NMOS and PMOS transistors. Also, provide the truth table showing the 'ON' and 'OFF' states of each MOSFET for every input test case.	[8]

Soln:

(a) Upper threshold, $V_{TH} = \frac{R_1}{R_1 + R_2} V_H = \frac{30k}{30k + 20k} \times 5V$

$$V_{TH} = 3V$$

Lower threshold, $V_{TL} = \frac{R_1}{R_1 + R_2} V_L = \frac{30k}{30k + 20k} \times (-10V)$

$$V_{TL} = -6V$$

(b)

given, $f = 100 \text{ Hz}$

$$\therefore \text{period, } T = \frac{1}{f} = \frac{1}{100} = 10 \text{ ms.}$$

$$\begin{aligned} \rightarrow T_1 &= R_x C_x \ln \left| \frac{V_H - V_{TL}}{V_H - V_{TH}} \right| \\ &= R_x C_x \ln \left| \frac{5+6}{5-3} \right| \\ &= R_x C_x \ln(5.5) \end{aligned}$$

$$\begin{aligned} \rightarrow T_2 &= R_x C_x \ln \left| \frac{V_L - V_{TH}}{V_L - V_{TL}} \right| \\ &= R_x C_x \ln \left| \frac{-10-3}{-10+6} \right| \\ &= R_x C_x \ln(3.25) \end{aligned}$$

$$\therefore T = T_1 + T_2$$

$$\Rightarrow 10 \text{ ms} = R_x C_x (\ln 5.5 + \ln 3.25)$$

$$\Rightarrow R_x C_x = \frac{10 \text{ ms}}{\ln 5.5 + \ln 3.25} = 3.46 \text{ ms}$$


$$\begin{aligned} \therefore T_1 &= 3.46 \ln(5.5) \\ &= 5.91 \text{ ms} \end{aligned}$$

$$\therefore \text{Time constant, } \tau = R_x C_x = 3.46 \text{ ms}$$

$$\begin{aligned} \text{Duty cycle, } D &= \frac{T_1}{T} \times 100\% \\ &= \frac{5.91}{10} \times 100\% \\ &= 59.1\% \end{aligned}$$


(Ans:)

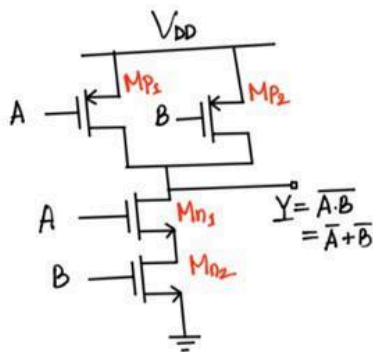(c) $Y = \overline{A+B} = \overline{A \cdot B}$



A	B	Y	Mn ₁	Mn ₂	Mp ₁	Mp ₂
0	0	1	OFF	OFF	ON	ON
0	1	1	OFF	ON	ON	OFF
1	0	1	ON	OFF	OFF	ON
1	1	0	ON	ON	OFF	OFF

Schmitt Trigger [QSH]

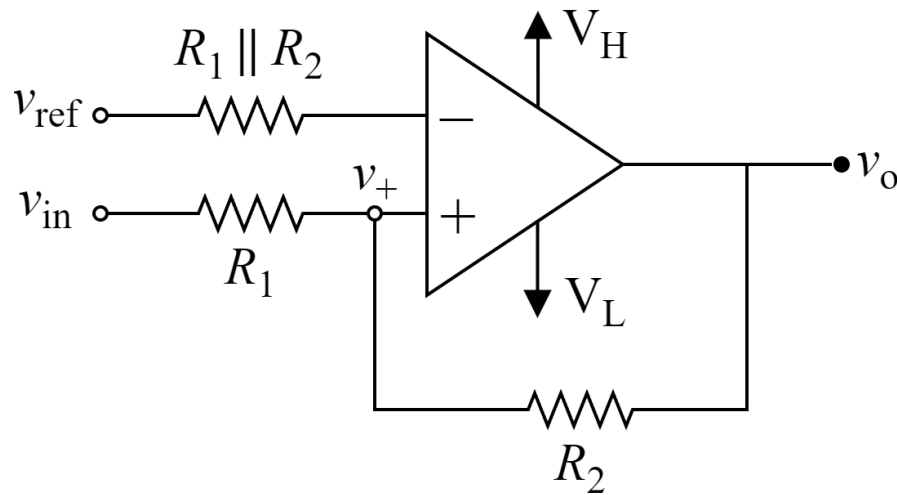

Given,

For Set A : $V_H = 10V$, $V_L = -10V$, $v_{ref} = 2V$

For Set B : $V_H = 9V$, $V_L = -9V$, $v_{ref} = 3V$

(a)	CO3	What type of schmitt trigger circuit is this (inverting or non-inverting)?	[2]
(b)	CO3	Draw the VTC (v_{in} vs v_o) of this schmitt trigger circuit. Correctly label the plot (Depict V_{TH}, V_{TL}, V_H, V_L, Hysteresis Width). Given, For Set A : $R_1 = 1k\Omega$ and $R_2 = 2k\Omega$ for question (b) only. For Set B : $R_1 = 1k\Omega$ and $R_2 = 3k\Omega$ for question (b) only.	[8]
(c)	CO3	Determine the value of R_1 and R_2. Given, For Set A : $R_1 \parallel R_2 = 4k\Omega$; $V_{TH} = 5V$ and $V_{TL} = 0V$ is required, for question (c) only. For Set B : $R_1 \parallel R_2 = 6k\Omega$; $V_{TH} = 9V$ and $V_{TL} = 0V$ is required, for question (c) only.	[10]

Solution:

Set A

(a) Non-inverting

$$(b) \quad V_{TH} = v_{ref} \left(\frac{R_1 + R_2}{R_2} \right) + \left(-\frac{R_1}{R_2} \right) V_L$$


$$V_{TH} = 8 \text{ V}$$

$$V_{TL} = v_{ref} \left(\frac{R_1 + R_2}{R_2} \right) + \left(-\frac{R_1}{R_2} \right) V_H$$

$$V_{TL} = -2 \text{ V}$$

$$\text{Hysteresis Width} = V_{TH} - V_{TL}$$
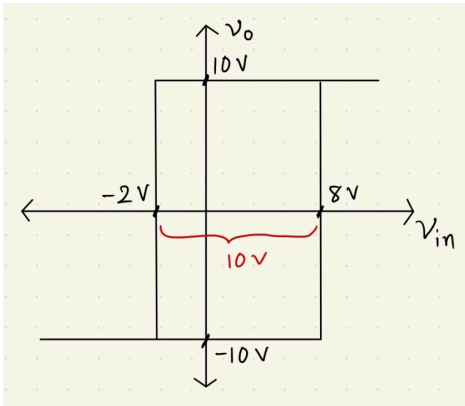
$$\text{Hysteresis Width} = 10 \text{ V}$$



$$(c) \text{Hysteresis Width} = \left(-\frac{R_1}{R_2} \right) (V_L - V_H)$$

$$\Rightarrow \frac{R_1}{R_2} = \frac{1}{4}$$

$$\Rightarrow R_2 = 4R_1$$

$$\text{Given, } R_1 \parallel R_2 = 4k\Omega$$

$$\Rightarrow R_1 = 5k\Omega$$

$$\Rightarrow R_2 = 20k\Omega$$

Set B

(a) Non-inverting

$$(b) \quad V_{TH} = v_{ref} \left(\frac{R_1 + R_2}{R_2} \right) + \left(-\frac{R_1}{R_2} \right) V_L$$


$$V_{TH} = 7 \text{ V}$$

$$V_{TL} = v_{ref} \left(\frac{R_1 + R_2}{R_2} \right) + \left(-\frac{R_1}{R_2} \right) V_H$$

$$V_{TL} = 1 \text{ V}$$

$$\text{Hysteresis Width} = V_{TH} - V_{TL}$$
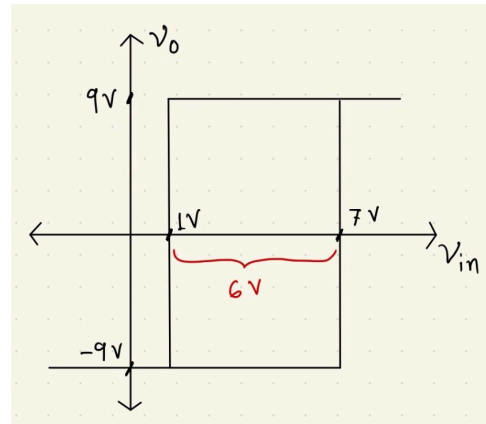
$$\text{Hysteresis Width} = 6 \text{ V}$$



$$(c) \text{Hysteresis Width} = \left(-\frac{R_1}{R_2} \right) (V_L - V_H)$$

$$\Rightarrow \frac{R_1}{R_2} = \frac{1}{2}$$

$$\Rightarrow R_2 = 2R_1$$

$$\text{Given, } R_1 \parallel R_2 = 6k\Omega$$

$$\Rightarrow R_1 = 9k\Omega$$

$$\Rightarrow R_2 = 18k\Omega$$

ADC [SZZ]

Solution:

(a)

Set A & Set B

Quantization Range (V)	Digital Output	LED 1	LED 0
0 - 1.25	00	OFF	OFF
1.25 - 3.75	01	OFF	ON
3.75 - 6.25	10	ON	OFF
6.25 - 10	11	ON	ON

(b)

Set A

Time (s)	Sampled value (V)	Quantization Range (V)	Digital Output
0.0	5.00	3.75 - 6.25	10
0.5	7.40	6.25 - 10	11
3.0	5.71	3.75 - 6.25	10
4.0	1.22	0 - 1.25	00

Set B

Time (s)	Sampled value (V)	Quantization Range (V)	Digital Output
4.0	1.22	0 - 1.25	00
3.0	5.71	3.75 - 6.25	10
0.5	7.40	6.25 - 10	11
0.0	5.00	3.75 - 6.25	10

