
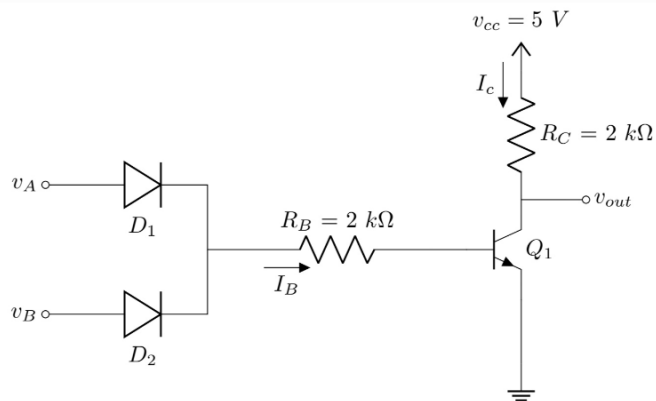


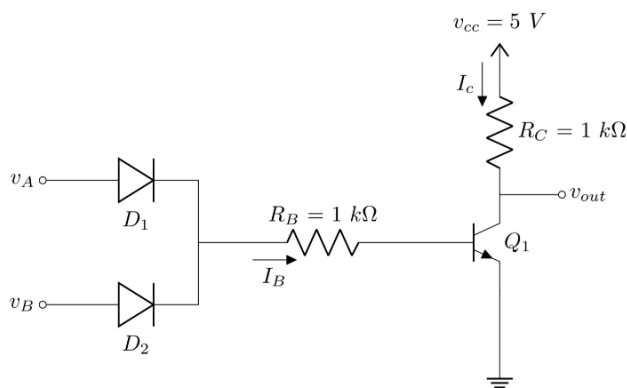

Set-A

Question-1

(a) Q_1 saturation $\Rightarrow V_{BE} = 0.8V$

$$V_D = 0.7V$$

$$V_{CE} = 0.1V$$

$$\text{thus, } I_B = \frac{5 - 0.7 - 0.8}{1k} = 3.5mA$$

$$I_C = \frac{5 - 0.1}{1k} = 4.9mA$$

Set-B

Question-4

(a) Q_1 saturation $\Rightarrow V_{BE} = 0.8V$

$$V_D = 0.7V$$

$$V_{CE} = 0.1V$$

$$\text{thus, } I_B = \frac{5 - 0.7 - 0.8}{2k} = 1.75mA$$

$$I_C = \frac{5 - 0.1}{2k} = 2.45mA$$

(b) When $V_A = V_B = 5V$,

D_1 - forward bias

D_2 - forward bias

Q_1 - Saturation

(b) When $V_A = V_B = 5V$,

D_1 - forward bias

D_2 - forward bias

Q_1 - Saturation

(c) Power = $5 \times (3.5 + 4.9) = 42mW$

(c) Power = $5 \times (1.75 + 2.45) = 21mW$

(d) When $V_A = V_B = 0.1V$

D_1 - reverse bias

D_2 - reverse bias

Q_1 - cutoff

(d) When $V_A = V_B = 0.1V$

D_1 - reverse bias

D_2 - reverse bias

Q_1 - cutoff

(e) NOR Gate

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

(e) NOR Gate

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

Set-A Q(2)

(a)

D_A just ON, $T_1 D_2 T_2$ ON

$$\therefore V_P = V_A + V_N + 0.6 = 10.6 + V_N$$

$$\text{again, } V_P = V_{BE2} + V_{D2} + V_{BE1} = 0.8 + 0.7 + 0.7 = 2.2$$

$$\therefore V_N + 10.6 = 2.2 \rightarrow V_N = -8.4$$

$$\hookrightarrow |V_N| = 8.4 \quad \boxed{\text{Ans}}$$

(b)

$$\frac{10 - V_{C1}}{14k\Omega} = \left(\frac{V_{C1} - 2.2}{15k\Omega} \right) \times 26$$

$$\hookrightarrow V_{C1} = 2.509V$$

$$I_1 = \frac{10 - 2.509}{14k\Omega} = 0.535mA \quad \boxed{\text{Ans}}$$

$$I_{B2} = I_1 - \frac{0.8}{90k\Omega} = 0.526mA \quad \boxed{\text{Ans}}$$

$$I_3 = \frac{10 - 0.1}{2k\Omega} = 4.95mA \quad \boxed{\text{Ans}}$$

$$\text{Load} \rightarrow I_1 = \frac{10 - 0.8}{29k\Omega} = 0.317mA \quad \boxed{\text{Ans}}$$

(c)

$$\frac{I_3 + 40 \times 0.317}{0.526} < 25$$

$$\hookrightarrow I_3 = 6.81mA \rightarrow \frac{10 - 0.1}{R_C} = 6.81mA \rightarrow R_C = 1.45k\Omega$$

$$\text{OR, } \boxed{1.454k\Omega < R_C < 1.525k\Omega}$$

Single value or Range both valid.

Set-B (Q3)

(a)

D_A just ON, $T_1 D_2 T_2$ ON

$$\therefore V_P = V_A + V_N + 0.6 = 10.6 + V_N$$

$$\text{again, } V_P = V_{BE2} + V_{D2} + V_{BE1} = 0.8 + 0.7 + 0.7 = 2.2$$

$$\therefore V_N + 10.6 = 2.2 \rightarrow V_N = -8.4 \rightarrow |V_N| = 8.4V$$

$\boxed{\text{Ans}}$

(b)

$$\frac{10 - V_{C1}}{13k\Omega} = 36 \times \left(\frac{V_{C1} - 2.2}{16k\Omega} \right)$$

$$\hookrightarrow V_{C1} = 2.458V$$

$$I_1 = \frac{10 - 2.458}{13k\Omega} = 0.58mA \quad \boxed{\text{Ans}}$$

$$I_{B2} = I_1 - \frac{0.8}{80k\Omega} = 0.57mA \quad \boxed{\text{Ans}}$$

$$I_3 = \frac{10 - 0.1}{2.4k\Omega} = 4.125mA \quad \boxed{\text{Ans}}$$

$$\text{Load} \rightarrow I_1 = \frac{10 - 0.8}{29k\Omega} = 0.317mA \quad \boxed{\text{Ans}}$$

(c)

$$\frac{I_3 + 40 \times 0.317}{0.57} < 35$$

$$\hookrightarrow I_3 = 7.27mA \rightarrow \frac{10 - 0.1}{R_C} = 7.27mA \rightarrow R_C = 1.362k\Omega$$

$$\text{OR, } \boxed{1.362k\Omega < R_C < 1.424k\Omega}$$

Single value or Range both valid.

Midterm - Set A

Q3

(a)

both inputs are low = 0.1V

$Q_1 \rightarrow$ saturation, $Q_2 \rightarrow$ cutoff, $Q_3 \rightarrow$ cutoff

$Q_4 \rightarrow$ Forward active

$$\text{individual demand, } i'_L = 0.4 \times \frac{5 - 2.3}{6k\Omega}$$

$$= 0.18 \text{ mA}$$

} (2)

$$\text{total demand, } i_{E4} = \cancel{2 \times 0.18} 8 \times 0.18$$

$$= 1.44 \text{ mA}$$

So, total supply = 1.44 mA

$$\text{Now, } I_{B4} = \frac{1.44}{(\beta + 1)} = \frac{1.44}{41} = 0.0351 \text{ mA} \rightarrow (2)$$

$$\text{Now, } I_{B4} = \frac{5 - V_{B4}}{21k\Omega}$$

$$\cancel{V_{B4} = 4.02} \quad \boxed{V_{B4} = 4.93 \text{ V}} \rightarrow (2)$$

$$\boxed{V_o = 3.53 \text{ V}} \rightarrow (2)$$

(b)

$$I_{B4} = 0.0351 \text{ mA}$$

$$I_{C4} = 40 \times 0.0351 = 1.404 \text{ mA}$$

(2)

$$\text{So, } I_{C4} = \frac{5 - V_{C4}}{20 \Omega}, \quad V_{C4} = 4.97192 \text{ V.}$$


$$V_{C4} = 4.97192 \text{ V} \quad \left. \right\} (2)$$

$$V_{B4} = 4.23 \text{ V.}$$

$$\text{So, } (V_{CE})_4 = 0.742 > 0.1. \quad \left. \right\} (2)$$

So, Q_4 in forward active [verified]

(c)

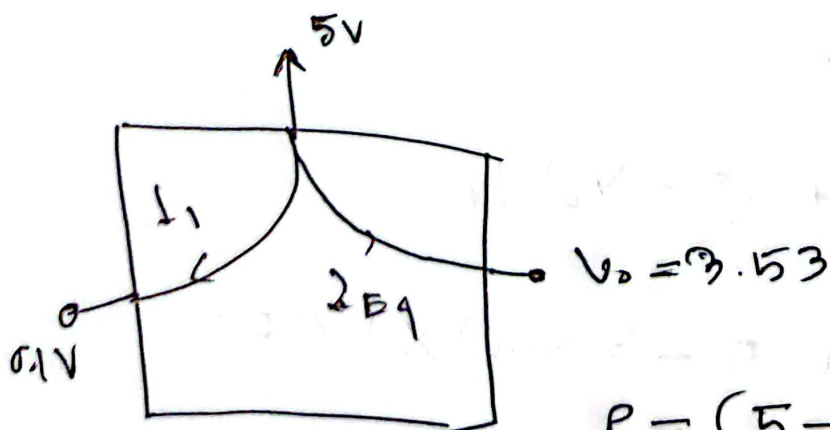

$$I_{B4} = 1.14 \text{ mA} \quad \left. \right\} (2)$$

$$I_1 = \frac{5 - 0.1}{6 \text{ k}\Omega}$$

$$= 0.683 \text{ mA}$$

$$P = (5 - 0.1) \times I_1 + (5 - 3.53) \times I_{B4}$$

$$P = 5.4635 \text{ mW} \quad \left. \right\} (4)$$

$$\frac{9c + B}{Q2}$$

Q1

$$i_L = 0.3 \times \frac{5 - 2.3}{51} = 0.162 \text{ mA}, \quad i_{B4} = 1.458 \text{ mA}$$

$$I_{B4} = \frac{1.458}{31} = 0.047 \text{ mA}$$

$$\therefore V_{B4} = 4.906 \text{ V.}$$

$$\boxed{V_0 = 3.506 \text{ V}}$$

Q2 $I_{C4} = 30 \times 0.047 = 1.41 \text{ mA}$

$$I_{C4} = \frac{5 - V_{C4}}{46}, \quad V_{C4} = 4.9436 \text{ V.}$$

$$V_{B4} = 4.206, \quad V_{C4} = 0.7376791$$

is in active mode

Q3


$$P = (5 - 0.1) \times I_L + (5 - V_0) I_{B4}$$

$$= (5 - 0.1) \times 0.162 + 5(-3.506) \times 1.458$$

$$\boxed{P = 6.2 \text{ mW}}$$

Set A

Question 4

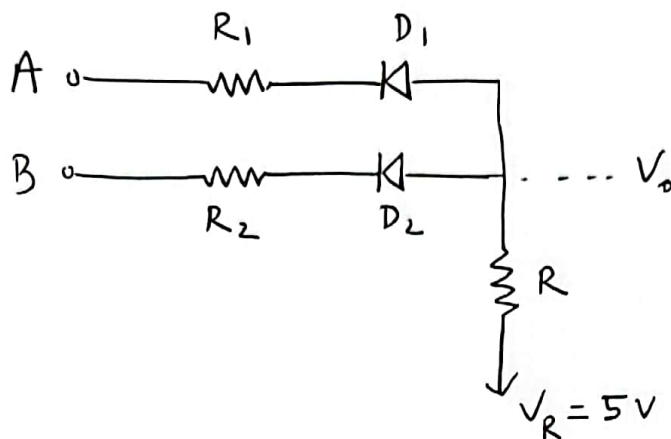

$$R_1 = R_2 = 680 \Omega$$

$$R = 91 \text{ k}\Omega$$

(a) $A = B = 5 \text{ V}$

D_1, D_2 both OFF.

$V_0 = 5 \text{ V}$ **Set B: 5 V**

(b) $A = 5 \text{ V}, B = 0 \text{ V}$

or $A = 0 \text{ V}, B = 5 \text{ V}$

$$\frac{(V_0 - 0.7) - 0}{R_1} = \frac{V_R - V_0}{R}$$

$$\Rightarrow \frac{V_0 - 0.7}{R_1} = \frac{5 - V_0}{R}$$

$$\Rightarrow V_0 = 0.7319 \text{ V} \text{ (upto 4 decimal place)}$$

Set B: 0.7252 V


(c) $A = B = 0 \text{ V}$

$$2 \times \frac{V_0 - 0.7}{R_1} = \frac{5 - V_0}{R}$$

$$\Rightarrow V_0 = 0.716 \text{ V} \text{ (upto 4 decimal place)}$$

Set B: 0.7126 V

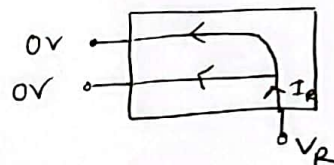(b) Maximum power dissipation when $A = B = 0 \text{ V}$



$$P = (V_R - 0) \times I_R$$

$$= (5 - 0) \times \frac{5 - V_0(0,0)}{R} \text{ **Set B: 0.2257**}$$

$$= 5 \times \frac{5 - 0.716}{91} = \text{0.2354 mW} \text{ (upto 4 d.p.)}$$

(c) You can neglect and set $R_1 = R_2 = 0$ at the beginning of the calculation.

Then, $V_0 = 0.7 \text{ V}$

and, $P = 5 \times \frac{5 - 0.7}{R} < 1$

$$\Rightarrow R > 21.5 \text{ k}\Omega$$

$\therefore R_{\min} = 21.5 \text{ k}\Omega$

Set B: same

Or, you can write 'P' as a function of ' R ', ' R_1 ', ' R_2 ' and eliminate R_1, R_2 by comparing with ' R '. This should result in the same value but with a lot of calculation.