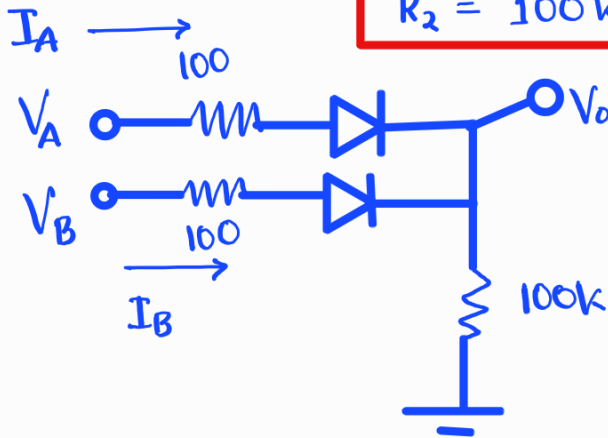


Set-A Q₁

① We choose $R_1 = 100\Omega$

$$R_2 = 100k\Omega$$



Case 1 Both input low

$$V_O = 0V$$

Case 2 Single input high

$$V_A = 5V, V_B = 0V$$

$$\text{at node } V_O, \frac{V_O}{100k} = \frac{5 - V_O - 0.7}{100}$$

$$\Rightarrow V_O = 4.2957V$$

Case 3 Both inputs high

$$\text{at node } V_O, \frac{V_O}{100k} = 2 \times \frac{5 - V_O - 0.7}{100}$$

$$\Rightarrow V_O = 4.2978V$$

② Maximum power consumption for case-3 (both input high)

$$I_A = I_B = \frac{5 - 4.2978 - 0.7}{100}$$


$$= 2.2 \times 10^{-5} A$$

$$P = 2 \times I_A \times (5 - 0) = 2.2 \times 10^{-1} W$$

Set-B Q₄

① We choose $R_1 = 100\Omega$

$$R_2 = 100k\Omega$$

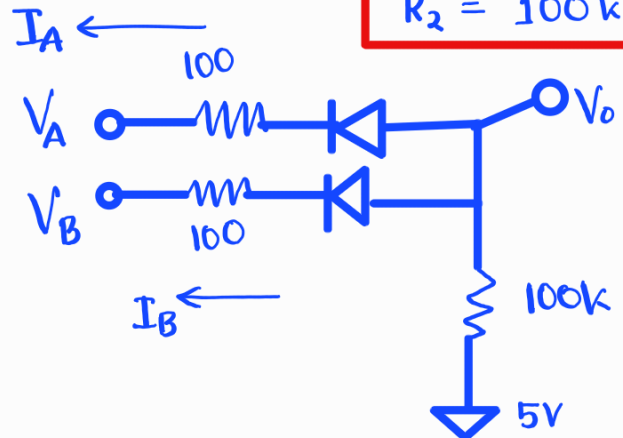

Case 1 Both input high

$$V_O = 5V$$

Case 2 Single input high

$$V_A = 5V, V_B = 0V$$

$$\text{at node } V_O, \frac{5 - V_O}{100k} = \frac{V_O - 0.7}{100}$$

$$\Rightarrow V_O = 0.7043 V$$

Case 3 Both inputs low

$$\text{at node } V_O, \frac{5 - V_O}{100k} = 2 \times \frac{V_O - 0.7}{100}$$

$$\Rightarrow V_O = 0.70214 V$$

② Maximum power consumption for case-3 (both input low)

$$I_A = I_B = \frac{0.70214 - 0.7}{100}$$


$$= 2.14 \times 10^{-5} A$$

$$P = 2 \times I_A \times (5 - 0) = 2.14 \times 10^{-1} W$$

Set-A (Q2)

(a) NAND gate.

V_A	V_B	T_1	T_2	V_O
0	0	cut	cut	5V
0	5	cut		5V
5	0		cut	5V
5	5	sat.	sat.	0.4V

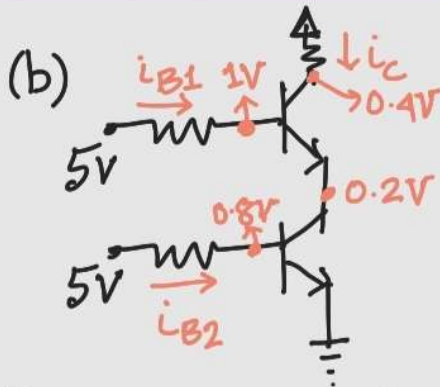

$$P = i_{B1} \times (5-0) + i_{B2} \times (5-0) + i_C \times (5-0)$$


$$220 = \frac{5-1}{0.4} \times 5 + \frac{5-0.8}{0.4} \times 5 + \frac{5-0.4}{R_c} \times 5$$

$$\Rightarrow R_c = 0.196 \text{ k}\Omega$$

Set-B (Q3)

(a) NAND gate.


V_A	V_B	T_1	T_2	V_O
0	0	cut	cut	5V
0	5	cut		5V
5	0		cut	5V
5	5	sat.	sat.	0.4V

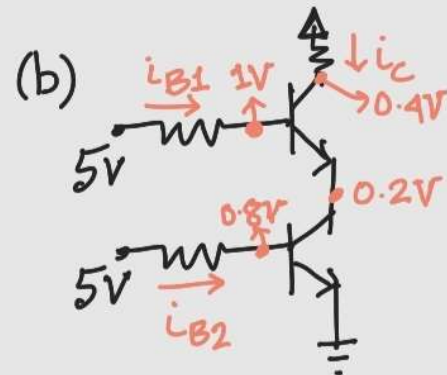

$$P = i_{B1} \times (5-0) + i_{B2} \times (5-0) + i_C \times (5-0)$$


$$175 = \frac{5-1}{0.3} \times 5 + \frac{5-0.8}{0.3} \times 5 + \frac{5-0.4}{R_c} \times 5$$
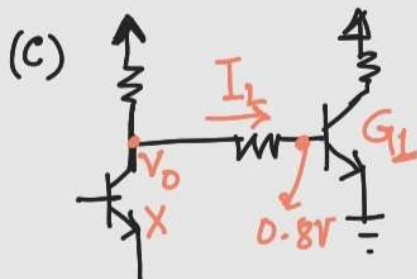
$$\Rightarrow R_c = 0.6 \text{ k}\Omega$$



$$\frac{5-V_O}{R_c} = 5 \times \frac{V_O-0.8}{5}$$

$$\Rightarrow V_O = 4.3117 \text{ V}$$

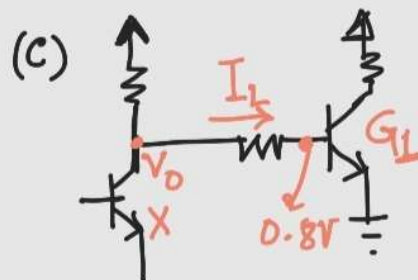

$$\frac{5-V_O}{R_c} = 6 \times \frac{V_O-0.8}{6}$$

$$\Rightarrow V_O = 3.425 \text{ V}$$

Set-A Q₃

(a) $0.2V$ $V_{CE}(\text{sat})$

(b)

$$\frac{V_P - 0.7 - 0.2}{2} \times 3 + \frac{V_P + 12}{R_2 + R_B} = \frac{V_{CC} - V_P}{R_1}$$

$$\Rightarrow V_P = 1.3016V$$

$$i_L = \frac{V_P - 0.7 - 0.2}{2} = 0.2008 \text{ mA}$$

$$I_1 = \frac{V_{CC} - V_P}{R_1} = 0.7132 \text{ mA}$$

$$I_2 = \frac{V_P + 12}{R_2 + R_B} = 0.1108 \text{ mA}$$

$$I_B = I_C = 0$$

Set-B Q₁

(a) $0.2V$ $V_{CE}(\text{sat})$

(b)

$$\frac{V_P - 0.7 - 0.2}{2} \times 3 + \frac{V_P + 12}{R_2 + R_B} = \frac{V_{CC} - V_P}{R_1}$$

$$\Rightarrow V_P = 1.1841V$$

$$i_L = \frac{V_P - 0.7 - 0.2}{2} = 0.1421 \text{ mA}$$

$$I_1 = \frac{V_{CC} - V_P}{R_1} = 0.5408 \text{ mA}$$

$$I_2 = \frac{V_P + 12}{R_2 + R_B} = 0.1146 \text{ mA}$$

$$I_B = I_C = 0$$

(c) All inputs are low

$$V_B = V_P - I_2 R_2$$

$$= -0.9144V$$

$$V_{BE} < V_r ; \text{Cutoff}$$

(If answered with all high)

$$I_1 = \frac{V_{CC} - 0.8}{R_1 + R_2} = 0.32 \text{ mA}$$

$$I_B = I_1 - \frac{0.8 + 12}{R_B} = 0.192 \text{ mA}$$

$$I_C = \frac{V_{CC} - 0.2}{R_L} = 3.933 \text{ mA}$$

$$I_C / I_B = 20.49 < \beta_F (\text{Sat})$$

(c) All inputs are low

$$V_B = V_P - I_2 R_2$$

$$= -0.5349V$$

$$V_{BE} < V_r ; \text{Cutoff}$$

(If answered with all high)

$$I_1 = \frac{V_{CC} - 0.8}{R_1 + R_2} = 0.32 \text{ mA}$$

$$I_B = I_1 - \frac{0.8 + 12}{R_B} = 0.192 \text{ mA}$$

$$I_C = \frac{V_{CC} - 0.2}{R_L} = 3.933 \text{ mA}$$

$$I_C / I_B = 20.49 < \beta_F (\text{Sat})$$

$$V_{B0} = 0.8, V_0 = 0.1,$$

$$V_{C1} = 0.9, V_{B2} = 1.6, V_{B1} = 2.3$$

Set-A-Q4

$$\textcircled{a} \quad I_1 = \frac{6-2.3}{10k} = 0.37 \text{ mA}$$

$$I_{EX} = I_{EY} = \beta_F I_1 = 0.037 \text{ mA}$$

$$I_{B2} = I_1 + 2 I_{EX} = 0.444 \text{ mA}$$

$$I_2 = \frac{5-0.9}{4k} = 1.275 \text{ mA}$$

$$I_{E2} = I_2 + I_{B2} = 1.72 \text{ mA}$$

$$I_{B0} = I_{E2} - I_4 = 1.32 \text{ mA}$$

$$I_3 = \frac{6-0.1}{5k} = 1.18 \text{ mA}$$

Individual Load current,

$$I_L = I_1' = \frac{6-0.9}{10k} = 0.51 \text{ mA}$$

$$\therefore \frac{I_3 + N I_L}{I_{B0}} \leq \beta_F$$

$$\hookrightarrow \frac{1.18 + N(0.51)}{1.32} \leq 30$$

$$\hookrightarrow N = \lfloor 75.33 \rfloor = 75$$

$$\begin{aligned} \textcircled{b} \quad P &= 6(I_1 + I_2 + I_3 + I_{EX} + I_{EY}) \\ &\quad + 10(0.1)(I_L) \\ &= 17.904 \text{ mW} \end{aligned}$$

$$\textcircled{c} \quad \frac{1.18 + 70(0.51)}{1.32} < \beta_F$$

$$\hookrightarrow 27.939 < \beta_F$$

Set-B-Q2

$$\textcircled{a} \quad I_1 = \frac{5-2.3}{5} = 0.54 \text{ mA}$$

$$I_{EX} = I_{EY} = \beta_F I_1 = 0.054 \text{ mA}$$

$$I_{B2} = I_1 + 2 I_{EX} = 0.648 \text{ mA}$$

$$I_2 = \frac{5-0.9}{2k} = 2.05 \text{ mA}$$

$$I_{E2} = I_2 + I_{B2} = 2.698 \text{ mA}$$

$$I_{B0} = I_{E2} - I_4 = 2.298 \text{ mA}$$

$$I_3 = \frac{5-0.1}{4k} = 1.225 \text{ mA}$$

Individual Load current,

$$I_L = I_1' = \frac{5-0.9}{5k} = 0.82 \text{ mA}$$

$$\therefore \frac{I_3 + N I_L}{I_{B0}} \leq \beta_F$$

$$\hookrightarrow \frac{1.225 + N(0.82)}{2.298} \leq 40$$

$$\hookrightarrow N = \lfloor 110.60 \rfloor = 110$$

$$\begin{aligned} \textcircled{b} \quad P &= 6(I_1 + I_2 + I_3 + I_{EX} + I_{EY}) \\ &\quad + 20(0.1)(I_L) \\ &= 25.178 \text{ mW} \end{aligned}$$

$$\textcircled{c} \quad \frac{1.225 + 100(0.82)}{2.298} < \beta_F$$

$$\hookrightarrow 36.216 < \beta_F$$